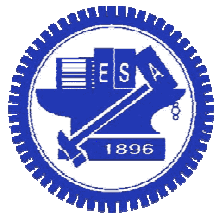


Register Transfer Level Design



Chun-Jen Tsai
National Chiao Tung University
12/20/12

Review of Digital Systems

- ❑ A digital system is a sequential logic system constructed with flip-flops and gates
- ❑ To specify a large digital system with a state table is very difficult
- ❑ A large system is usually decomposed into modular subsystems
 - Each subsystem is composed of basic components such as: registers, decoders, multiplexers, arithmetic elements, and control logic.
 - These basic components are interconnected with datapaths and control signals.

Descriptions of Digital Designs

☐ Structural

- The lowest and most detailed level
- Specified in terms of physical components and their interconnection

☐ Register Transfer Level

- Imply a certain hardware configuration
- Specified in terms of the registers, operations performed, and control that sequences the operations.

☐ Algorithmic-based behavioral

- The most abstract level
- Most appropriate for simulating complex to verify design ideas and explore tradeoffs

Register Transfer Level Notation (1/2)

- ❑ A digital system is represented at the register transfer level (RTL) when it is specified by the following three components:
 - The set of **registers** in the system.
 - The **operations** performed on the data in the registers.
 - The **controllers** that supervise the sequence of operations.
- ❑ Notations:
 - Letters and numbers denotes a register (ex. R2, PC, ...)
 - Parentheses denotes register bits (ex. R1(7:0), R2(4))
 - Arrow (\leftarrow) denotes data transfer (ex. $R1 \leftarrow R2$)
 - Comma separates parallel operations (ex. $R1 \leftarrow R2, R0 \leftarrow R3$)
 - Brackets [] – Specifies a memory address (ex. $R0 \leftarrow M[100]$)

Register Transfer Level Notation (2/2)


- ❑ A conditional statement governing a register transfer operation is symbolized with an if-then statement

- Example:

If ($T1 = 1$) then ($R2 \leftarrow R1$)

where $T1$ is a control signal generated in the controller.

 - The statement can also be expressed as $T1: (R2 \leftarrow R1)$
- A logic diagram for the statement is as follows:



Register Operations

- ❑ The type of operations most often encountered in digital systems are as follows:
 - Transfer: transfer data from one register to another.
 - Arithmetic: perform arithmetic on data in registers.
 - Logic: perform bit manipulation of data in registers.
 - Shift: shift data between registers.
- ❑ Example of operations:
 - $R1 \leftarrow R1 + R2$ // Add contents of R2 to R1
 - $R3 \leftarrow R3 + 1$ // Increment R3 by 1
 - $R4 \leftarrow \text{shr } R4$ // Shift right R4
 - $R5 \leftarrow 0$ // Clear R5 to 0

Operator Notations in HDL

- ❑ The notation for various operations in RTL models (text, VHDL, and Verilog) are as follows:

Operation	Text RTL	VHDL	Verilog
Combinational assignment	=	<= (concurrent)	assign = (nonblocking)
Register transfer	←	<= (concurrent)	<= (nonblocking)
Addition	+	+	+
Subtraction	−	−	−
Bitwise AND	^	and	&
Bitwise OR	∨	or	
Bitwise XOR	⊕	xor	^
Bitwise NOT	¬ (overline)	not	~
Shift left (logical)	sl	sll	<<
Shift right (logical)	sr	srl	>>
Vectors/registers	A(3:0)	A(3 down to 0)	A[3:0]
Concatenation		&	{ , }

RTL Model and Logic Synthesis

- ❑ An RTL model is a “program” that describes the operations (behavior) of a digital circuit based on register operations
- ❑ An RTL model can be translated into a gate-level model by a process called “logic synthesis.”
 - A gate-level model usually goes through the mapping and the place-and-route processes to become an implementation model for a specific target hardware.
- ❑ A continuous assignment in an RTL model is synthesized into combinational circuit:

assign S = A + B;


where S is a signal wire.

Logic Synthesis of Cyclic Behavior

- ❑ A cyclic behavior may imply a combinational or a sequential circuit, depending on whether the event control expression is level sensitive or edge sensitive

 
- Examples:

```
always@(A or B or S)
begin
    if (S) Y = A;
    else Y = B;
end
```



synthesized into a combinational circuit block.
 
```
always@(posedge clk)
begin
    A <= A + B;
end
```




translates into a synchronous sequential circuit block.

Blocking vs. Non-blocking Behavior


- ❑ Blocking operation is for combinational behavior:
 
```
always@(posedge clk)  
begin  
    A = A + B;  
    D = A;  
end
```




- ❑ Non-blocking operation is for sequential behavior:
 
```
always@(posedge clk)  
begin  
    A <= A + B;  
    D <= A;  
end
```




HDL-based Design Flow

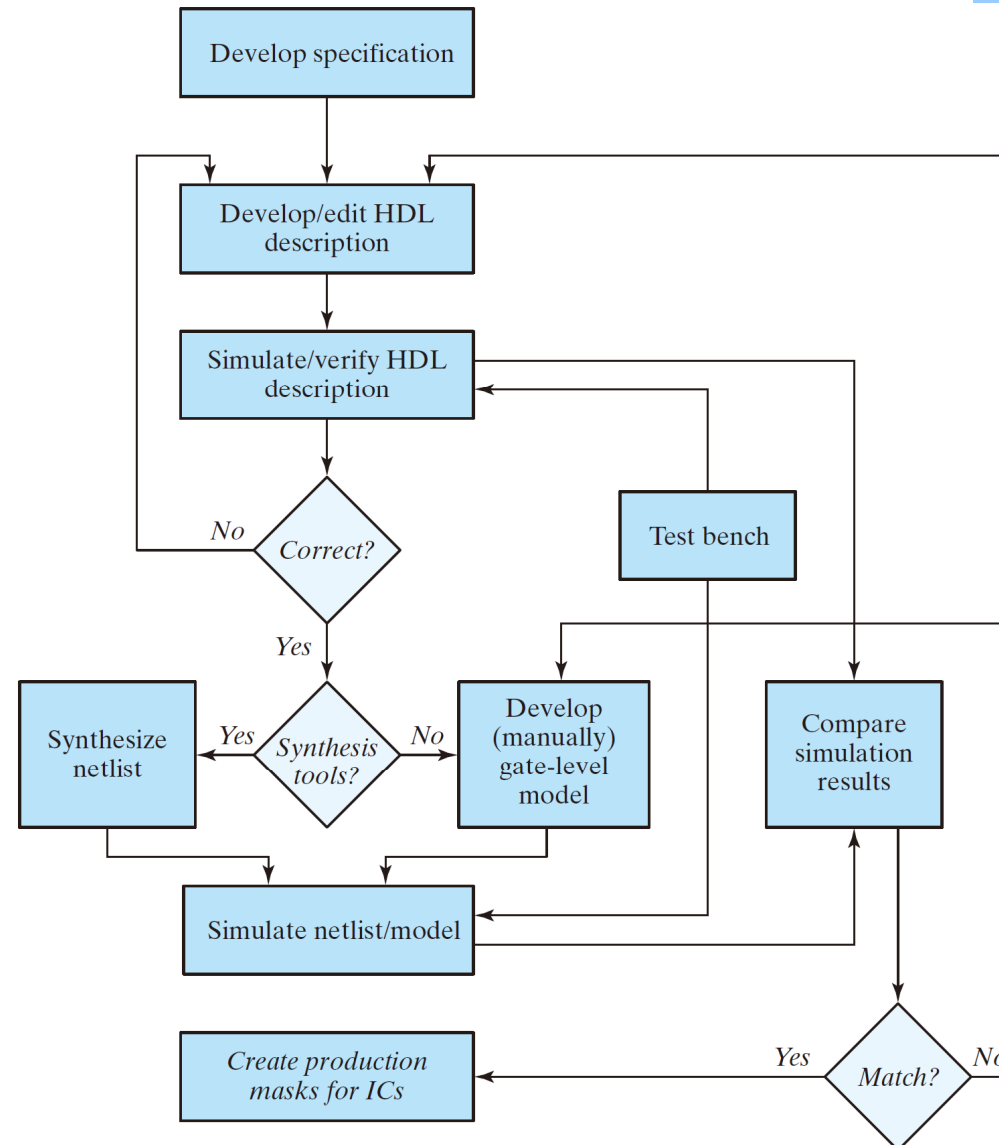

Digital Systems = FSM + DP (1/2)

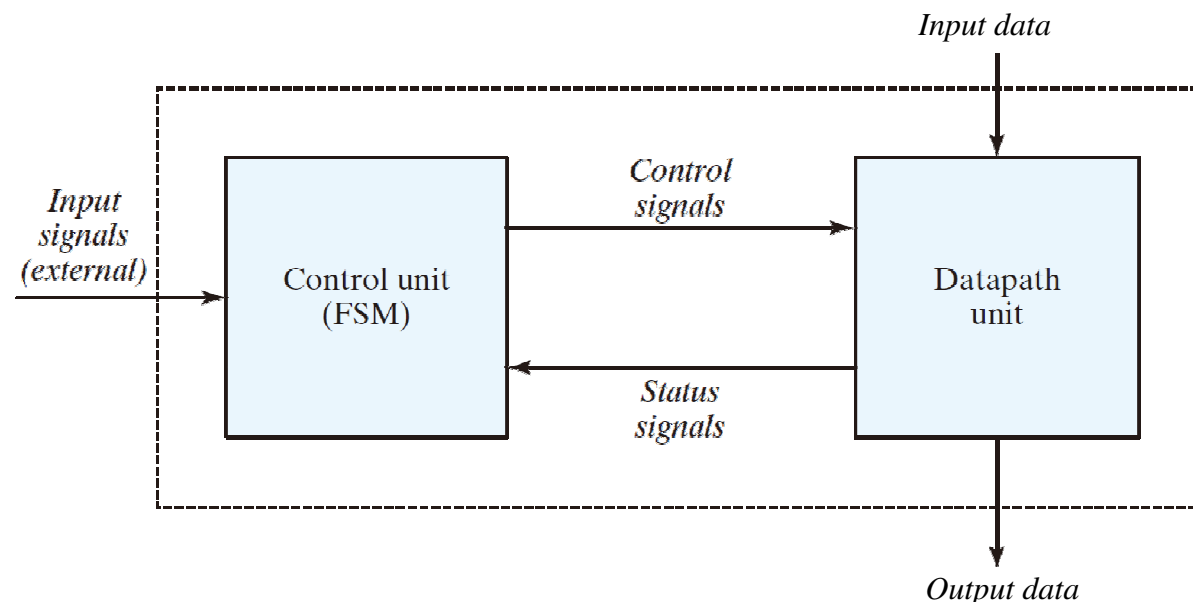- ❑ Logic design of digital system can be divided into two distinct parts:
 - Datapath design – the design of the digital circuits that perform the data-processing operations
 - Controller design – the design of the control circuits that arrange the sequence in which the actions are performed.




Digital Systems = FSM + DP (2/2)


- ❑ The control logic that generates the signals for sequencing the operations in the data path unit is a finite state machine (FSM).
 - The control sequence and datapath tasks of the digital system are specified by means of a hardware algorithm.
- ❑ A flowchart that has been developed specifically to define digital hardware algorithm is called an algorithmic state machine (ASM) chart.

ASM Charts

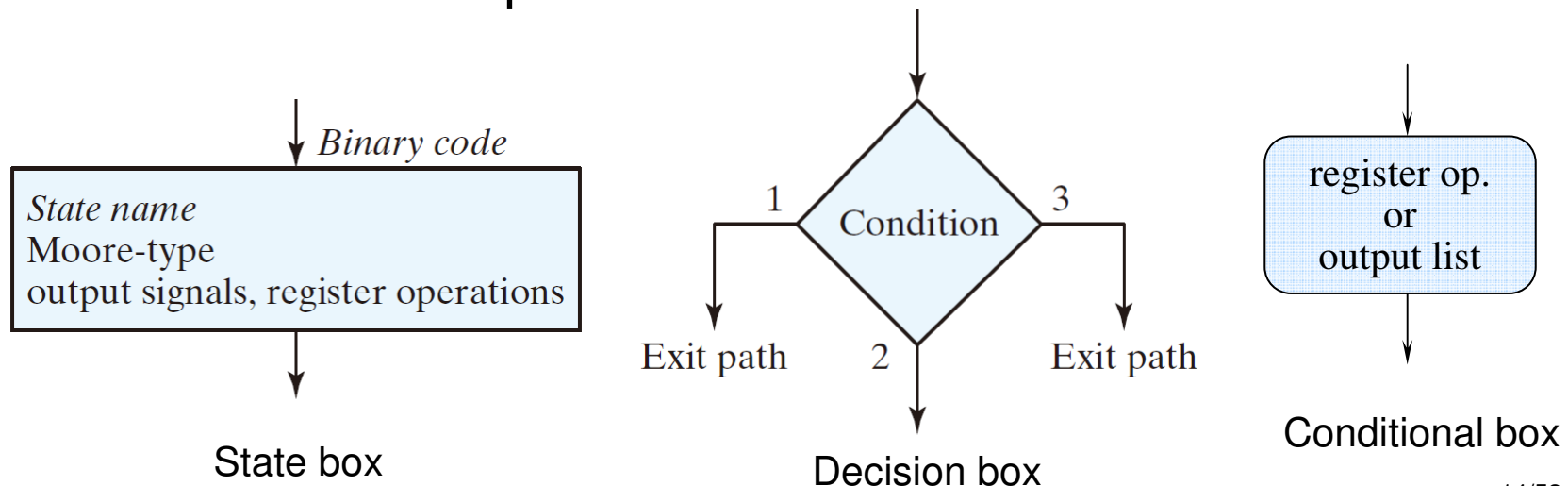- ❑ The ASM chart is composed of three basic elements:
 - State box
 - Decision box
 - Conditional box
- ❑ They are connected by directed edges indicating the sequential precedence and evolution of the states as the machine operates.





AMS Chart Examples

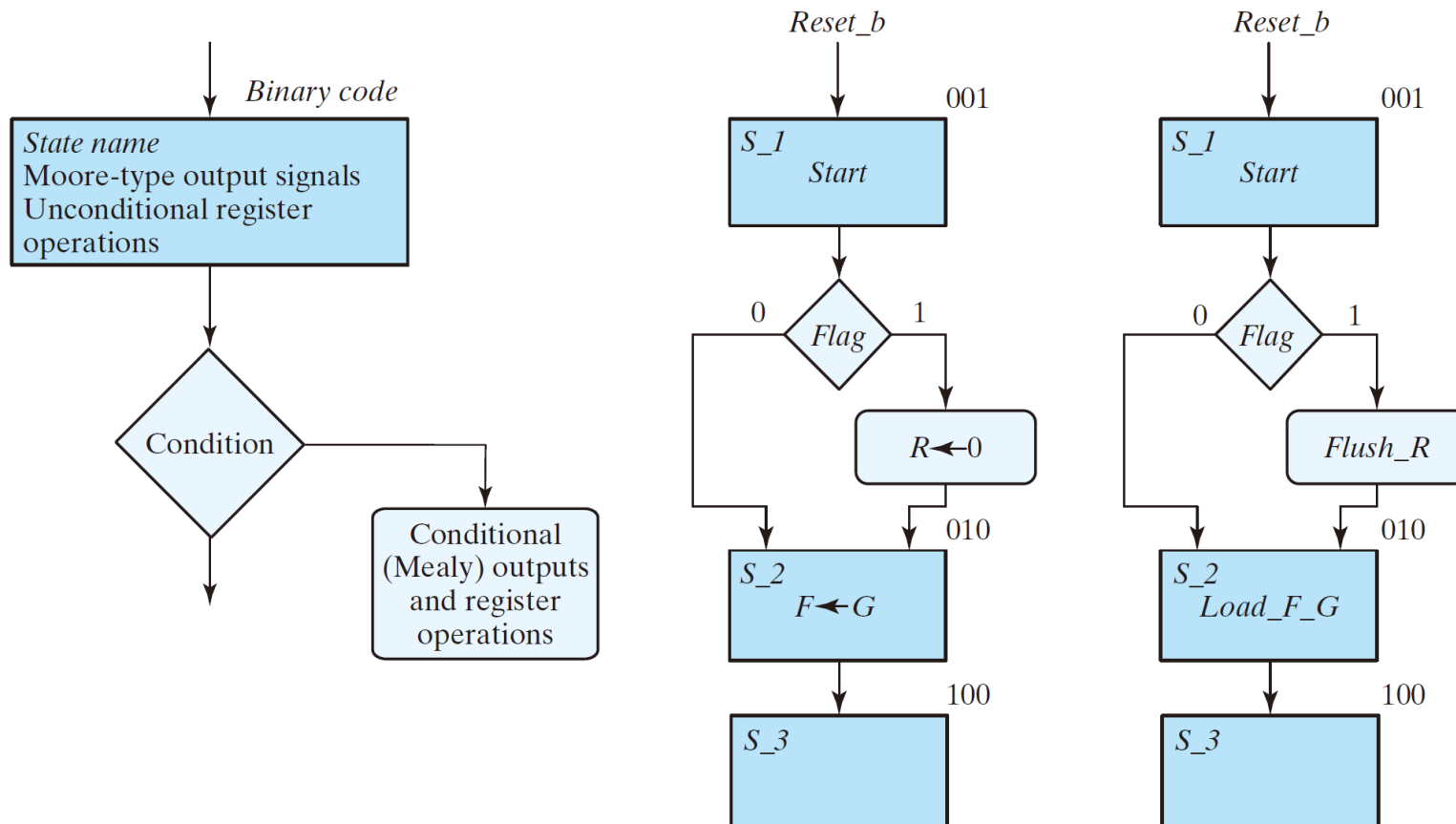


ASM Blocks

 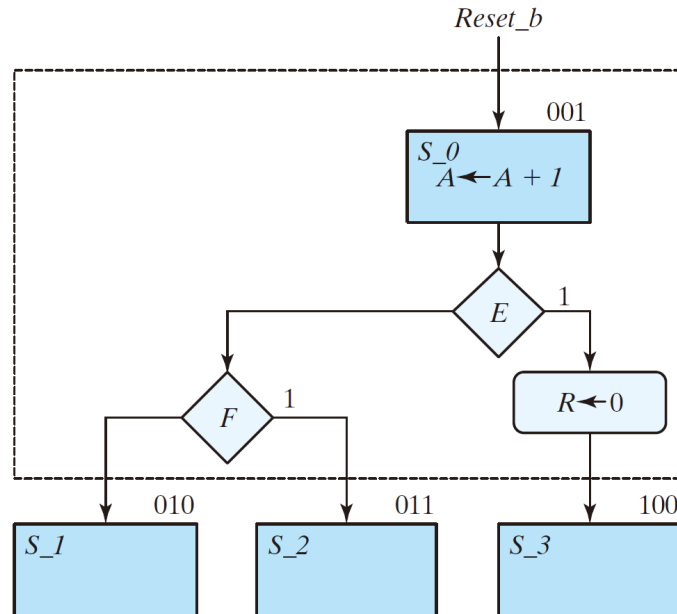- ❑ An ASM chart is composed of many ASM blocks
 - Each block contains exactly one state box and describes the state of the system during one clock-pulse interval.
 - May have decision boxes and conditional boxes.
 - One entrance path, one or more exit paths.



Timing Considerations

 - ❑ The timing for all register and flip-flop in digital system is controlled by a master-clock generator
- ❑ All the operations within an ASM block must be completed within one clock period
 - All operations in a block are concurrent



ASMD Chart


- ❑ An Algorithmic State Machine and Datapath (ASMD) chart is a variant to a ASM chart:
 - ASMD charts do not list register operations in state boxes.
 - The edges of an ASMD charts are annotated with register operations that are concurrent with the state transition indicated by the edge.
 - An ASMD chart includes conditional boxes identifying the signals which control the register operations that annotate the edges of the chart.
 - An ASMD chart associates register operations with state transitions rather than with state.

ASMD Chart Design

- ❑ Designing an ASMD chart has three steps:
 - Form an ASM chart displaying only how the inputs to the controller determine its state transitions.
 - Convert the ASM chart to an ASMD chart by annotating the edges of ASM chart to indicate the concurrent register operations of the datapath unit.
 - Modify the ASMD chart to identify the control signals that are generated by the controller which cause the indicated register operations in the datapath unit.


ASMD Chart Design Example

- ❑ A binary counter with two flags:

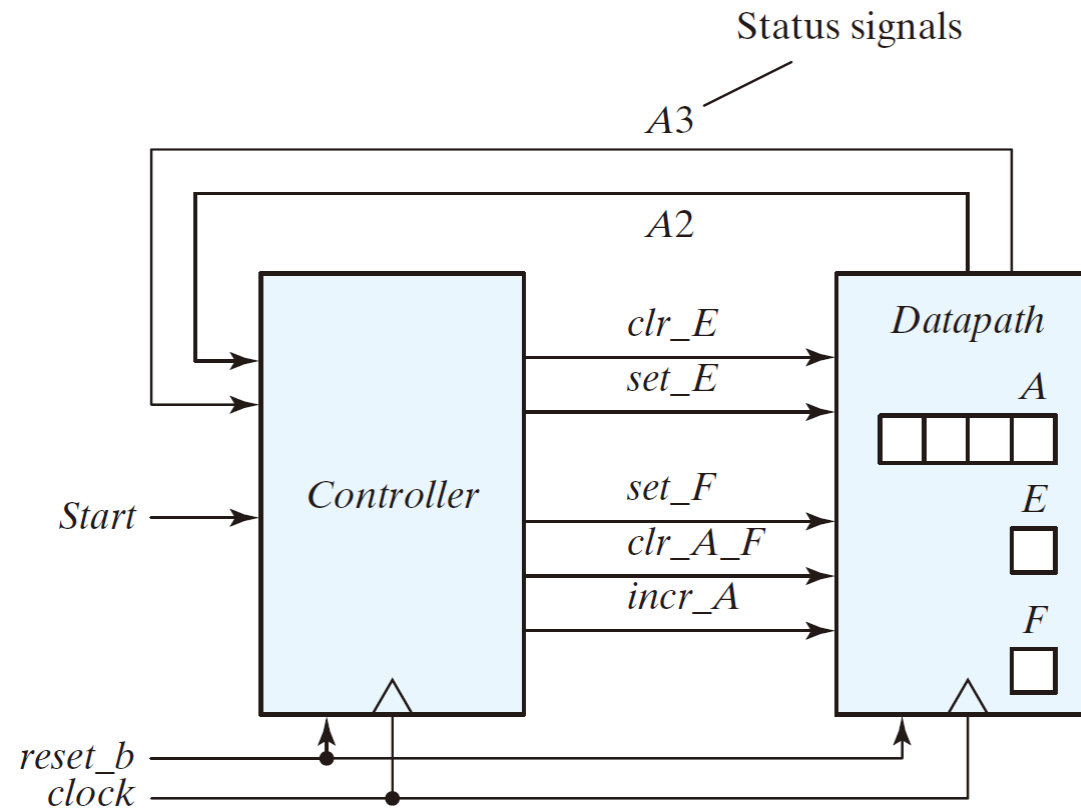


ASM Chart for State Transitions

 - ❑ State transitions with different reset behaviors:




asynchronous reset

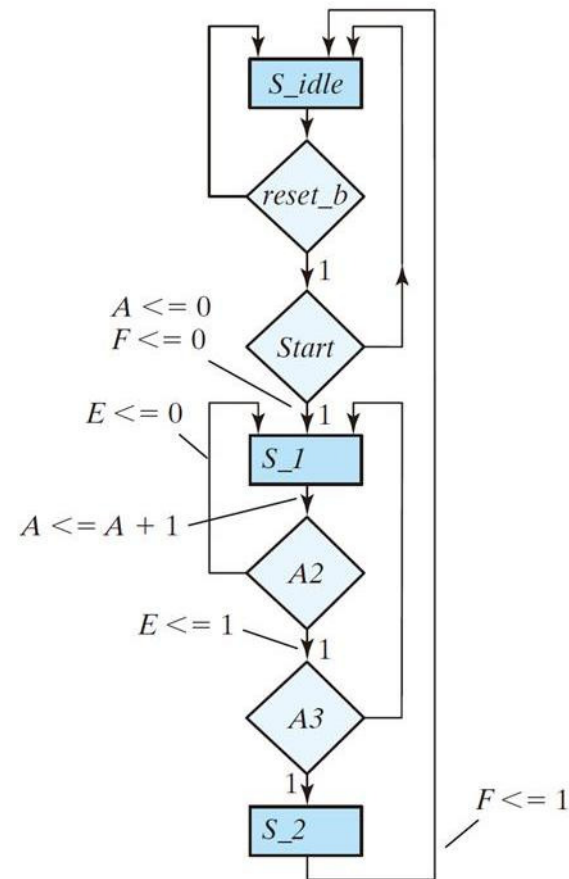

synchronous reset

Complete Controller ASM Chart

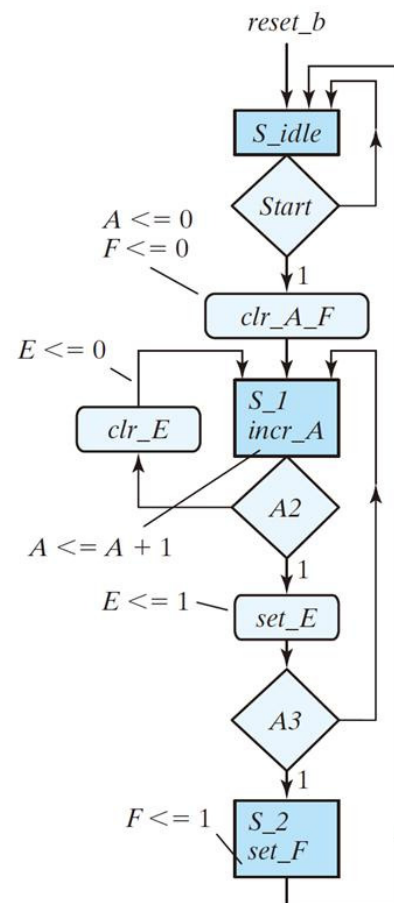- ❑ A complete controller generates various control signals throughout state transitions:



Example of Operations


- An example run of controller operation is as follows:

Sequence of Operations for Design Example


progress of timing clock ticks

Counter				Flip-Flops		Conditions	State
A_3	A_2	A_1	A_0	E	F		
0	0	0	0	1	0	$A_2 = 0, A_3 = 0$	S_1
0	0	0	1	0	0		
0	0	1	0	0	0		
0	0	1	1	0	0		
0	1	0	0	0	0	$A_2 = 1, A_3 = 0$	
0	1	0	1	1	0		
0	1	1	0	1	0		
0	1	1	1	1	0		
1	0	0	0	1	0	$A_2 = 0, A_3 = 1$	
1	0	0	1	0	0		
1	0	1	0	0	0		
1	0	1	1	0	0		
1	1	0	0	0	0	$A_2 = 1, A_3 = 1$	S_2
1	1	0	1	1	0		
1	1	0	1	1	1		S_{idle}

Datapath and Controller

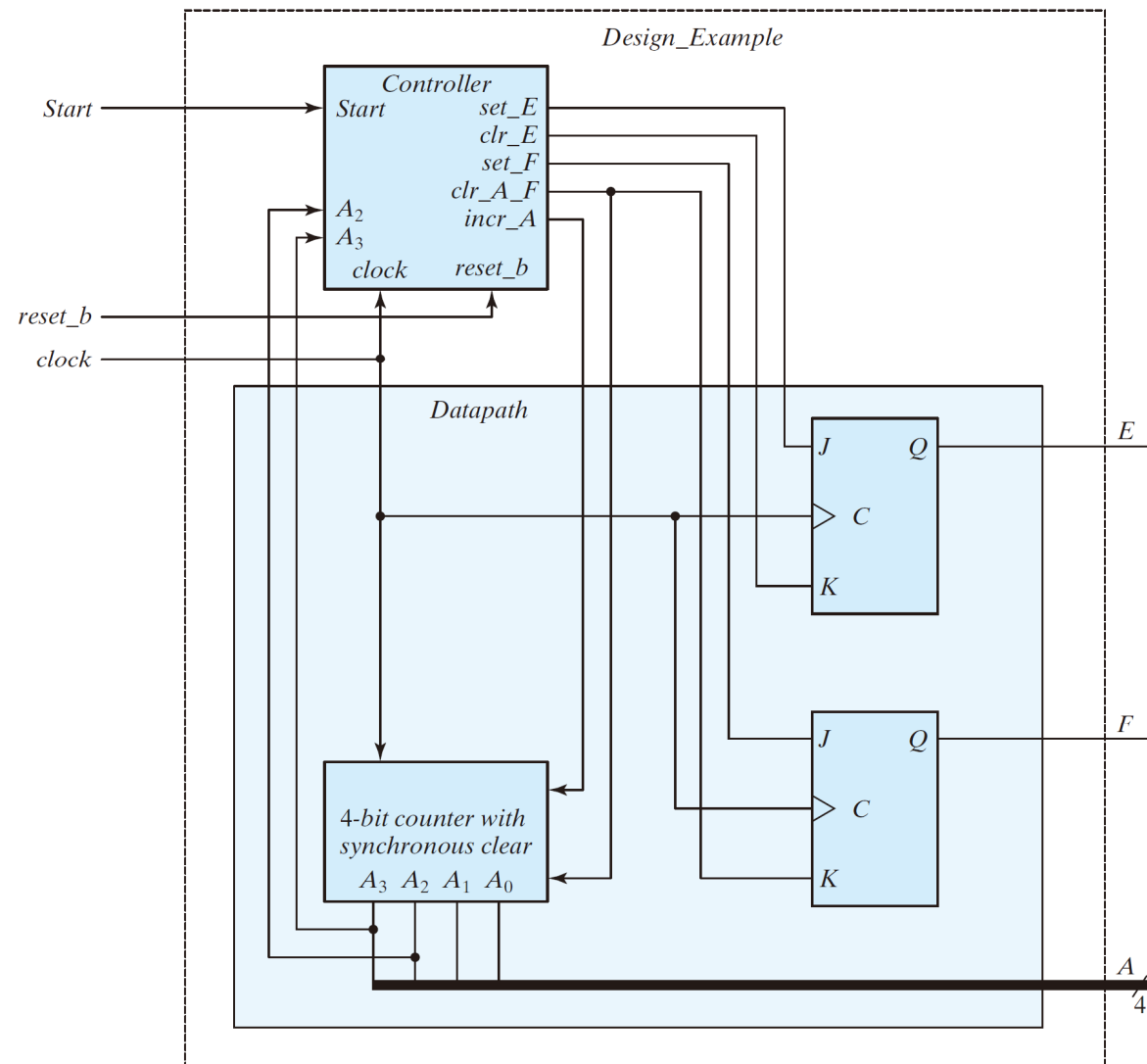

Register Transfer Level Description

 

$S_idle \longrightarrow S_1, clr_A_F:$

$A \longleftarrow 0, F \longleftarrow 0$

$S_1 \longrightarrow S_1, incr_A:$

$A \longleftarrow A + 1$

$if (A_2 = 1) then set_E:$

$E \longleftarrow 1$

$if (A_2 = 0) then clr_E:$

$E \longleftarrow 0$

$S_2 \longrightarrow S_idle, set_F:$

$F \longleftarrow 1$

State Table and FF Input Equations

□ State flip-flops (D-type) input equations:

- G_1 input equation: $D_{G_1} = S_I \cdot A_2 \cdot A_3$
- G_0 input equation: $D_{G_0} = Start \cdot S_idle + S_I$

State Table for the Controller


	Present State		Inputs			Next State		Outputs				
Present-State Symbol	G_1	G_0	$Start$	A_2	A_3	G_1	G_0	set_E	clr_E	set_F	clr_A_F	$incr_A$
S_idle	0	0	0	X	X	0	0	0	0	0	0	0
S_idle	0	0	1	X	X	0	1	0	0	0	1	0
S_I	0	1	X	0	X	0	1	0	1	0	0	1
S_I	0	1	X	1	0	0	1	1	0	0	0	1
S_I	0	1	X	1	1	1	1	1	0	0	0	1
S_2	1	1	X	X	X	0	0	0	0	1	0	0

Output Equations

□ To derive the five output function, we can exploit the fact that state 10 is not used, which simplifies the equation for clr_A_F :


- $set_E = S_1 \cdot A_2$
- $clr_E = S_1 \cdot A'_2$
- $set_F = S_2$
- $clr_A_F = Start \cdot S_idle$
- $incr_A = S_1$

Logic Diagram of the Controller

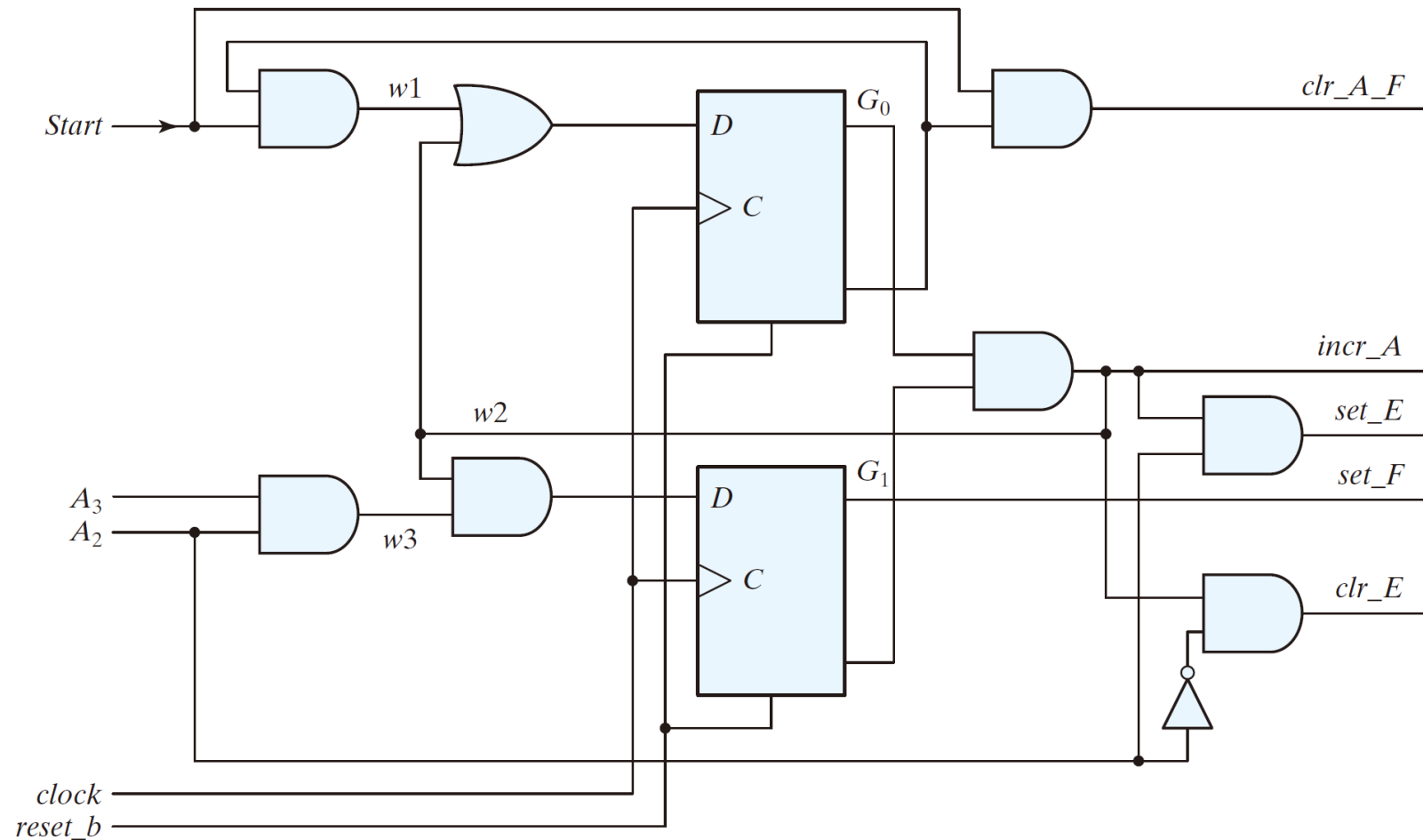

Waveform Simulation

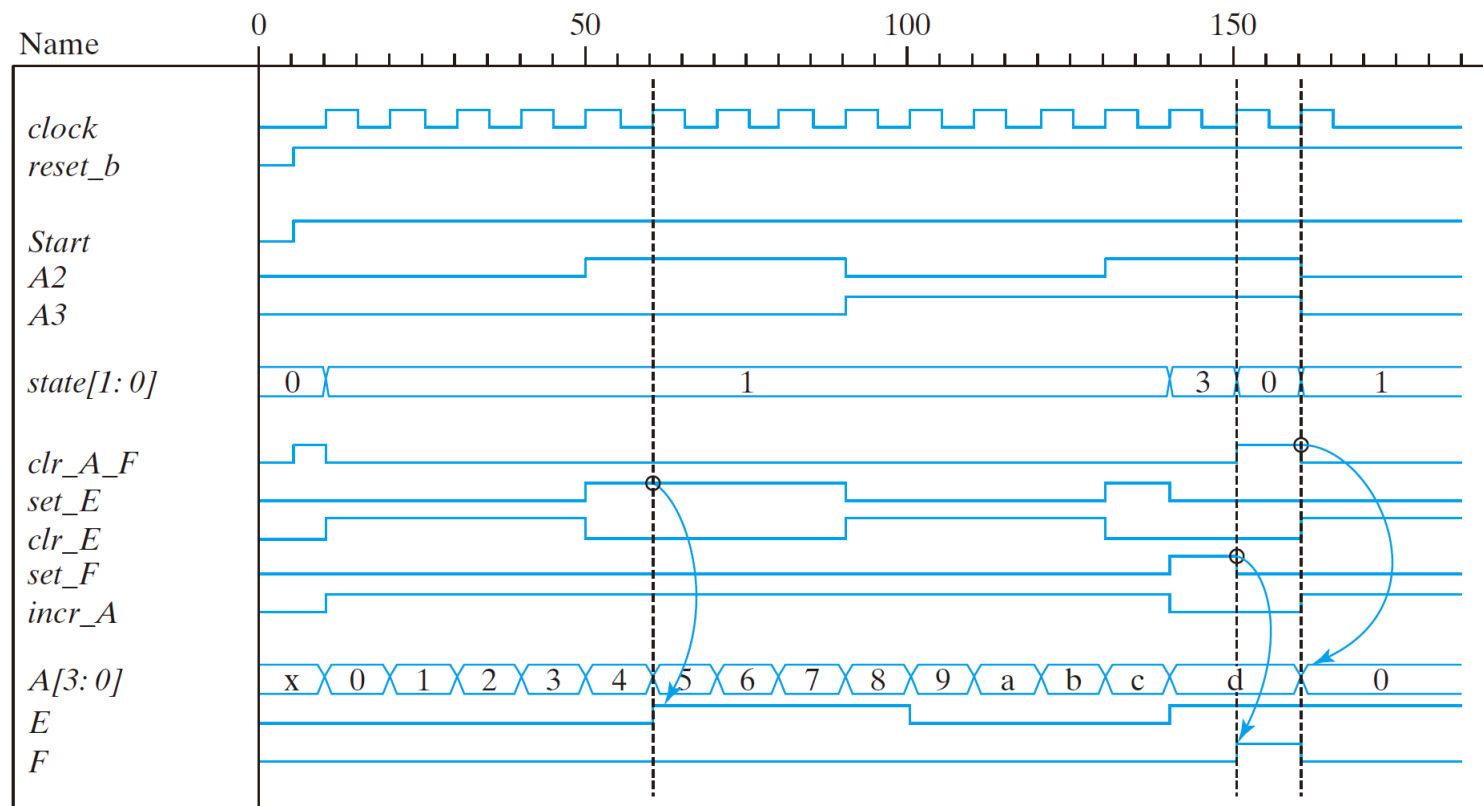- ❑ Verification of a digital design begins with functional waveform simulation:



Sequential Binary Multiplier


- ❑ Example behavior of sequential binary multiplication of 10111 and 10011 is as follows:

	10111	→ multiplicand
×	10011	→ multiplier
	10111	
	10111	
	00000	
	00000	
+	10111	
	110110101	→ product


The product obtained from the multiplication of two binary numbers of n bits each can have up to $2n$ bits.

Register Configuration


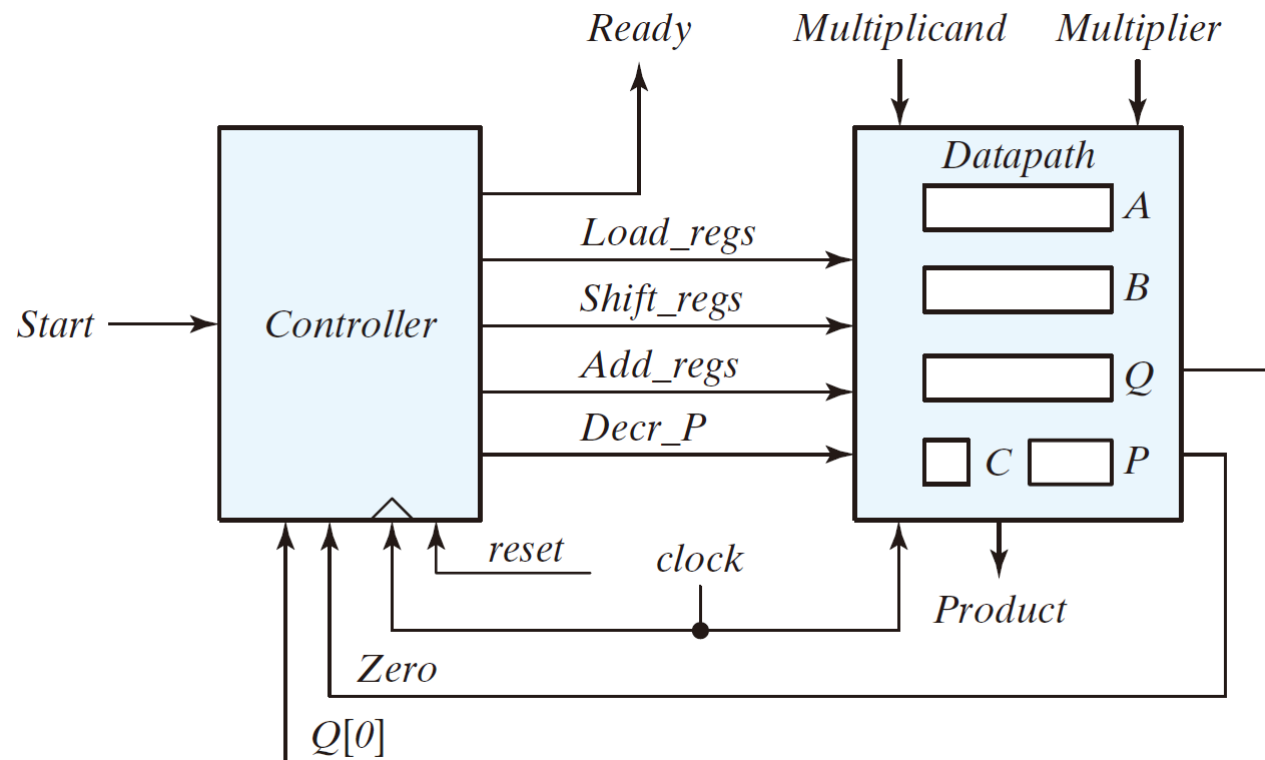
- ❑ The block diagram of the sequential multiplier:



Datapath of the Multiplier

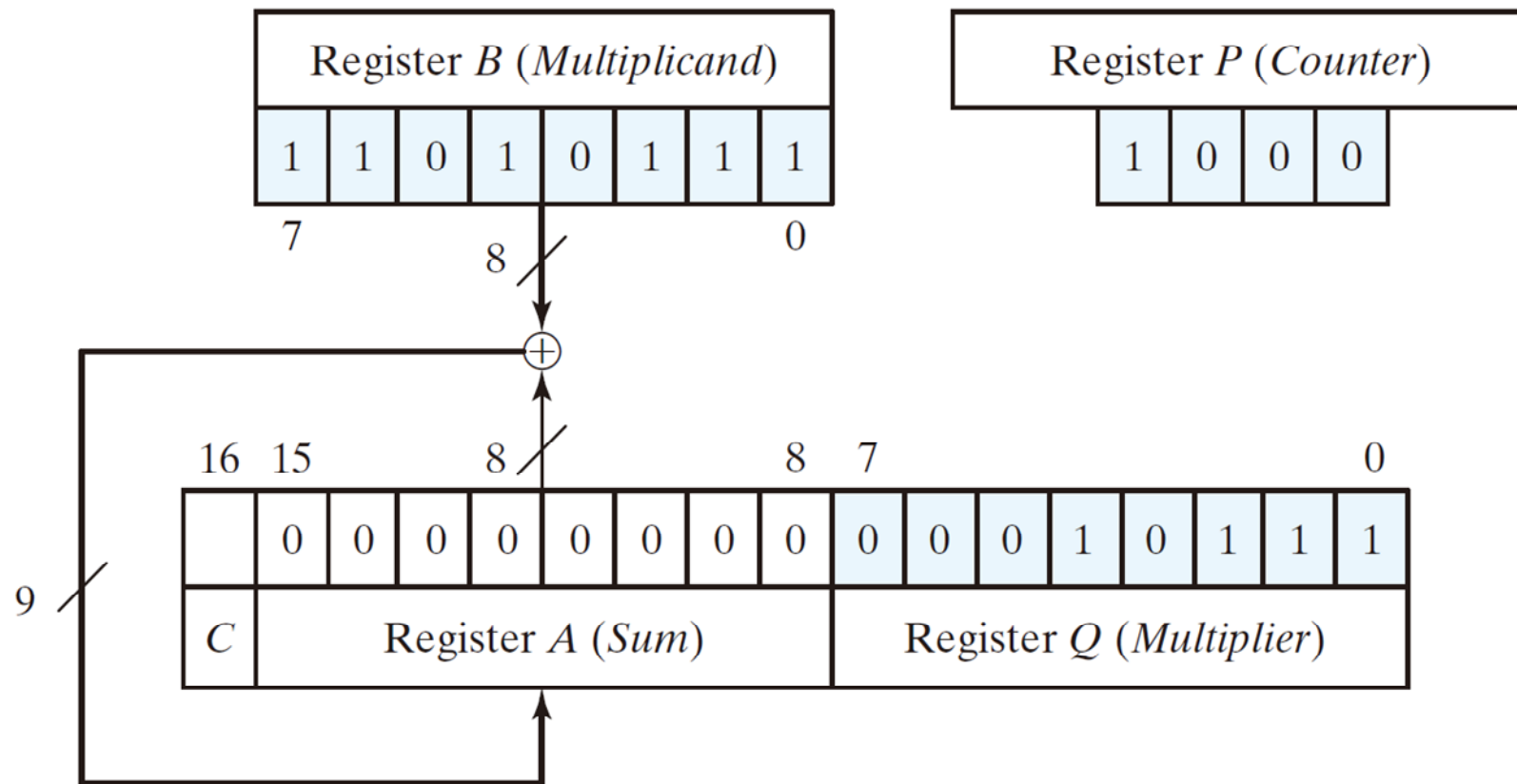

ASMD Chart of the Multiplier

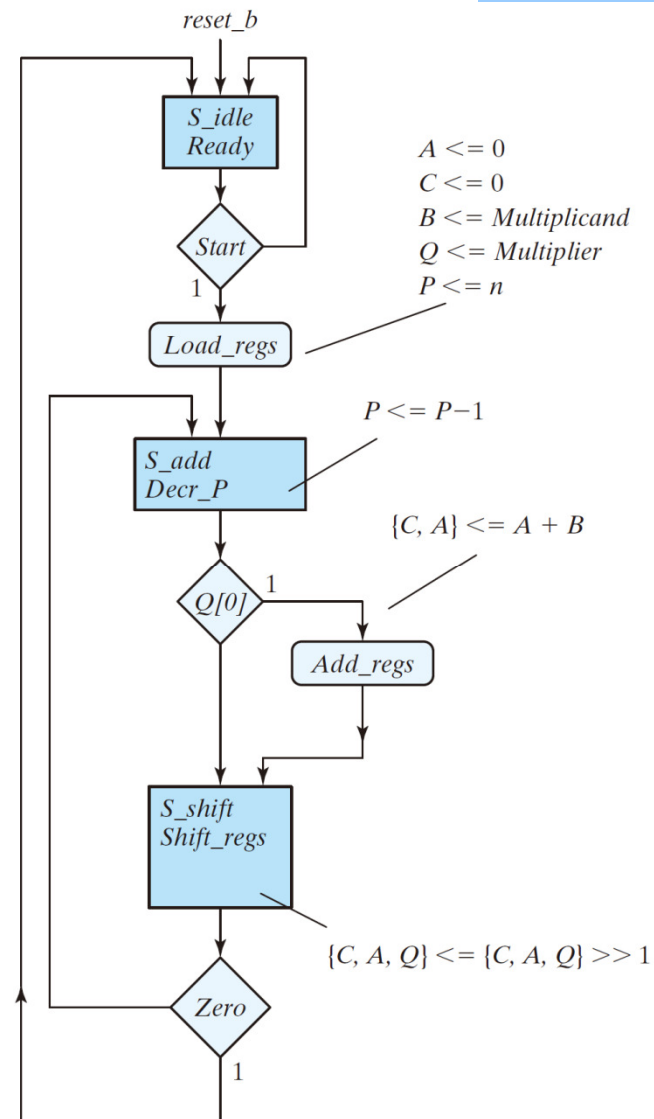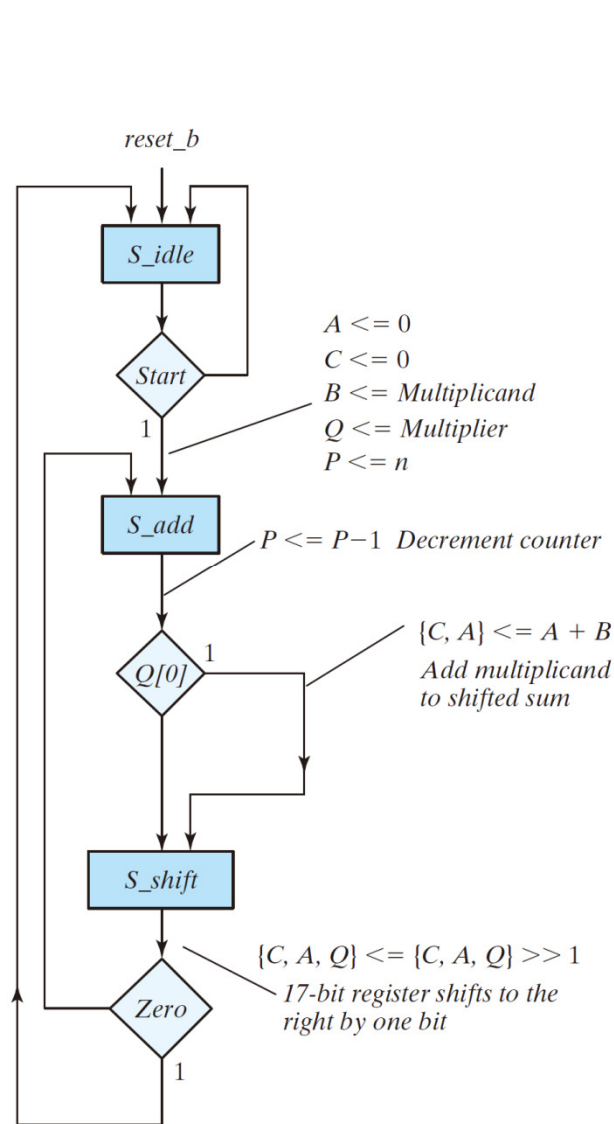

Register Notations for Shifting

- The shift operator \gg in the chart for concatenated registers $\{C, A, Q\}$ is equivalent to the following register transfer notation:

Shift right CAQ , $C \leftarrow 0$

- In terms of individual register symbols, the shift operation can be described by the following register operations:

$$\begin{aligned} A &\leftarrow \text{shr } A, A_{n-1} \leftarrow C \\ Q &\leftarrow \text{shr } Q, Q_{n-1} \leftarrow A_0 \\ C &\leftarrow 0 \end{aligned}$$

Example of Operations

- The registers change during a multiplication process:

Numerical Example For Binary Multiplier

Multiplicand $B = 10111_2 = 17_H = 23_{10}$

Multiplier $Q = 10011_2 = 13_H = 19_{10}$

Multiplier in Q

$Q_0 = 1$; add B

First partial product

Shift right CAQ

$Q_0 = 1$; add B

Second partial product

Shift right CAQ

$Q_0 = 0$; shift right CAQ

$Q_0 = 0$; shift right CAQ

$Q_0 = 1$; add B

Fifth partial product


Shift right CAQ

Final product in $AQ = 0110110101_2 = 1b5_H$

C	A	Q	P
0	00000	10011	101
	<u>10111</u>		
0	10111		100
0	01011	11001	
	<u>10111</u>		
1	00010		011
0	10001	01100	
0	01000	10110	010
0	00100	01011	001
	<u>10111</u>		
0	11011		
0	01101	10101	000

Multiplier Control Logic

 - The controller specification of the multiplier:



State Transition		Register Operations
<u>From</u>	<u>To</u>	
<i>S_idle</i>		Initial state
<i>S_idle</i>	<i>S_add</i>	$A \leq 0, C \leq 0, P \leq dp_width$
<i>S_add</i>	<i>S_shift</i>	$P \leq P - 1$ if ($Q[0]$) then ($A \leq A + B, C \leq C_{out}$)
<i>S_shift</i>		shift right {CAQ}, $C \leq 0$

State Assignment and State Table

- Possible state assignments for the multiplier:

State Assignment for Control

State	Binary	Gray Code	One-Hot
<i>S_idle</i>	00	00	001
<i>S_add</i>	01	01	010
<i>S_shift</i>	10	11	100

- State table (with binary states):

State Table for Control Circuit

Present-State Symbol	Present State		Inputs			Next State						
	<i>G₁</i>	<i>G₀</i>	<i>Start</i>	<i>Q[0]</i>	<i>Zero</i>	<i>G₁</i>	<i>G₀</i>	<i>Ready</i>	<i>Load_regs</i>	<i>Decr_P</i>	<i>Add_regs</i>	<i>Shift_regs</i>
<i>S_idle</i>	0	0	0	X	X	0	0	1	0	0	0	0
<i>S_idle</i>	0	0	1	X	X	0	1	1	1	0	0	0
<i>S_add</i>	0	1	X	0	X	1	0	0	0	1	0	0
<i>S_add</i>	0	1	X	1	X	1	0	0	0	1	1	0
<i>S_shift</i>	1	0	X	X	0	0	1	0	0	0	0	1
<i>S_shift</i>	1	0	X	X	1	0	0	0	0	0	0	1


State equations:

$$D_{G_1} = S_add$$

$$D_{G_0} = S_idle \cdot Start' + S_shift \cdot Zero'$$


Sequence Register and Decoder

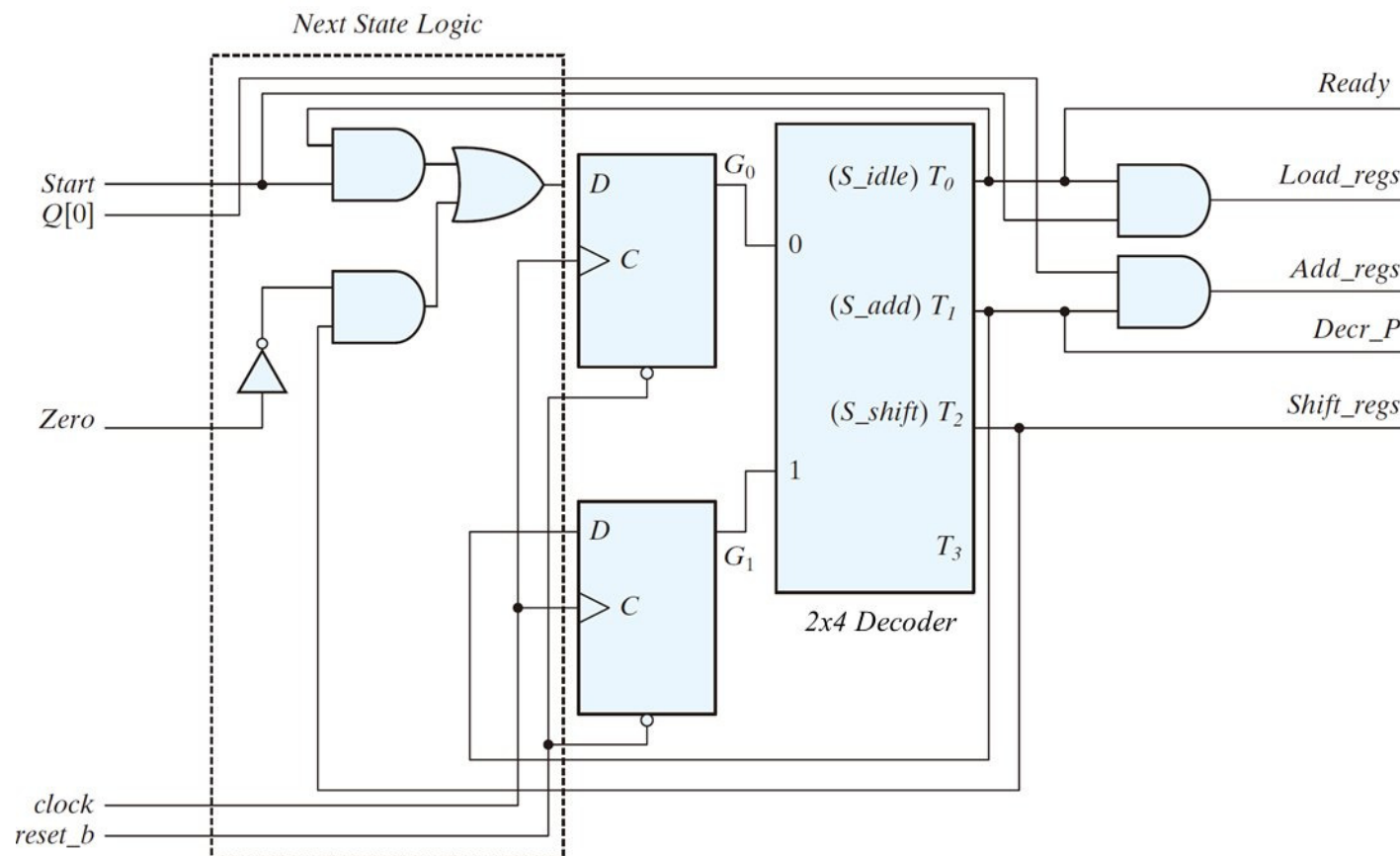- ❑ Logic diagram of binary multiplier controller using a sequence register and decoder



One-Hot Controller State

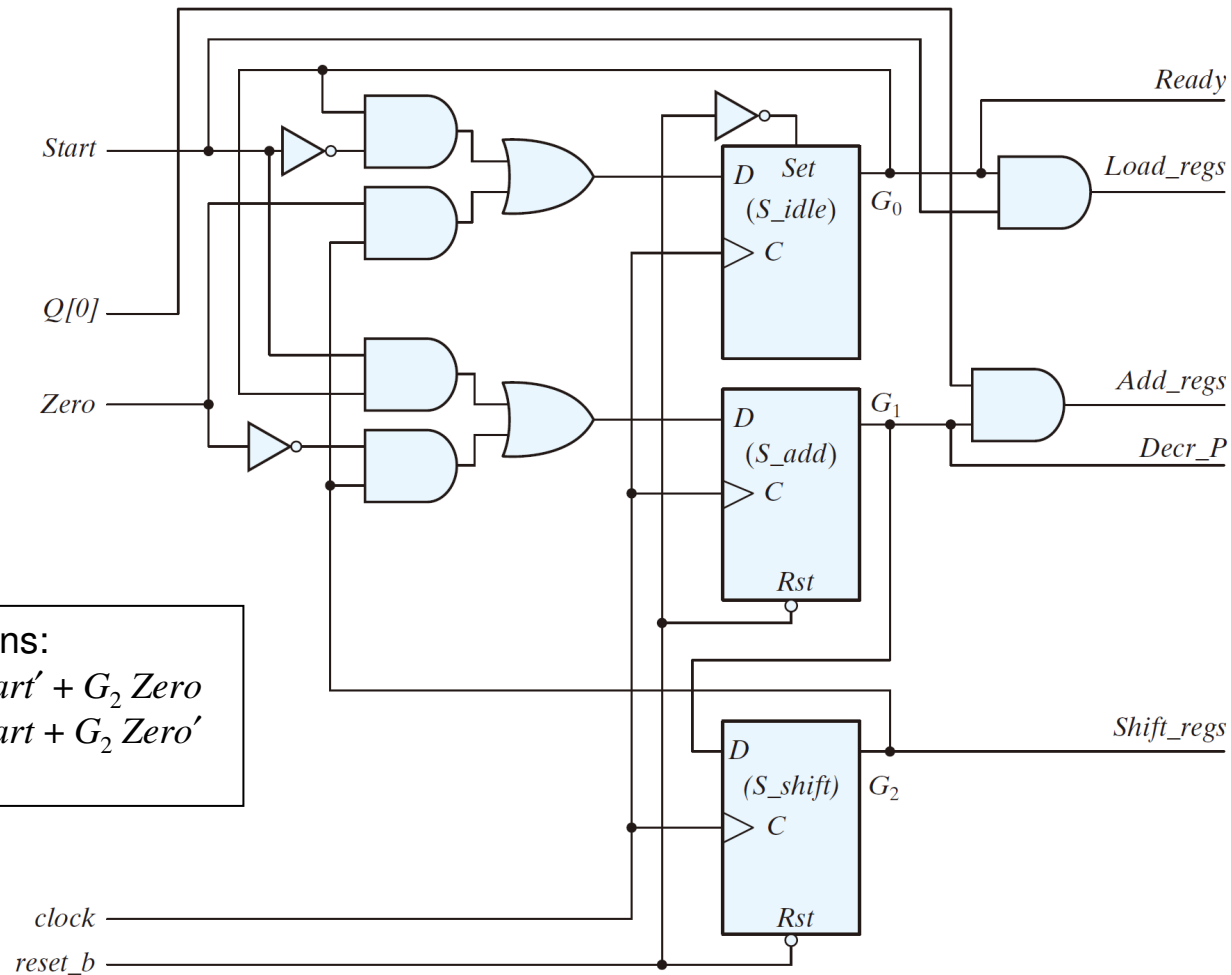- If one-hot state ID is used, the controller becomes:



State equations:


$$D_{G_0} = G_0 \text{ Start}' + G_2 \text{ Zero}$$

$$D_{G_1} = G_0 \text{ Start} + G_2 \text{ Zero}'$$

$$D_{G_2} = G_1$$


Design with Multiplexers

 - ❑ Replacing the gates with multiplexers results in a regular pattern of three levels of components.
 - Level 1: multiplexers that determine the next state.
 - Level 2: registers that hold the present binary state.
 - Level 3: a decoder that asserts a unique output line for each control state.
- ❑ Design example: 4 states, 4 control inputs



Control Implementation with MUX

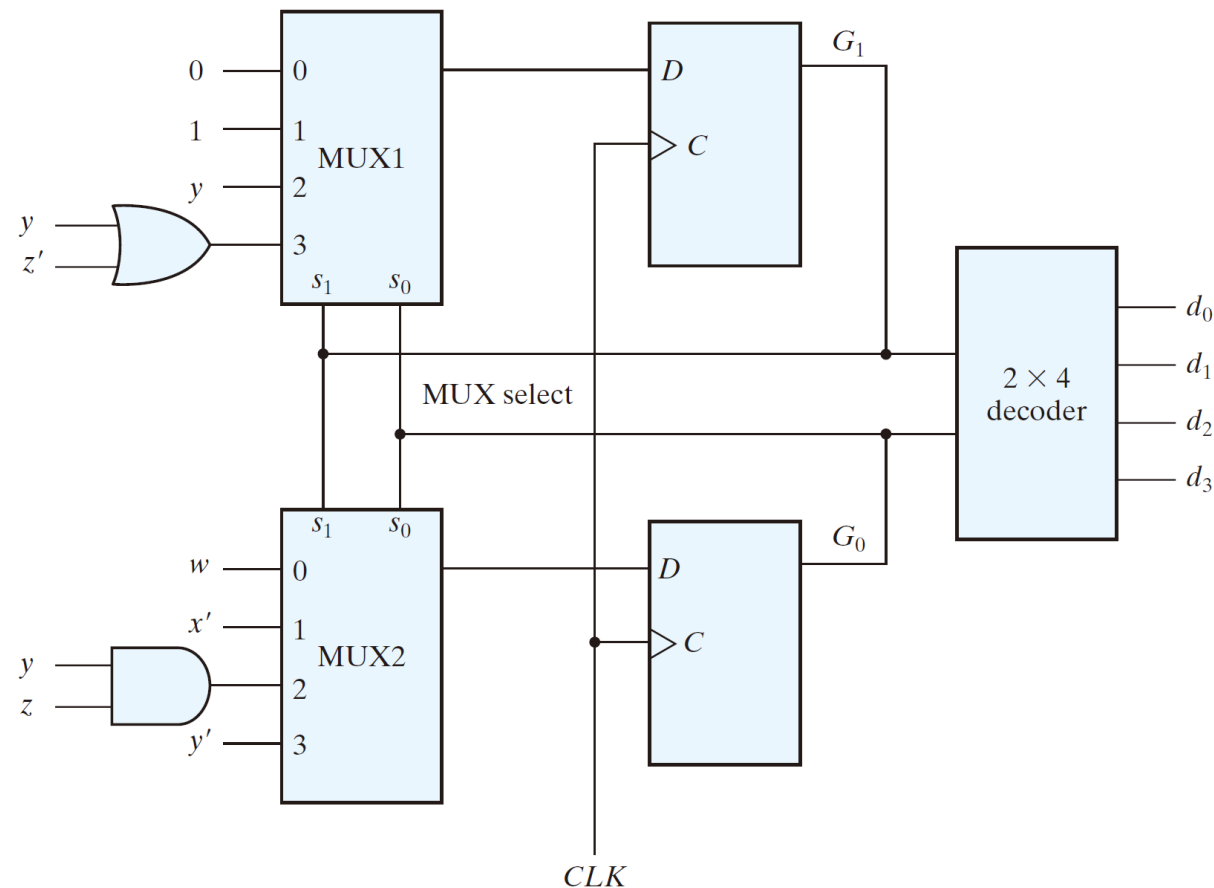- ❑ The multiplexers implement the state equations:
 - Current state selects the equations for next state.




State Table and MUX Inputs

Multiplexer Input Conditions


Present State		Next State		Input Condition	Inputs	
G_1	G_0	G_1	G_0	s	MUX1	MUX2
0	0	0	0	w'		
0	0	0	1	w	0	w
0	1	1	0	x		
0	1	1	1	x'	1	x'
1	0	0	0	y'		
1	0	1	0	yz'		
1	0	1	1	yz	$yz' + yz = y$	yz
1	1	0	1	$y'z$		
1	1	1	0	y		
1	1	1	1	$y'z'$	$y + y'z' = y + z'$	$y'z + y'z' = y'$

Design Example: 1's Counter

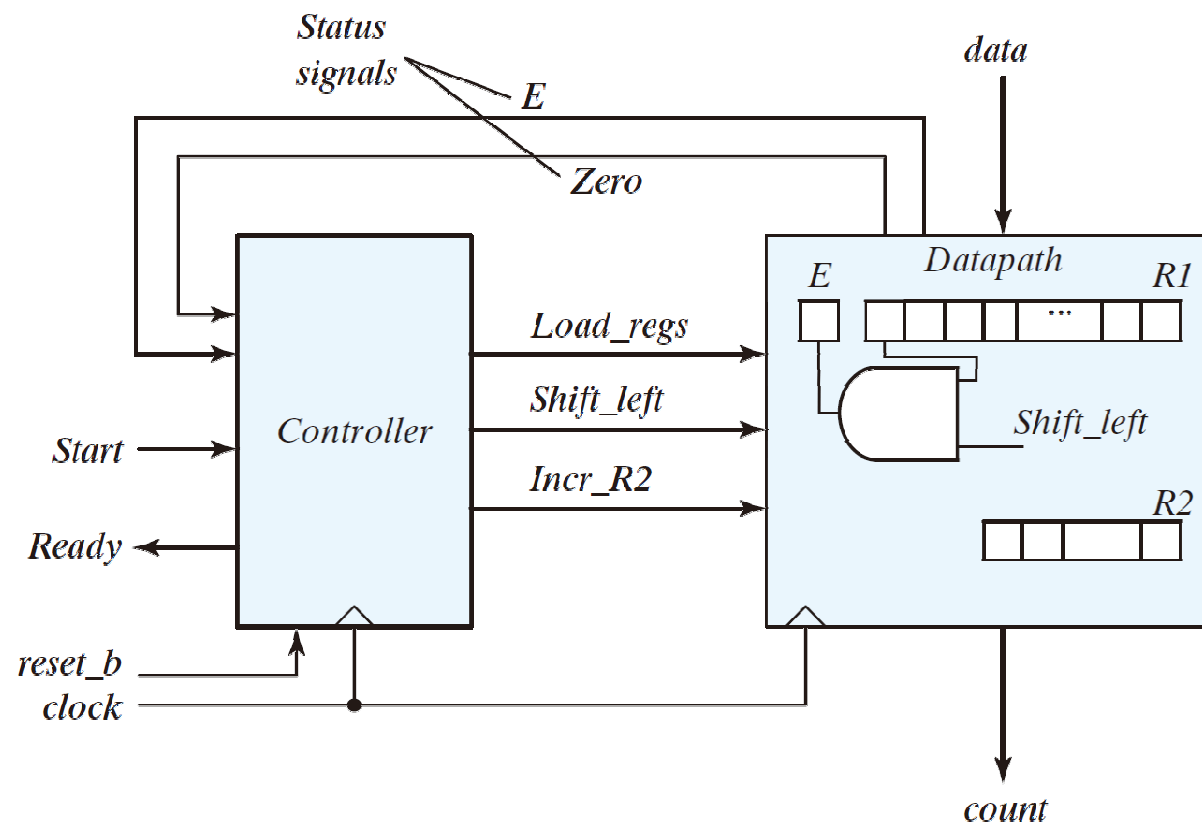- ❑ A system that counts the number of 1's in a word:



ASMD Chart of the 1's Counter

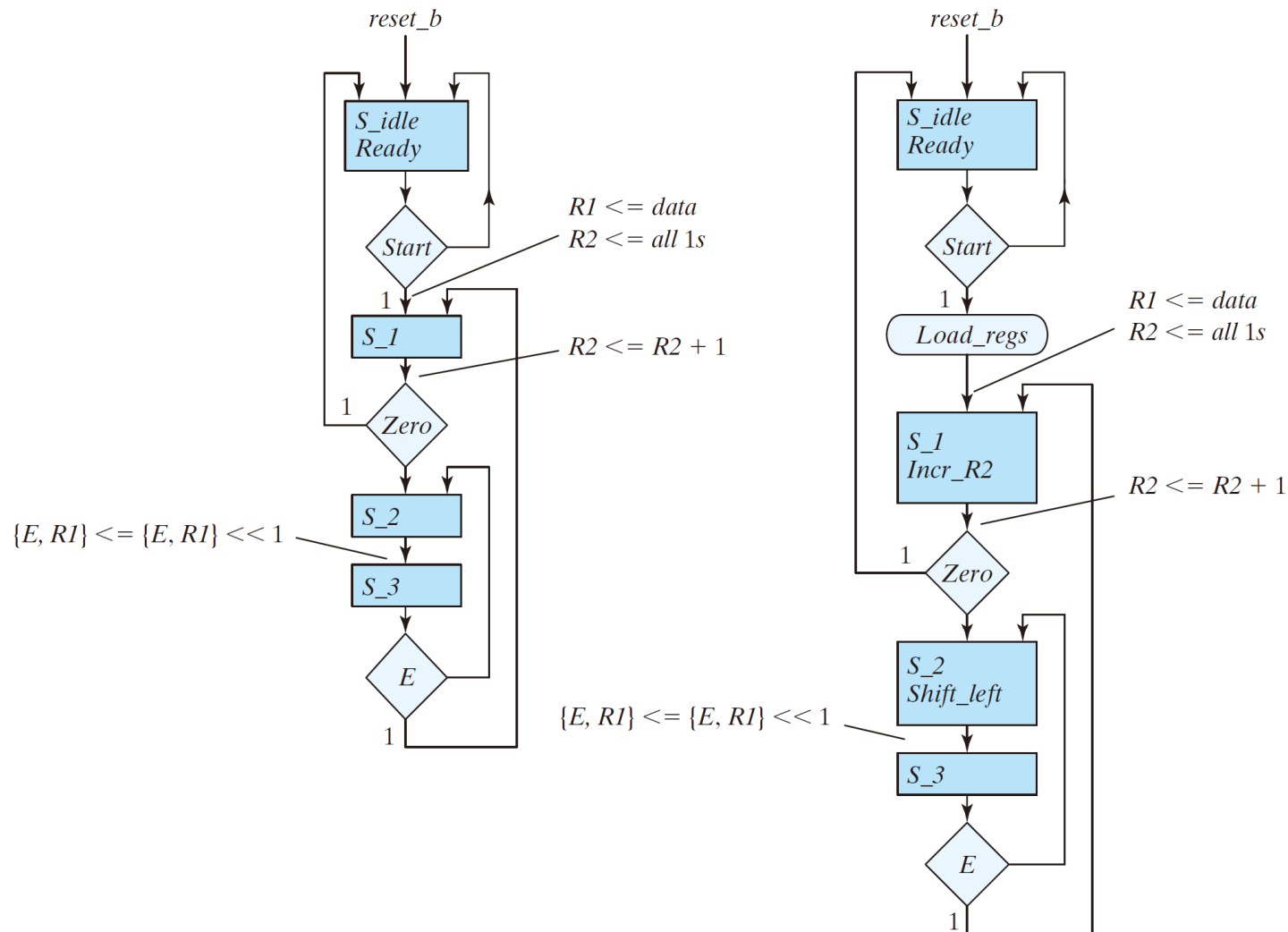


State Table of the 1's Counter

Multiplexer Input Conditions for Design Example

Present State		Next State		Input Conditions	Multiplexer Inputs	
G_1	G_0	G_1	G_0		MUX1	MUX2
0	0	0	0	<i>Start'</i>		
0	0	0	1	<i>Start</i>	0	<i>Start</i>
0	1	0	0	<i>Zero</i>		
0	1	1	0	<i>Zero'</i>	<i>Zero'</i>	0
1	0	1	1	<i>None</i>	1	1
1	1	1	0	<i>E'</i>		
1	1	0	1	<i>E</i>	<i>E'</i>	<i>E</i>


Controller of the 1's Counter Circuit

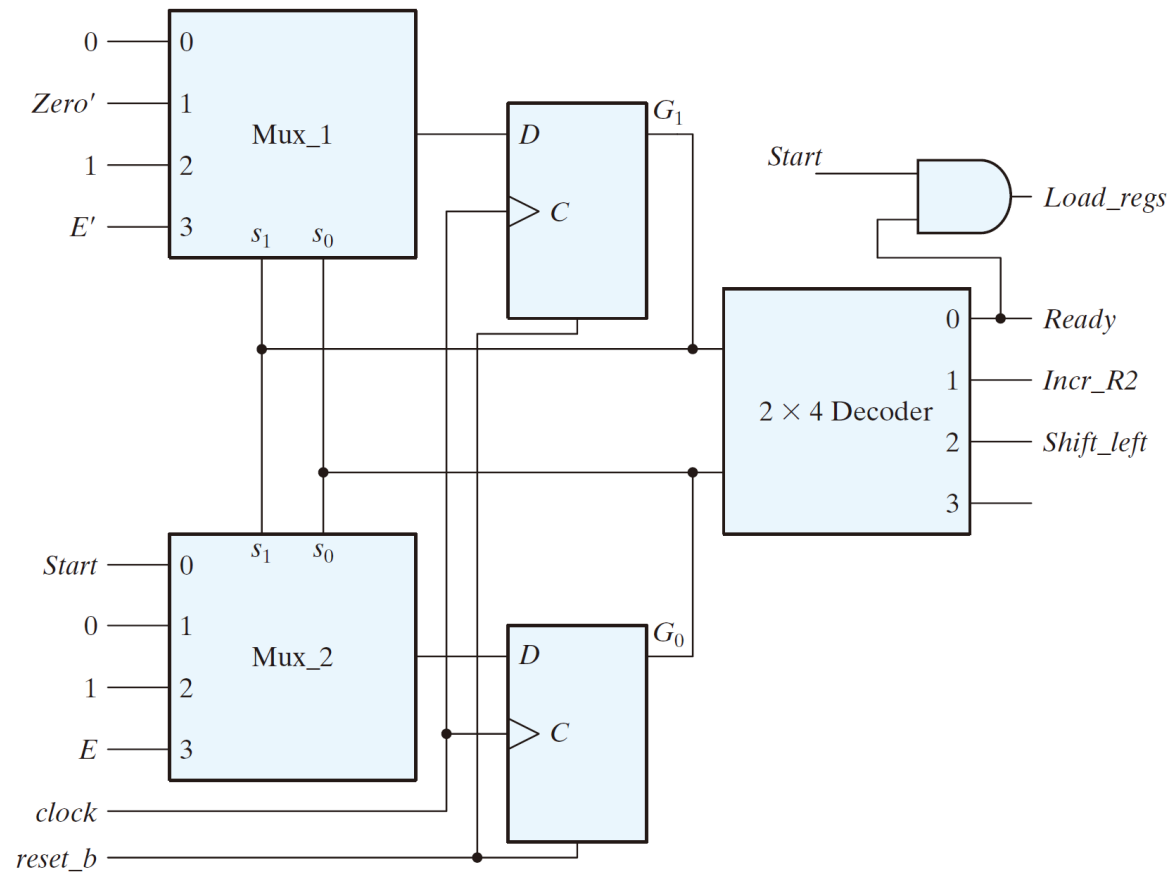

Race-Free Design

- ❑ Theoretically, any simulations of the behavior model of a circuit should match
 - In reality, software-based simulation may produce mismatch
- ❑ Potential cause of problem:
 - A physical feedback path exists between a datapath unit and control unit whose inputs include status signals fed back from the datapath unit.
 - Blocked propagation assignments execute immediately, and behavioral models simulate with 0 propagation delays, effectively creating immediate changes in the outputs of the combinational logic when its inputs change.
 - The order in which a simulator executes multiple blocked assignments to the same variable at a given time step of the simulation is indeterminate.

Waveform Simulation of 1's Counter

 

Latch-Free Design

- ❑ A feedback-free continuous assignment will synthesize to combinational logic, and the input-output relationship of the logic is automatically sensitive to all of the inputs of the circuit.
- ❑ If a level-sensitive cyclic behavior is used to describe combinational logic, it is essential that the sensitivity list include every variable; if the list is incomplete, the logic described by the behavior will be synthesized with latches at the output logic.