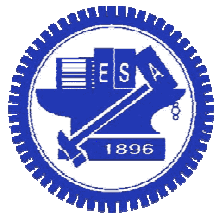


Registers and Counters




Chun-Jen Tsai
National Chiao Tung University
11/26/12

Registers


- ❑ We use single-bit flip-flops as the elementary memory device in a sequential circuit
- ❑ In practice, we need multiple bits for data storage in sequential circuits, such devices are called registers
 - A n-bit register can be constructed using an array of flip-flops or a special-purpose high-speed multi-bit memory device
 - A counter is a special-purpose register that goes through a predetermined sequence of states
- ❑ A collection of registers used in a sequential circuit is often called a “register file”

Flip-flop Implementation of Registers

 - ❑ An n -bit register
 - n flip-flops capable of storing n bits of binary information
 - Example: a 4-bit register
- ❑ Problem: what if we do not want to change the state every clock cycle?



A 4-bit Register with Parallel Load

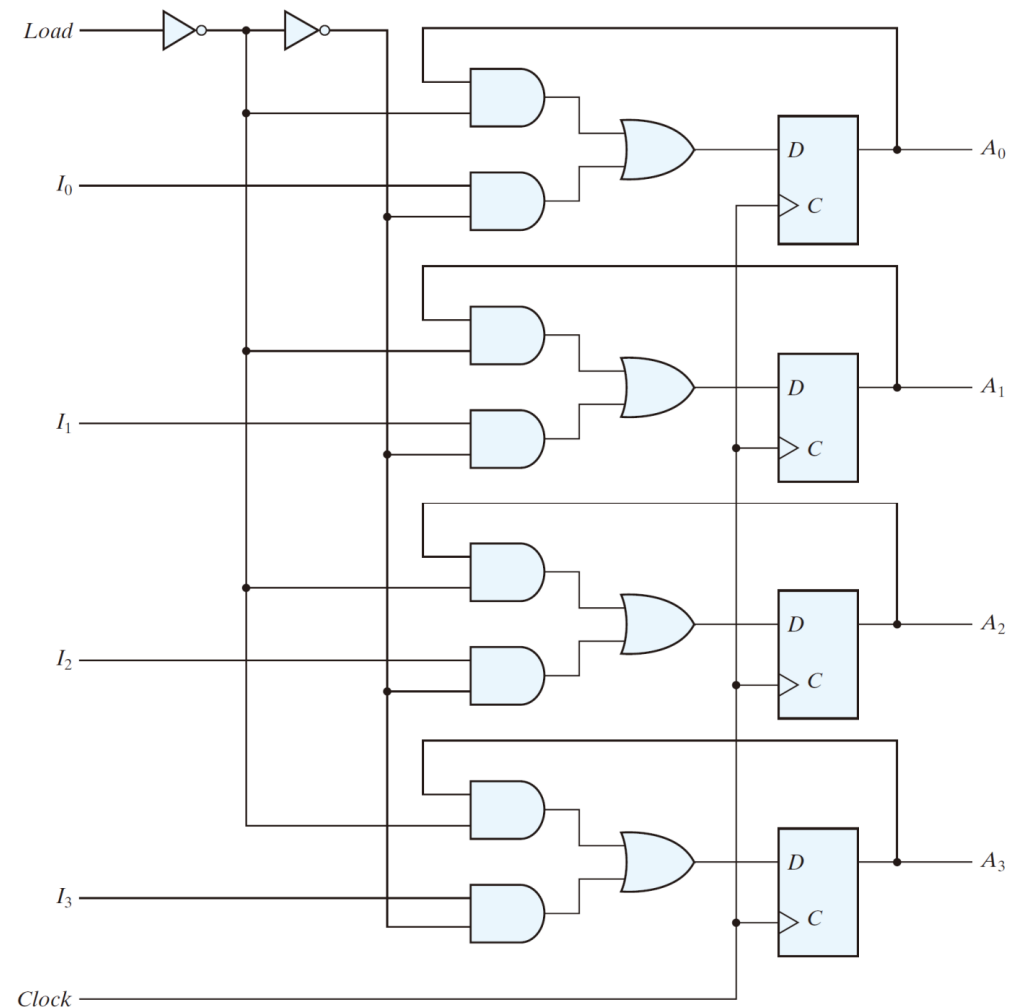


Shift Registers

❑ Shift register

- a register capable of shifting its binary information in one or both directions

❑ Example: 4-bit shift register


- What is it good for?

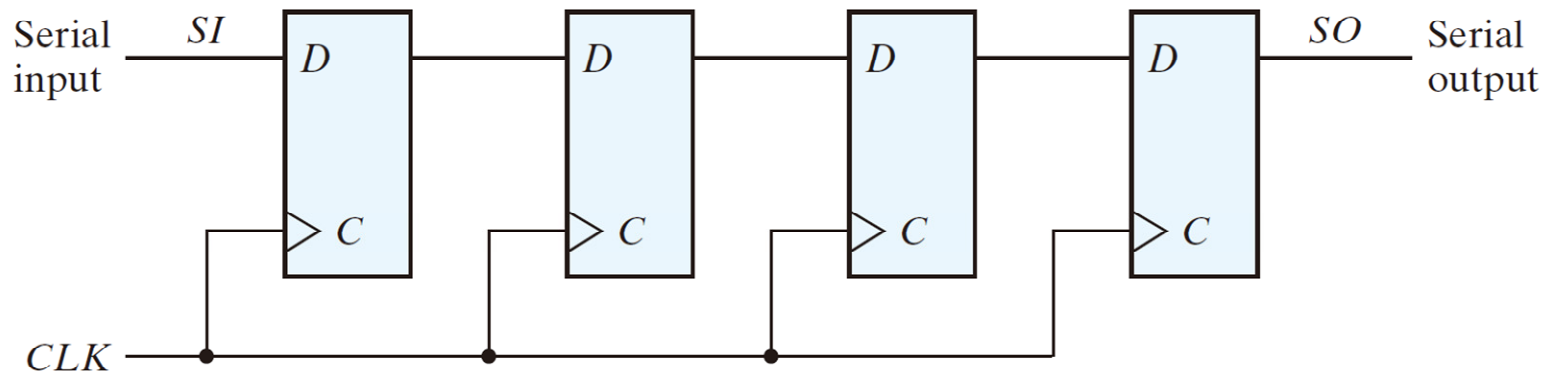


Data Transfer between Registers

- ❑ There are two type of data transfer from register to register:
- ❑ Serial transfer:
 - Information is transferred one bit at a time
 - shifts the bits out of the source register into the destination register
- ❑ Parallel transfer:
 - All the bits of the register are transferred at the same time

Serial Transfer from reg A to reg B

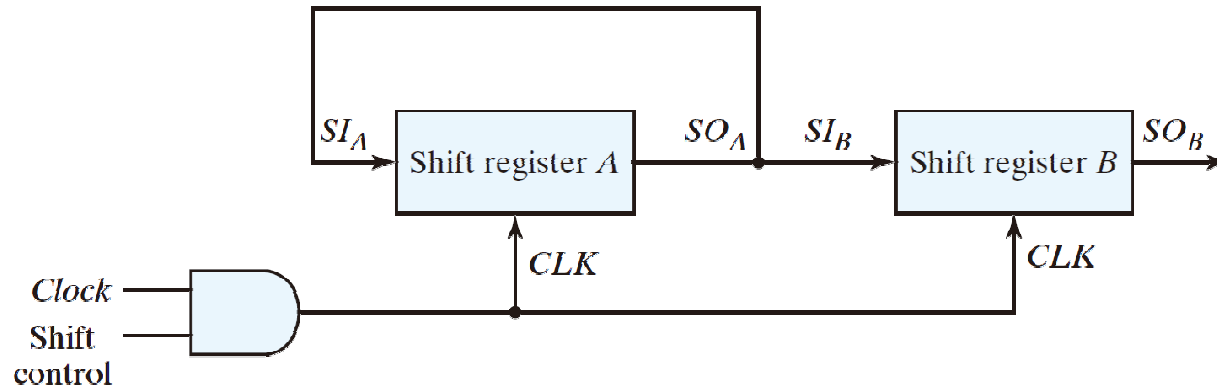


(a) Block diagram

 

(b) Timing diagram

Clock	Shift Reg A				Shift Reg B			
Initial value	1	0	1	1	0	0	1	0
After T_1	1	1	0	1	1	0	0	1
After T_2	1	1	1	0	1	1	0	0
After T_3	0	1	1	1	0	1	1	0
After T_4	1	0	1	1	1	0	1	1

Serial Addition using D Flip-Flops

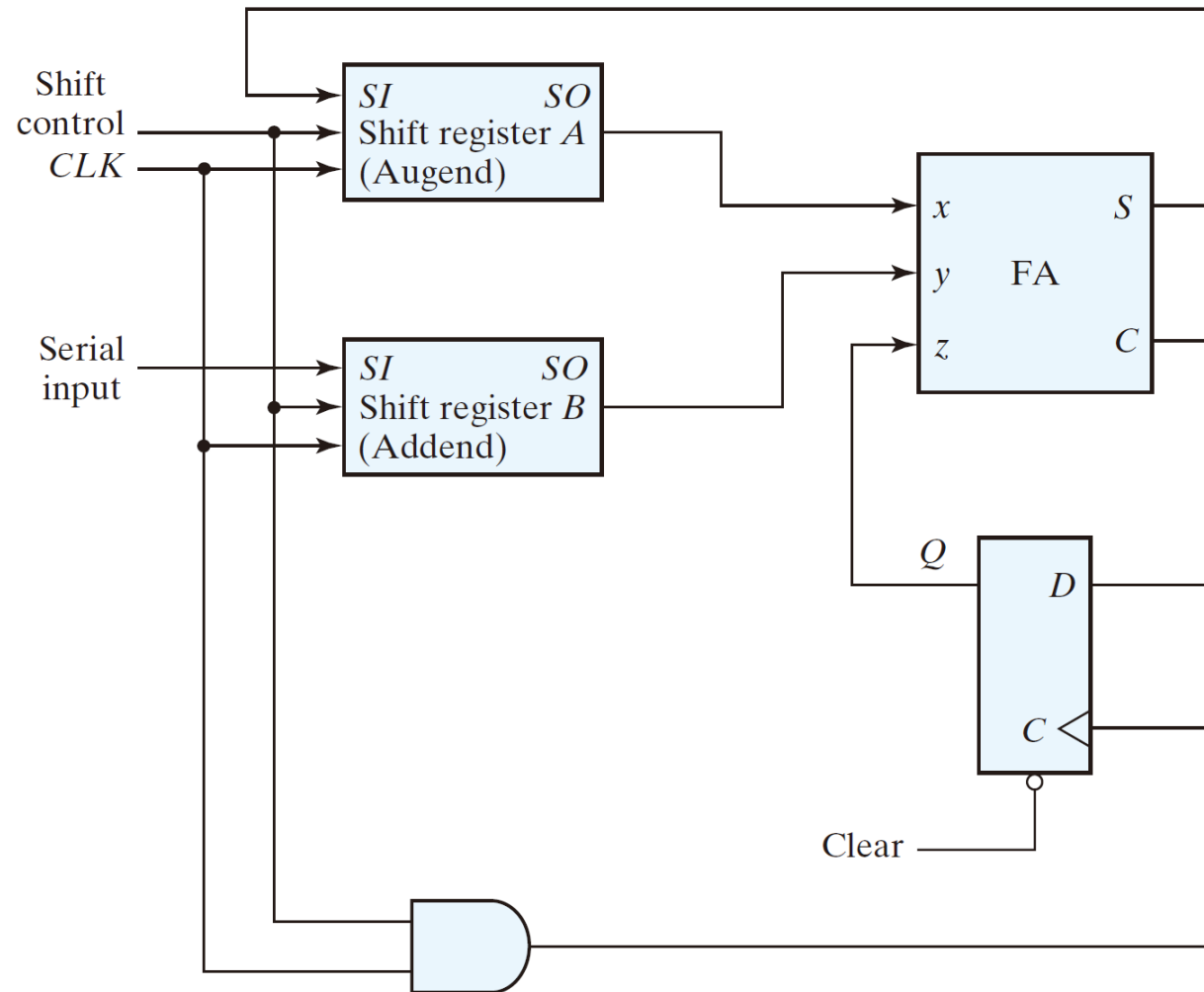

Serial Adder using JK Flip-Flops (1/2)

□ State Table:


Present State	Inputs		Next State	Output	Flip-Flop Inputs	
Q	x	y	Q	S	J_Q	K_Q
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0

□ State functions:

- $J_Q = x y$
- $K_Q = x' y' = (x + y)'$
- $S = x \oplus y \oplus Q$

Serial Adder using JK Flip-Flops (2/2)


❑ Logic Diagram:

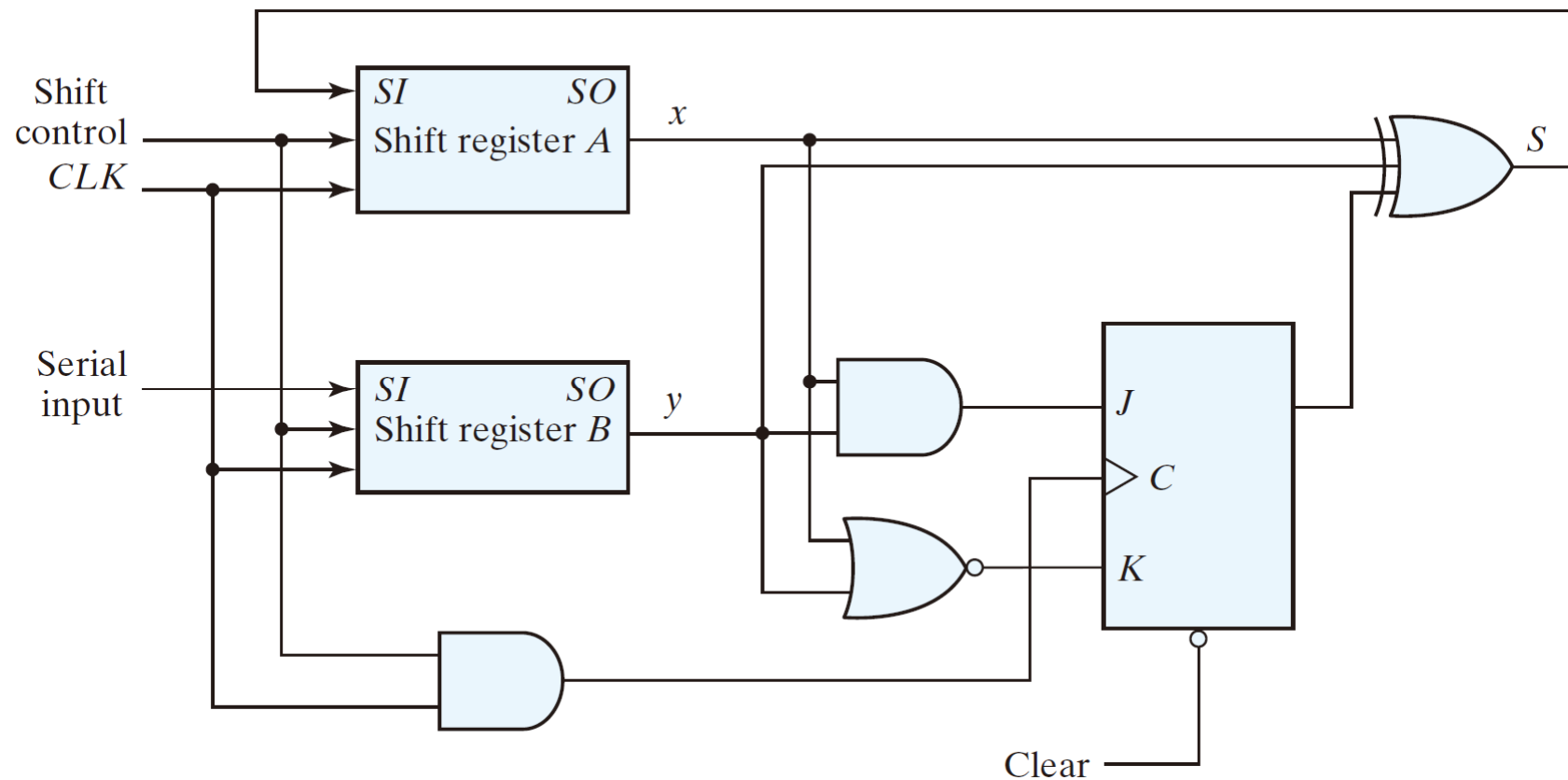

Universal Shift Register


- ❑ A universal shift register is a bi-directional shift register with parallel load/out capabilities
- ❑ I/O ports of a universal shift register
 - A “clear” input to clear the register to 0.
 - A “clock” input to synchronize the operations.
 - A “control” input to enable/disable the shift right/left, or n -bit parallel load operations.
 - n parallel output lines.

Example: 4-bit Universal Shift-Reg.

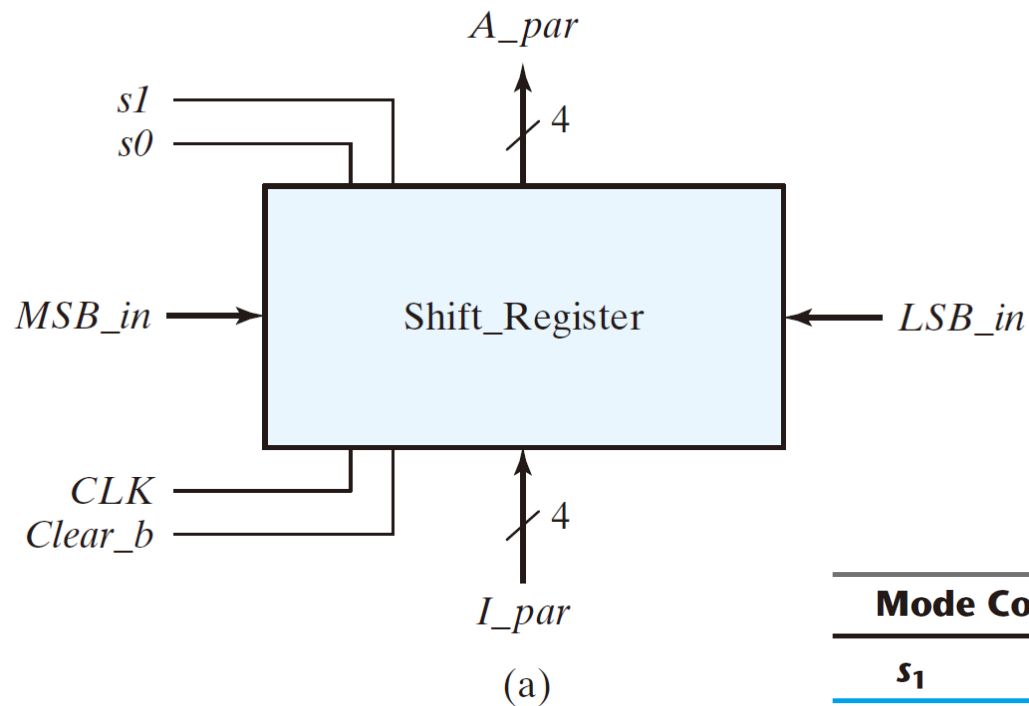

Mode Control		
s_1	s_0	Register Operation
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

Logic Diagram

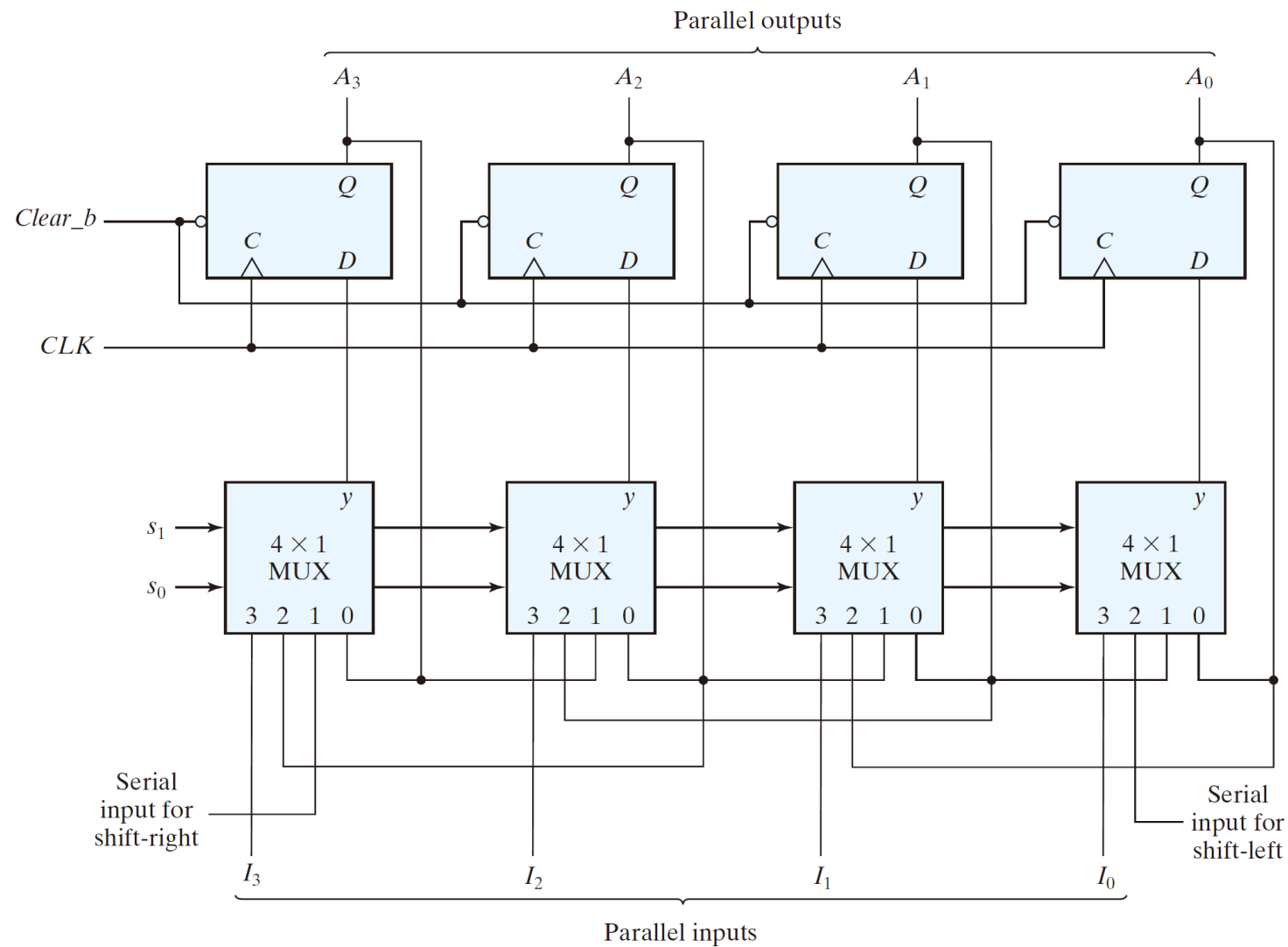

(b)

Ripple Counter

- ❑ A counter is a register that goes through a prescribed sequence of states upon the application of input pulses.
- ❑ The input pulses may be a clock pulses or a signal originating from some external source.
- ❑ The sequence of states may follow the binary number sequence (e.g. a binary counter) or any other sequence of states.

Categories of Counters

❑ Ripple counters:

- The flip-flop output transition serves as a source for triggering other flip-flops
- No common clock pulse (asynchronous)

❑ Synchronous counters:



- The clock input (CLK) of all flip-flops receive a common clock

Example: Binary Ripple Counter

- ❑ A binary ripple counter can be done easily with T or D flip-flops:



Binary Count Sequence

A_3	A_2	A_1	A_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

  

  
Example: BCD Counter

- The state and logic diagram of a decimal BCD counter:



Multi-digit Decimal BCD Counter

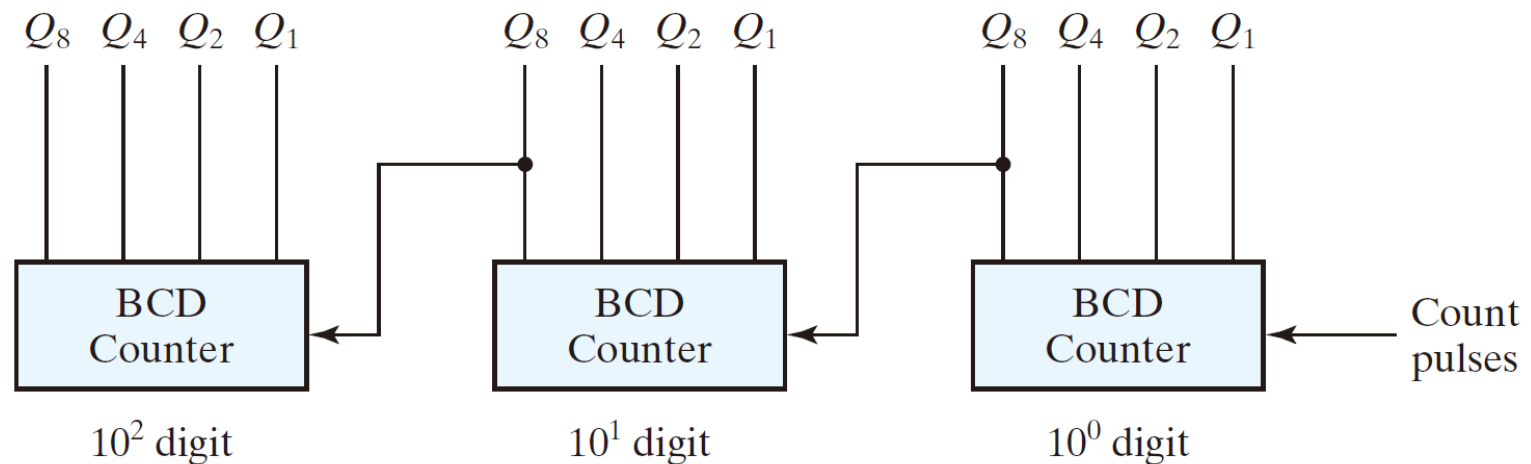- ❑ BCD counter can be chained together to form a multi-digit BCD counter




Sync. Counters

- ❑ A synchronous counter uses a common clock triggers all flip-flops simultaneously


- ❑ Note that:

 - $En_1 = En_0 A_0$
- $En_2 = En_0 A_0 A_1$
- $En_3 = En_0 A_0 A_1 A_2$



Up/Down Binary Counters

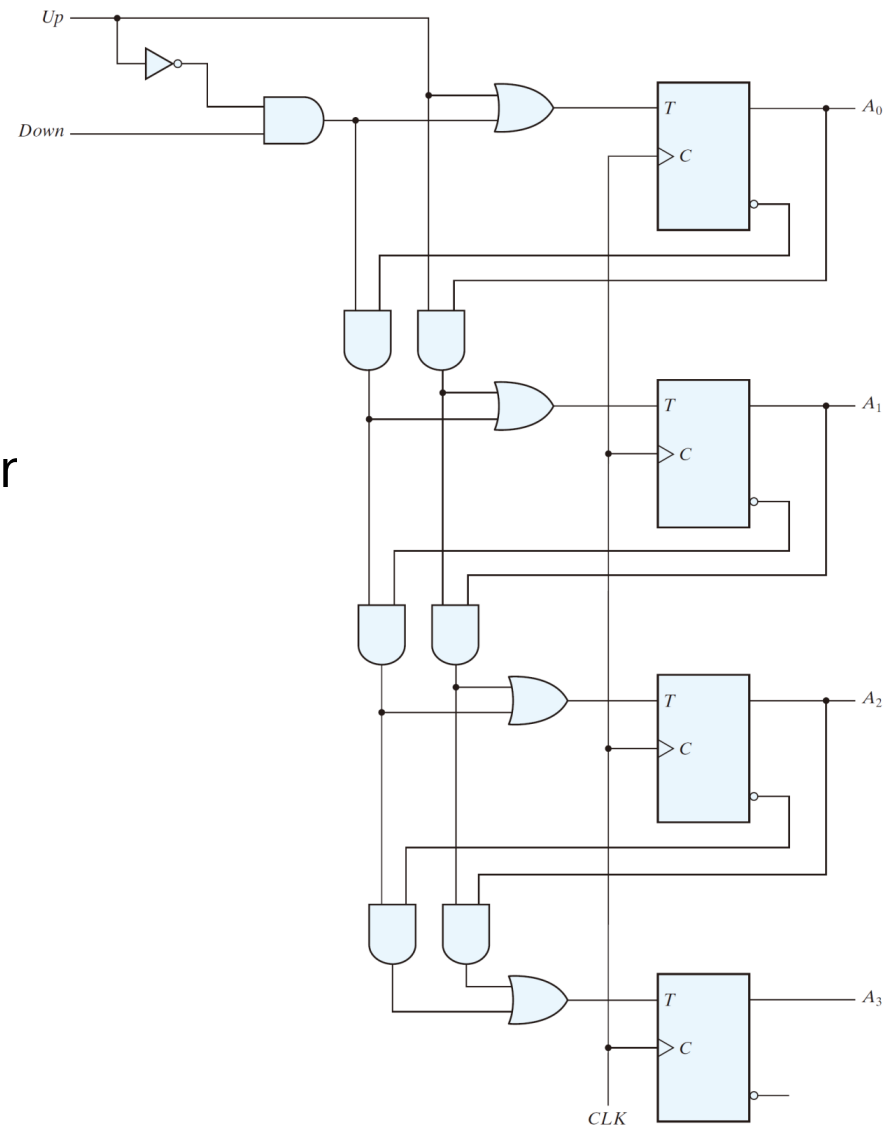- ❑ A up/down counters can perform counting in both directions
- ❑ Counting control:
 - $U/D = 1/0 \rightarrow$ counts up
 - $U/D = 0/1 \rightarrow$ counts down
 - $U/D = 0/0 \rightarrow$ pause
 - $U/D = 1/1 \rightarrow$ counts up



BCD Counters

- A BCD counter counts from 0 → 9, repeatedly

Present State				Next State				Output	Flip-Flop Inputs			
Q_8	Q_4	Q_2	Q_1	Q_8	Q_4	Q_2	Q_1	y	TQ_8	TQ_4	TQ_2	TQ_1
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	→ 0	0	0	0	1	1	0	0	1

- Simplified input functions for T flip-flops:

$$T_{Q1} = 1$$

$$T_{Q2} = Q'_8 Q_1$$

$$T_{Q4} = Q_2 Q_1$$

$$T_{Q8} = Q_8 Q_1 + Q_4 Q_2 Q_1$$


$$y = Q_8 Q_1$$

Binary Counter w/ Parallel Load (1/2)

- ❑ Counters often requires initialization before counting
- ❑ The function table for a counter with parallel load:


Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

- ❑ I/O ports

 



Binary Counter w/ Parallel Load (2/2)

Logic diagram:

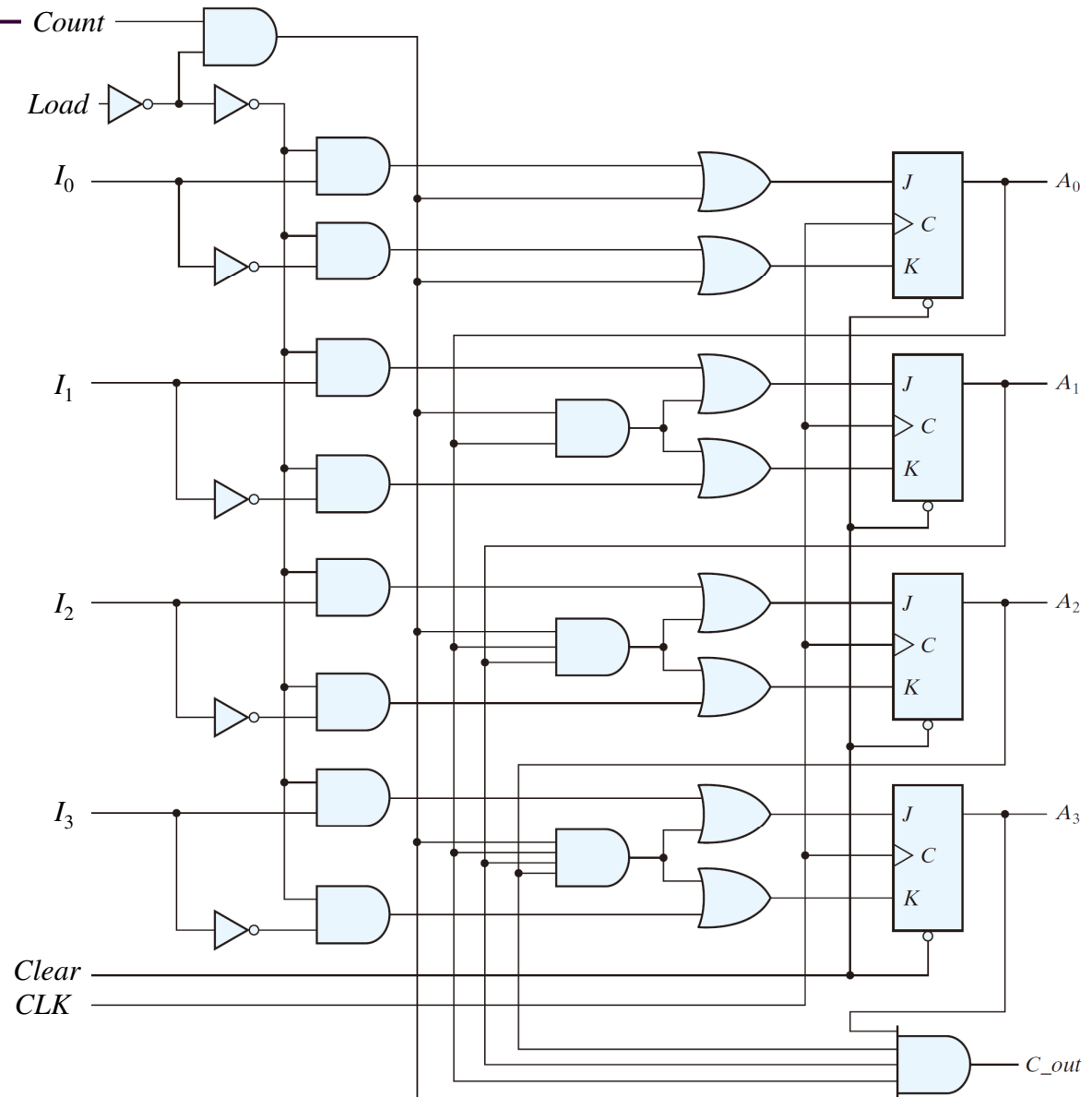

Count Sequence Control

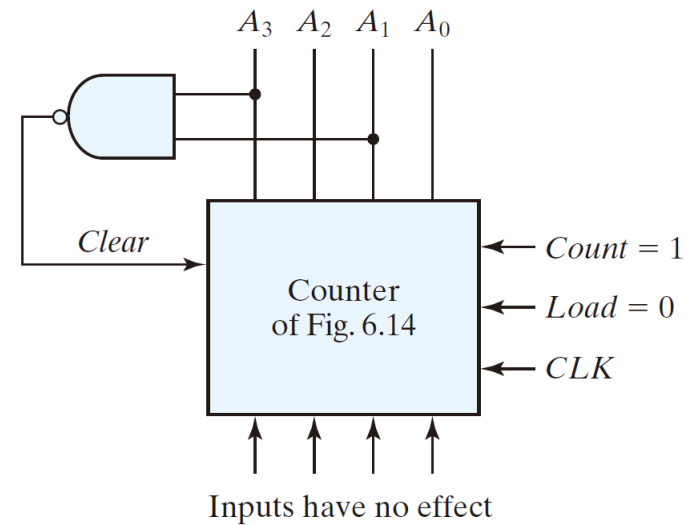 - ❑ A counter with parallel load can be used to perform counting for different count sequence
- ❑ Example: two ways to emulate BCD sequences:



Comments on Counter Design

- ❑ A counter can be designed to generate any desired sequence of states
 - Example: a divide-by- N counter (modulo- N counter) goes through a repeated sequence of N states; the sequence may follow the binary count or may be any arbitrary sequence
- ❑ Handling unused states
 - A counter composed of n flip-flops can represent 2^n states
 - Not all states are used; unused states may be treated as
 - Assigned specific next states → circuit behavior is deterministic
 - Don't-care conditions → circuit behavior should not have a trap!

Self-Correcting Counter (1/2)

- ❑ A self-correcting counter ensures that when it enters one of its unused states, it eventually goes into one of the valid states after one or more clock pulses
- ❑ Example: a counter with 2 unused states – 011 & 111

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J _A	K _A	J _B	K _B	J _C	K _C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X



set X to '1' for simplification!

Self-Correcting Counter (2/2)

□ The flip-flop input equations:

- $J_A = B, K_A = B$
- $J_B = C, K_B = 1$
- $J_C = B', K_C = 1$


□ The state and logic diagrams:

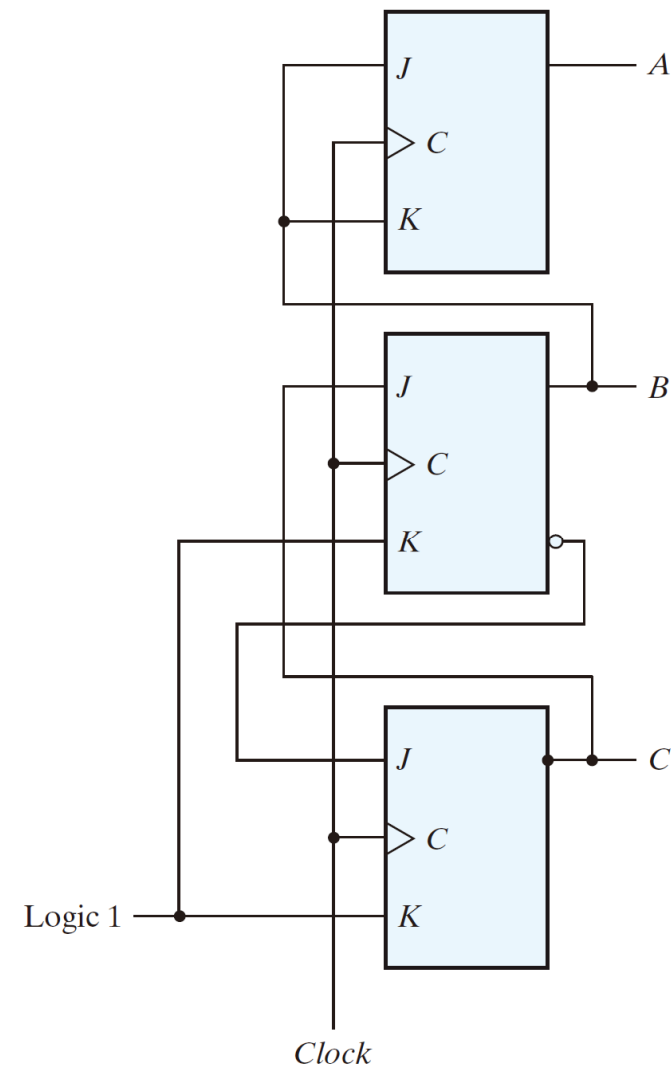 

Ring Counter

- ❑ A ring counter is a circular shift register with only one flip-flop being set at any particular time, all others are cleared (initial value = 1 0 0 ... 0)
- ❑ The single bit is shifted from one flip-flop to the next to produce the sequence of timing signals
- ❑ Example: 4-bit ring counter



A_3	A_2	A_1	A_0
1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1
1	0	0	0

 

  (a) Ring-counter (initial value = 1000)


Application of Ring Counters (1/2)

- ❑ Ring counters may be used to generate timing signals to control the sequence of operations in a digital system
- ❑ Approaches for generation of 2^n timing signals
 1. a shift register with 2^n flip-flops
 2. an n -bit binary counter together with an n -to- 2^n -line decoder




Application of Ring Counters (2/2)

- The resulting timing signals:

 

Switch-tail Ring Counter

 - ❑ A k -bit ring counter circulates a single bit among the flip-flops to provide k distinguishable states.
- ❑ A switch-tail ring counter use a circular shift register to provide twice the states of normal a ring counter
 - a k -bit switch-tail ring counter will go through a sequence of $2k$ distinguishable states (initial value = 0 0 ... 0).



Johnson Counters (1/2)

- ❑ A Johnson counter is a k -bit switch-tail ring counter plus $2k$ decoding gates
 - Each decoding gate has 2 inputs.
 - It provides $2k$ timing signals; only one is enabled at a time.
- ❑ Example: a 4-bit Johnson counter

Sequence number	Flip-flop outputs				Decoding Logic ($2k$ gates total)
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	AB'
3	1	1	0	0	BC'
4	1	1	1	0	CE'
5	1	1	1	1	AE
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

Count sequence and required decoding

Johnson Counters (2/2)

- ❑ If a Johnson counter enters an unused state, it will persist to circulate in the invalid states and never find its way back to a valid state.
 - The invalid states happens when three consecutive flip-flops have the value 0–1–0 or 1–0–1, a possible correcting scheme is to force the state of the third flip-flop to reset to 0 by the correction logic: $D_C = (A + C) B$
- ❑ Johnson counters can provide k timing sequences using only $k/2$ flip-flops and k decoding gates.