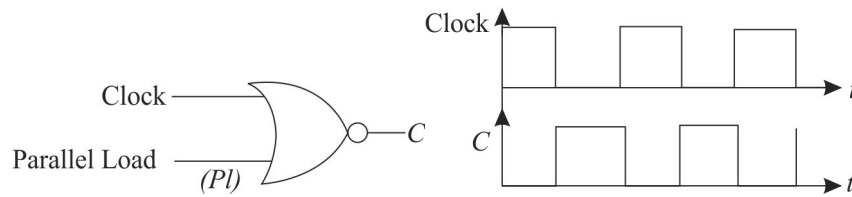



6.1




$$C = (\text{clock} + PL)'$$

When $PL = 0$, $C = (\text{clock})'$. Hence complete circuit diagram act as negative edge triggered, even though the flip-flops are positive edge triggered.
When, $PL = 1$, $C = 0$. Hence no change in output A.


6.6 First stage of register:

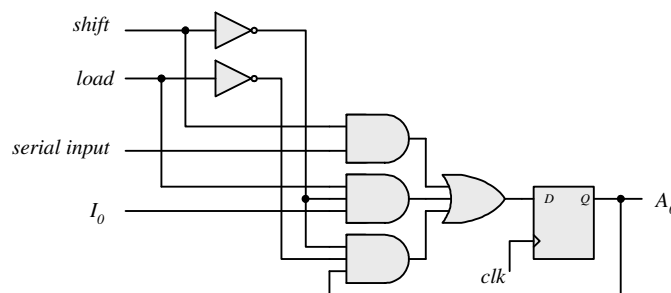


6.7 First stage of register:

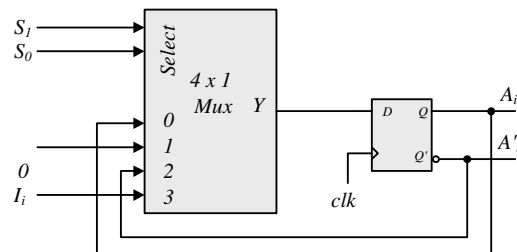

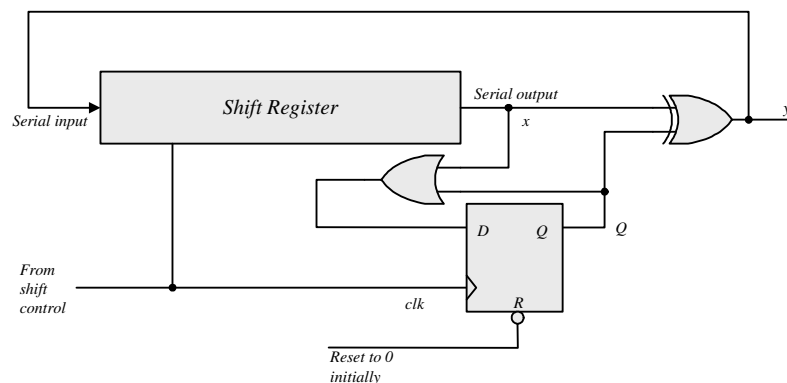6.10 Note that $y = x$ if $Q = 0$, and $y = x'$ if $Q = 1$. Q is set on the first 1 from x .
Note that $x \oplus 0 = x$, and $x \oplus 1 = x'$.




6.13

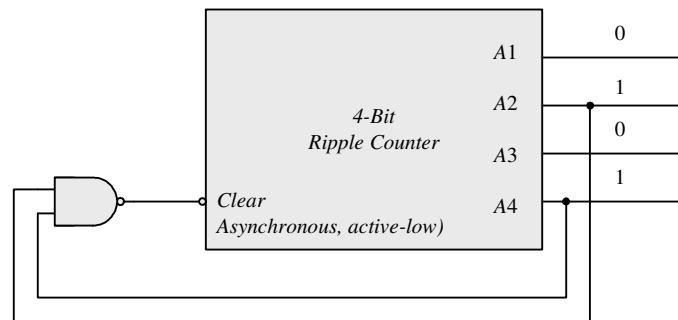



6.17

Present State	Next State		
Q_A Q_B Q_C	Q_A Q_B Q_C	D_A D_B D_C	
0 0 0	0 0 1	0 0 1	$D_A = \Sigma(3, 4, 5, 6)$
0 0 1	0 1 0	0 1 0	$D_B = \Sigma(1, 2, 5, 6)$
0 1 0	0 1 1	0 1 1	$D_C = \Sigma(0, 2, 4, 6)$
0 1 1	1 0 0	1 0 0	$D_A = Q_A \oplus Q_B \oplus Q_C$
1 0 0	1 0 1	1 0 1	$D_B = Q_B \oplus Q_C$
1 0 1	1 1 0	1 1 0	$D_C = Q'_C$
1 1 0	1 1 1	1 1 1	
1 1 1	0 0 0	0 0 0	

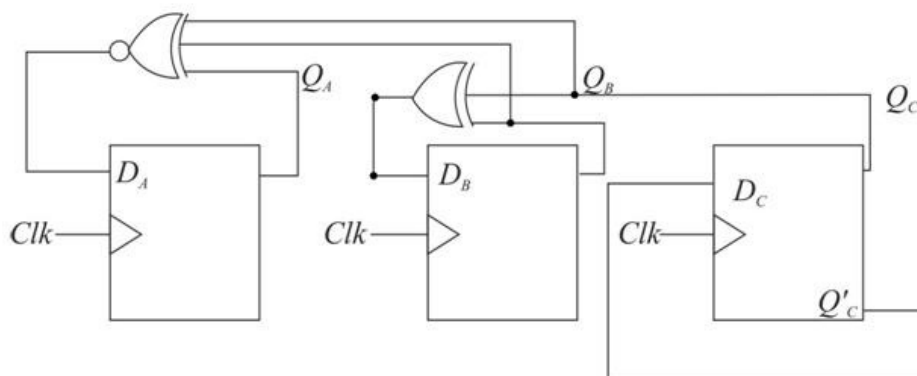

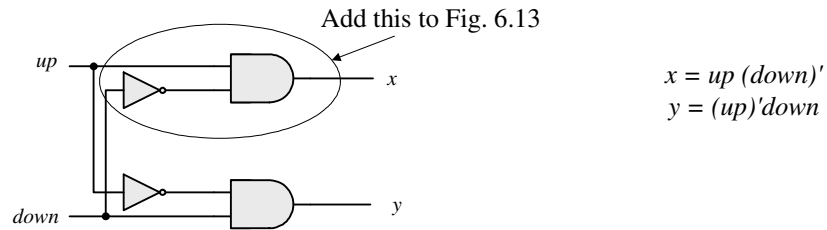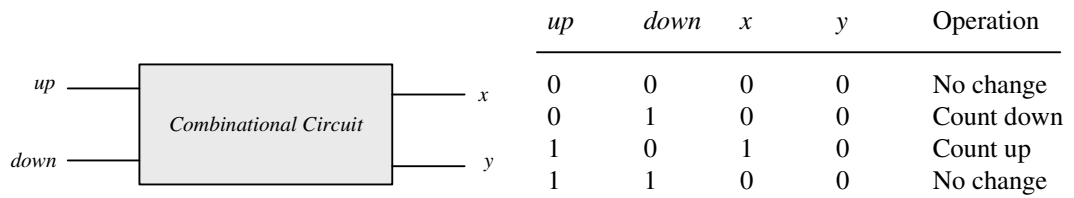
6.18

When $up = down = 1$ the circuit counts up.




6.24

Present state	Next state	Flip-flop inputs		
<i>ABC</i>	<i>ABC</i>	<i>T_A</i>	<i>T_B</i>	<i>T_C</i>
000	001	0	0	1
001	011	0	1	0
010	xxx	x	x	x
011	111	1	1	0
100	000	1	1	0
101	xxx	x	x	x
110	100	0	1	0
111	110	0	0	1

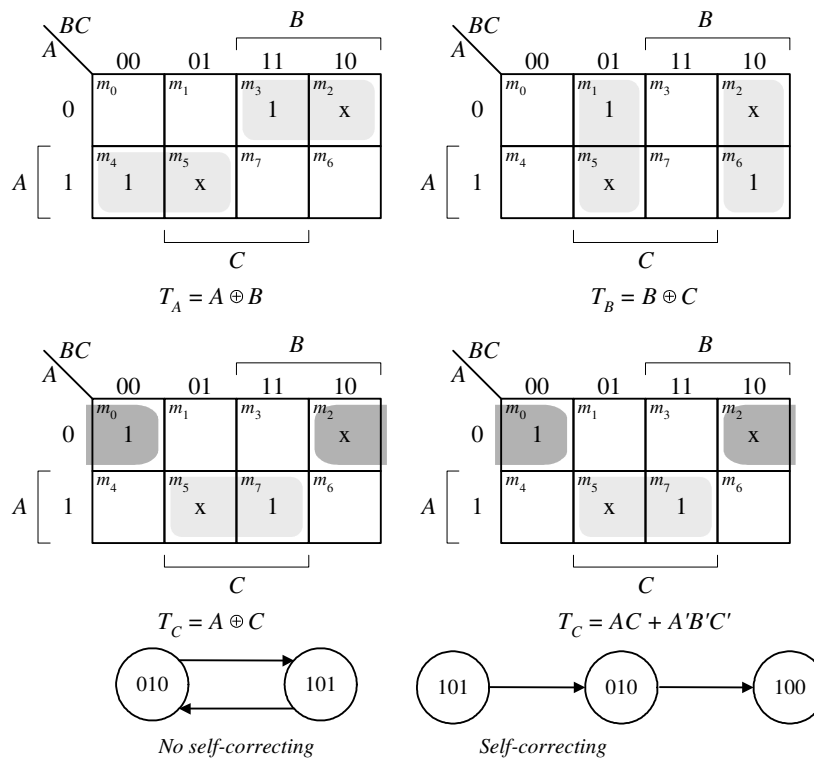

6.27


Present state	Next state	Flip-flop inputs					
ABC	ABC	J_A	K_A	J_B	K_B	J_C	K_C
000	001	0	x	0	x	1	x
001	010	0	x	1	x	x	1
010	011	0	x	x	0	1	x
011	100	1	x	x	1	x	1
100	100	x	x	0	0	1	x
101	110	x	x	1	x	x	1
110	000	x	x	x	1	0	x
111	xxx	x	x	x	x	x	x

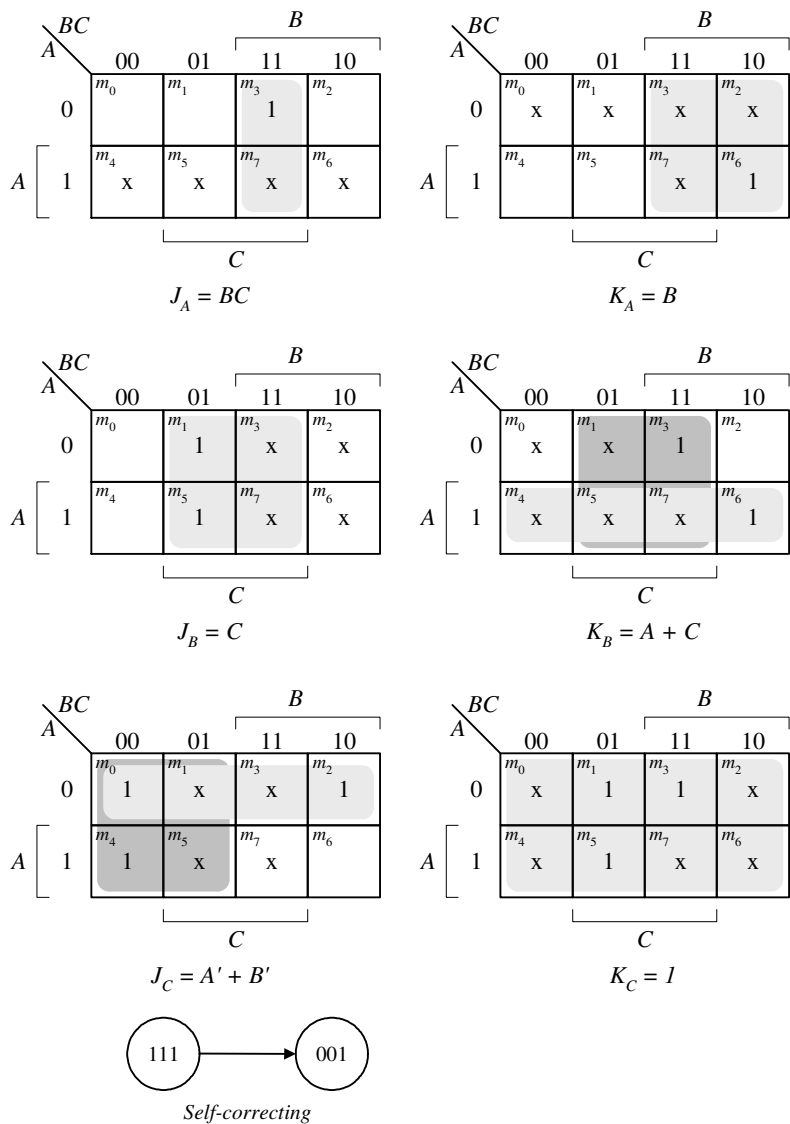

6.29 (a) The 8 valid states are in Fig. 6.18(b), with the sequence: 0, 8, 12, 14, 15, 7, 3, 1, 0, ...
 The 8 unused states and their next states are shown below:

<i>State</i>	<i>Next state</i>	<i>All invalid states</i>
<i>ABCE</i>	<i>ABCE</i>	
0000	1001	9
0100	1010	10
0101	0010	2
0110	1011	11
1001	0100	4
1010	1101	13
1011	0101	5
1101	0110	6

(b) Modification: $D_C = (A + C)B$.

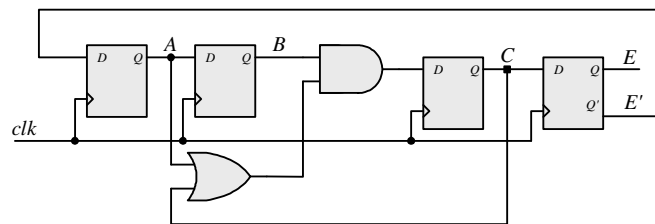

The valid states are the same as in (a). The unused states have the following sequences:

$2 \rightarrow 9 \rightarrow 4 \rightarrow 8$ and $10 \rightarrow 13 \rightarrow 6 \rightarrow 11 \rightarrow 5 \rightarrow 0$. The final states, 0 and 8, are valid.