 


Memory and Programmable Logic




Chun-Jen Tsai
National Chiao Tung University
12/06/12

High Capacity Memory Device


- ❑ Flip-flops are used only for small amount of data storage; different technology must be used for large amount of data storage
- ❑ RAM – Random-Access Memory
 - Allows both read and write operations at any selected storage cells
- ❑ ROM – Read-Only Memory
 - Allows only read operation; can be treated as a programmable logic device

Programmable Logic Devices

 - ❑ A programmable logic device (PLD) is a device that has a generic gate level structure that can be used to implement different digital circuits



Conventional OR gate symbol

 


Programmable OR gate symbol

- ❑ Examples of PLD are:
 - ROM
 - Programmable Logic Array (PLA)
 - Programmable Array Logic (PAL)
 - Field-programmable Gate Array (FPGA)

Random-Access Memory

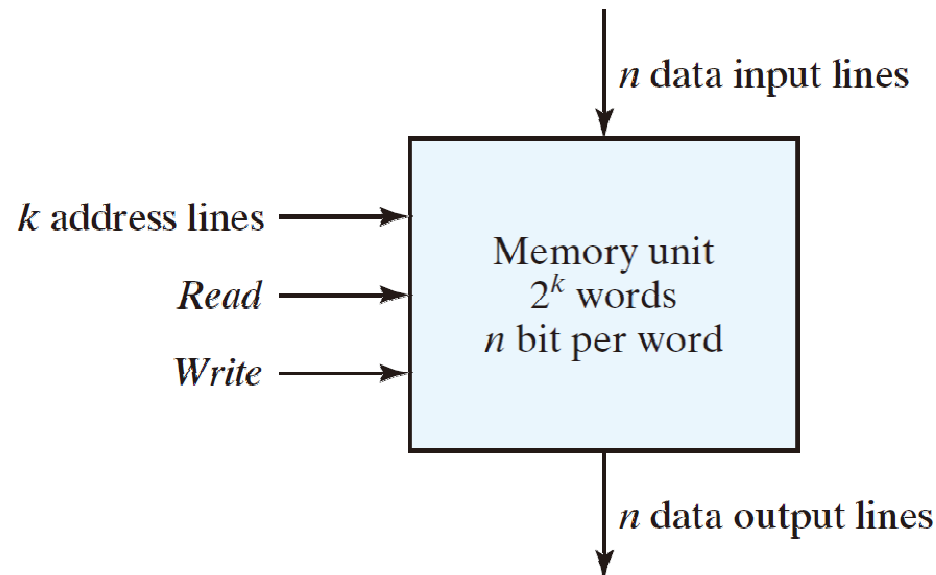- ❑ A memory device stores binary information in groups of bits, typically called “words”
- ❑ Each word can be identified by an “address”
- ❑ Block diagram of a memory device



Example: an 1024×16 Memory

- ❑ A 1024×16 device has 10-bit address lines and 16-bit data lines
 - Data input lines and data output lines may be separated

Memory address		Memory content
Binary	Decimal	
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101

Write and Read Operations

☐ Write operation

- Apply the binary address to the address lines
- Apply the data bits to the data input lines
- Activate the *write* input

☐ Read operation

- Apply the binary address to the address lines
- Activate the *read* input

Control Inputs to Memory Chip


Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word

Timing Waveforms

- ❑ The operation of the memory unit is controlled by an external device called memory controllers
- ❑ The *access time* is the time required to select a word and read it
- ❑ The *cycle time* is the time required to complete a write operation
- ❑ The read and write operations must be synchronized with an external clock

Timing Diagram of Write Operations

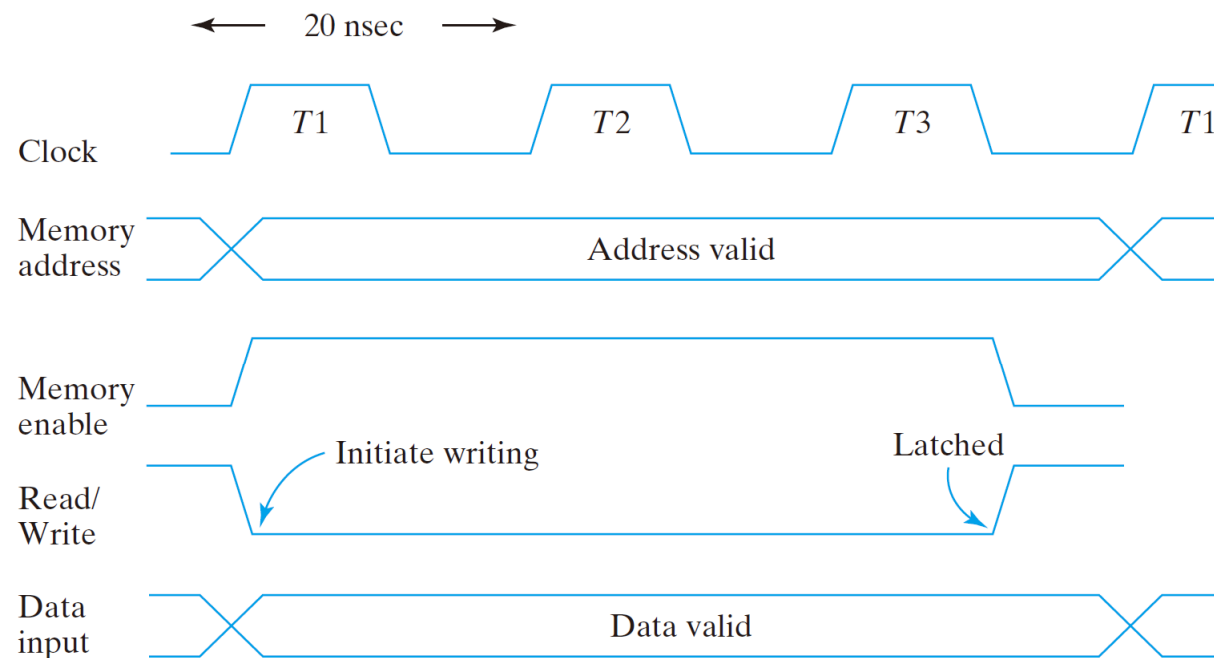
- ❑ CPU clock – 50 MHz
- ❑ The access/cycle time < 50 ns



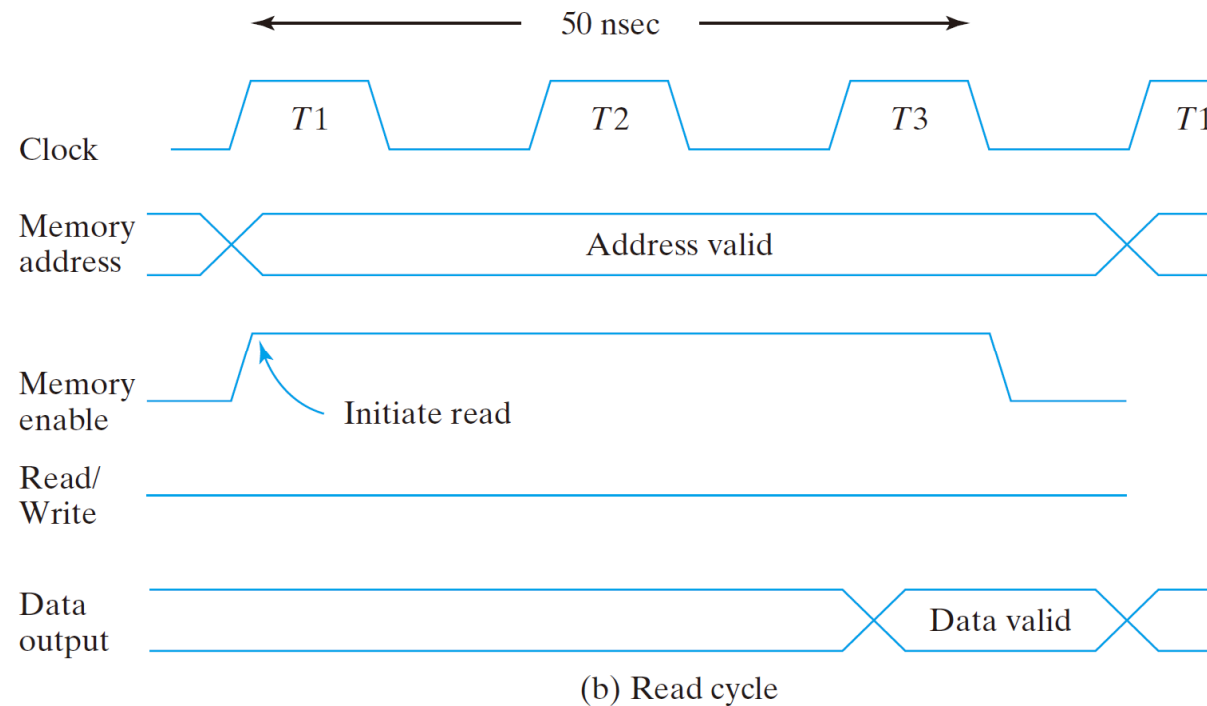(a) Write cycle

Timing Diagram of Read Operations

- ❑ In practice, due to the effect of the memory controller, a read cycle can be longer than a write cycle



Types of Memories (1/2)

- ❑ Static memory devices (e.g. SRAM)
 - Information are stored in latches
 - Remains valid as long as power is applied
 - Short read/write cycle
- ❑ Dynamic memory devices (e.g. DRAM)
 - Information are stored in the form of charges on capacitors
 - The stored charge tends to discharge with time
 - Need to be refreshed (by read-and-write-back, similar to what a buffer gate does)
 - Reduced power consumption
 - Larger memory capacity

Types of Memories (2/2)

☐ Volatile memory


- Lose stored information when power is turned off
- SRAM, DRAM

☐ Non-volatile memory

- Retains its stored information after the removal of power
- ROM
- EPROM, EEPROM
- Flash memory

Memory Decoding

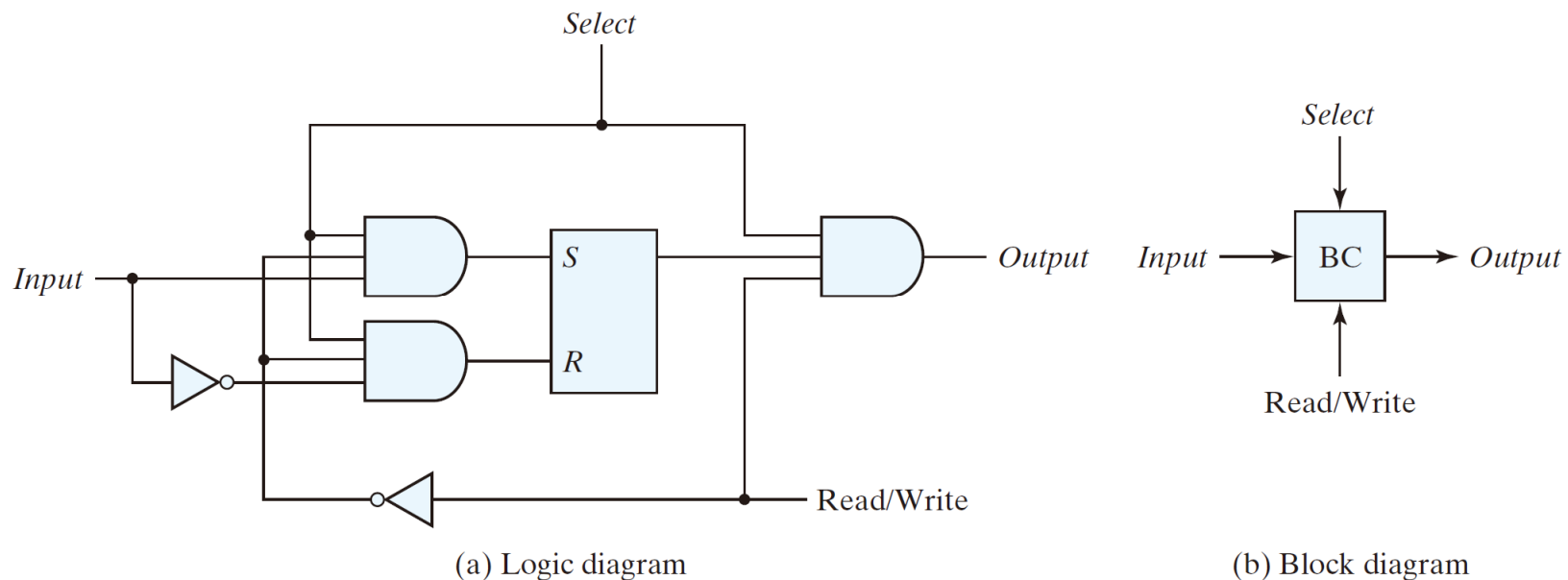- ❑ A memory unit is a storage components that has a decoding circuits to select the memory word for read/write operation
- ❑ The logic diagram of a memory binary cell (BC):




Internal Construction of RAM (1/2)

- ❑ A RAM of m words and n bits per word requires $m \times n$ binary storage cells
- ❑ The decoding circuits for selecting each individual word is a $k \times 2^k$ decoder, where $k = \lceil \log_2 m \rceil$
 - The decoder requires 2^k AND gates with k inputs per gate


Internal Construction of RAM (2/2)

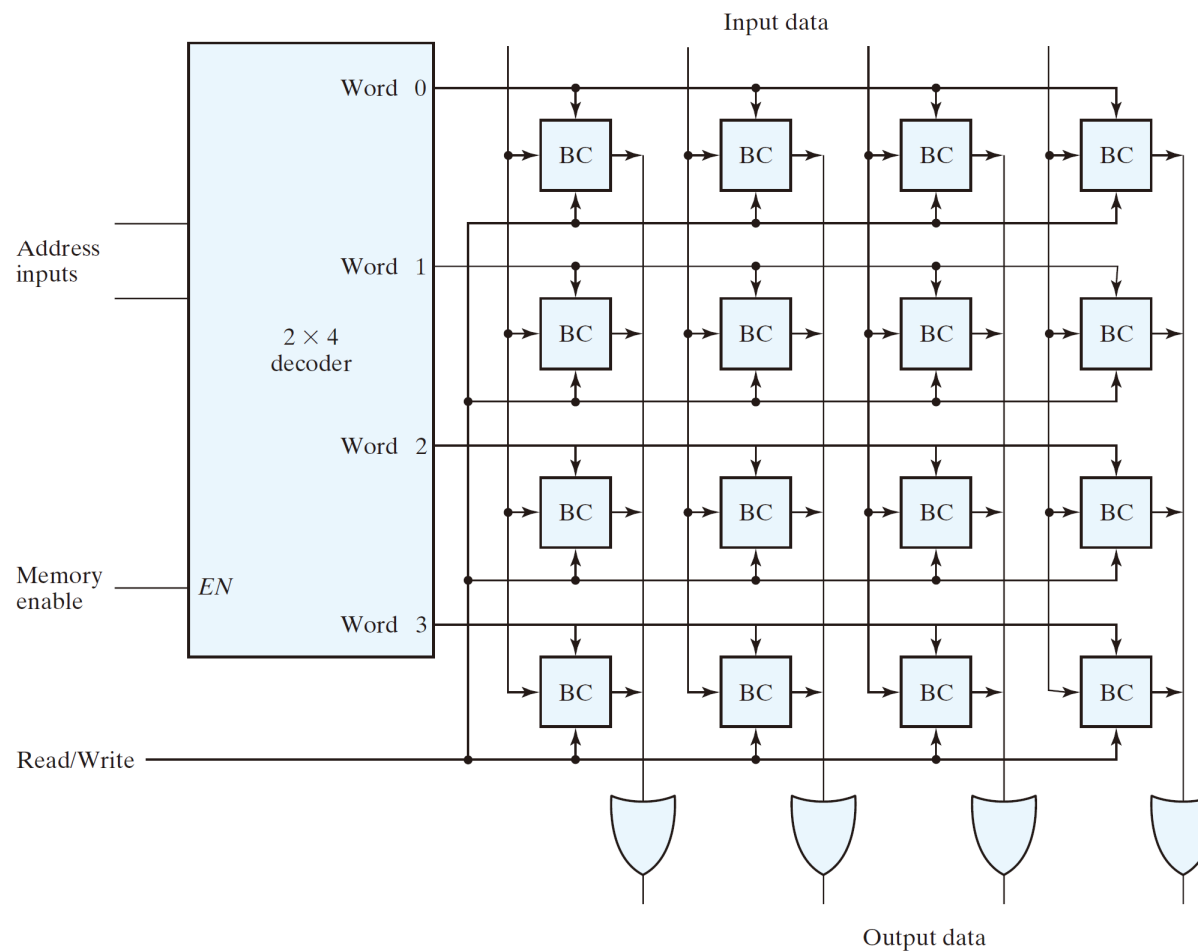- Example: a 4×4 RAM (a four 4-bit words RAM)



Coincident Decoding

 - ❑ To reduce the complexity of the address decoder, we can split the address into row and column addresses
 - A 10×1024 decoder needs 1024 10-input AND gates
 - Two 5×32 decoders need $2 \times (32 \text{ 5-input AND gates})$




Address Multiplexing (1/2)

- ❑ Address multiplexing is often used to reduce the number of pins in the IC package
 - A 64M×1 DRAM requires 26-bit address lines, which can be multiplexed into one set of, say 10, address input pins
- ❑ As in coincident decoding, an address is composed of a column address and a row address
- ❑ The signals CAS and RAS are used to indicate the current address type on the address lines
 - RAS – row address strobe
 - CAS – column address strobe

Address Multiplexing (2/2)

❑ Address multiplexing of a 64K DRAM:

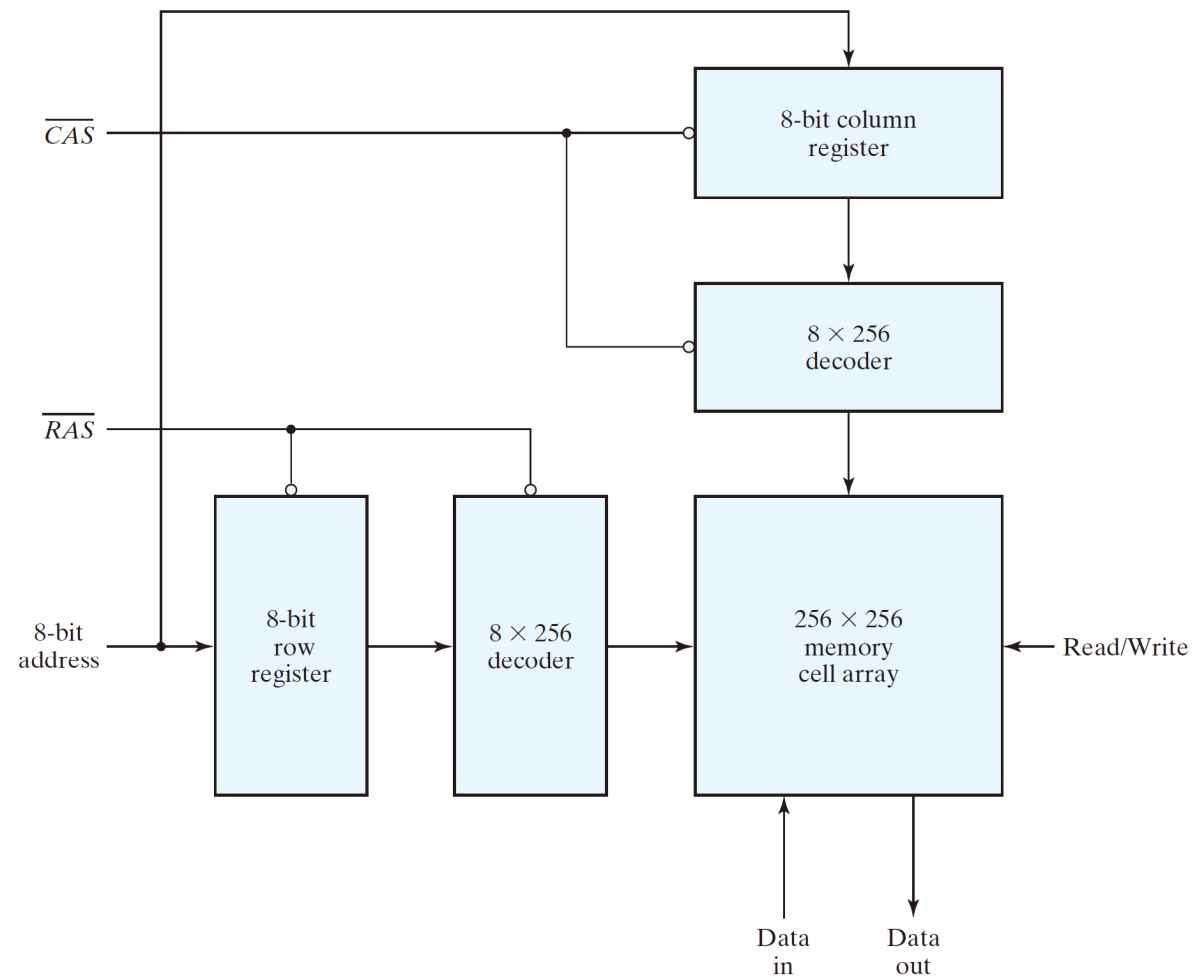

Error Detection And Correction

- ❑ Error detection and correction can improve the reliability of a memory unit
- ❑ A single parity bit can be used to detect errors in a word, but cannot correct errors
- ❑ An error-correction code must be used to correct errors:
 - Generates multiple parity check bits
 - The check bits generate a unique pattern, called a syndrome, which identify the specific bit in error

Hamming Code

❑ In Hamming code, k parity bits are added to an n -bit data word

- The bit positions are numbered in sequence from 1 to $n + k$, those positions numbered as a power of 2 are for the parity bits and the remaining bits are the data bits

- Example: for $n = 8$, $k = 4$:

Bit Position:	1	2	3	4	5	6	7	8	9	10	11	12
	P_1	P_2	D_1	P_4	D_2	D_3	D_4	P_8	D_5	D_6	D_7	D_8

- Note that k must fulfill the following constraint: $2^k - 1 \geq n + k$

Number of Check Bits, k	Range of Data Bits, n
3	2–4
4	5–11
5	12–26
6	27–57
7	58–120

ECC Example (1/3)

□ For $n = 8$ bits data word 11000100, we can design the following even parity check rule:

- $P1 = \text{XOR of bits (3, 5, 7, 9, 11)} = 1 \oplus 1 \oplus 0 \oplus 0 \oplus 0 = 0$
- $P2 = \text{XOR of bits (3, 6, 7, 10, 11)} = 1 \oplus 0 \oplus 0 \oplus 1 \oplus 0 = 0$
- $P4 = \text{XOR of bits (5, 6, 7, 12)} = 1 \oplus 0 \oplus 0 \oplus 0 = 1$
- $P8 = \text{XOR of bits (9, 10, 11, 12)} = 0 \oplus 1 \oplus 0 \oplus 0 = 1$

□ Therefore, the stored 12-bit word becomes:

001110010100

ECC Example (2/3)


- ❑ When the 12 bits are read from the memory
 - Check bits are calculated
$$C_1 = \text{XOR of bits (1, 3, 5, 7, 9, 11)}$$
$$C_2 = \text{XOR of bits (2, 3, 6, 7, 10, 11)}$$
$$C_4 = \text{XOR of bits (4, 5, 6, 7, 12)}$$
$$C_8 = \text{XOR of bits (8, 9, 10, 11, 12)}$$
- ❑ If no error, the syndrome $C = C_8C_4C_2C_1 = 0000$
- ❑ If only a single error occurred in bit position j , then syndrome is the binary code of j . That is: $j = 8 \times C_8 + 4 \times C_4 + 2 \times C_2 + C_1$
- ❑ If more than one bits are in error, they cannot be corrected

ECC Example (3/3)

- ❑ Previous Hamming code can detect and correct only a single error, multiple errors can not be detected.
- ❑ An extra even parity bit P of the $n+k$ coded bits can be used to further detect double errors:
 - If $C = 0$, $P = 0$, no error
 - If $C \neq 0$, $P = 1$, detects a single error that can be corrected
 - If $C \neq 0$, $P = 0$, detects an uncorrectable double-error
 - If $C = 0$, $P = 1$, an error occurred in the P bit

Read-Only Memory

 
- ❑ ROM is used to store permanent binary information
- ❑ A $2^k \times n$ ROM has:
 - k address input lines
 - n data outputs



- ❑ A ROM used for circuit implementation also has
 - An enable inputs
 - Three-state outputs

 Example: 32×8 ROM (1/3)

- ❑ Requires a 5×32 decoder
 - 8 OR gates (each has 32 inputs)
 - 32×8 internal programmable connections



Example: 32×8 ROM (2/3)

- The ROM contents can be specified by a truth table:


ROM Truth Table (Partial)

Inputs					Outputs							
I_4	I_3	I_2	I_1	I_0	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		\vdots						\vdots				
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

- Programmable interconnections are used to program the ROM

 Example: 32×8 ROM (3/3)

- Programmable interconnections can close or open the joint of two crossing lines by a fuse or anti-fuse



Combinational Circuit Using ROM


- ❑ A ROM is a decoder plus OR gates
 - Can express sum of minterms
 - For an n -input, m -output combinational circuit, we need a $2^n \times m$ ROM
- ❑ Design procedure:
 1. Determine the size of the ROM to be used
 2. Obtain the truth table to be implemented
 3. The truth table will be used as the fuse pattern

ROM of a 3-input, 6-output Function

□ The truth table of the function:

Inputs			Outputs						Decimal
A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

□ Simplified function:

 

(a) Block diagram

A_2	A_1	A_0	B_5	B_4	B_3	B_2
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0


(b) ROM truth table

Types of ROM


- ❑ Mask programming ROM
 - Through IC fabrication
 - Economical only if large quantities
- ❑ Programmable ROM (PROM)
 - Programming using fuses with a programmer
- ❑ Erasable PROM (EPROM)
 - Programming using floating gate transistors, using ultraviolet light for erasing
- ❑ Electrically erasable PROM (EEPROM)
 - Electronically erasable floating gate transistors
 - Popular today, known as flash storage
 - Limited times of write operations

Combinational PLDs

 - Programmable two-level logic is composed of an AND array and an OR array



(a) Programmable read-only memory (PROM)

 

(b) Programmable array logic (PAL)



(c) Programmable logic array (PLA)

Programmable Logic Array

❑ A PLA has

- an array of programmable AND gates
 - can generate any product terms of the inputs
- an array of programmable OR gates
 - can generate the sums of the products
- use less circuits than ROM
 - only the needed product terms are generated


PLA Implementation of a Function

□ Example:
for a 3-input,
2-output
function:

■ $F_1 = AB' + AC + A'BC'$

■ $F_2 = (AC + BC)'$

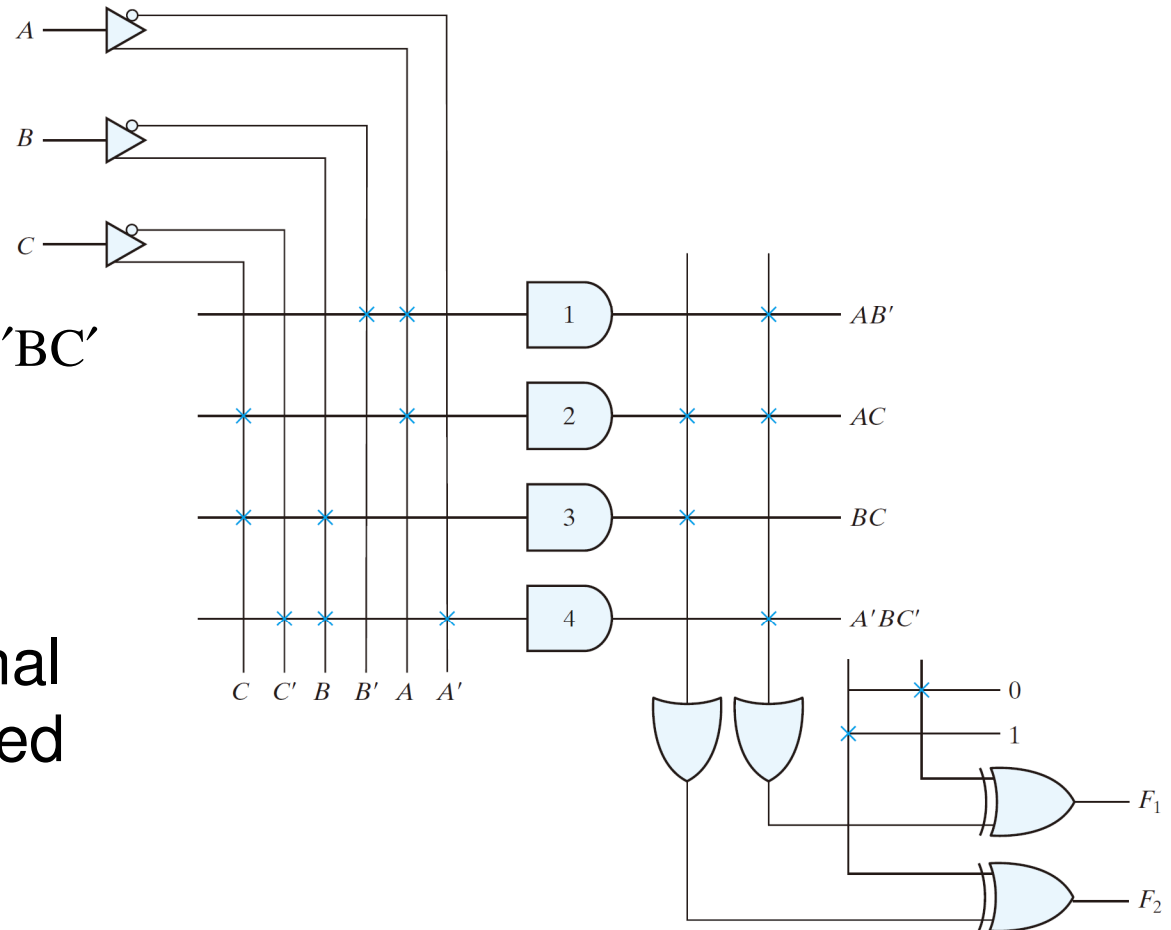□ XOR gates are
used to take
either the original
or complemented
outputs



PLA Programming Table

- ❑ We use a PLA programming table to specify the fuse map of the device
- ❑ Example:

PLA Programming Table

Product Term		Inputs			Outputs	
					(T)	(C)
		A	B	C	F ₁	F ₂
AB'	1	1	0	—	1	—
AC	2	1	—	1	1	1
BC	3	—	1	1	—	1
A'BC'	4	0	1	0	1	—

Note that:

1. T stands for “true” and C stands for “complement”
2. “—” means the literal (or product term) is absent

PLA Implementation Issues

- ❑ The size of a PLA is determined by
 - The number of inputs
 - The number of product terms (AND gates)
 - The number of outputs (OR gates)
- ❑ When implementing with a PLA we must reduce the number of distinct product terms; the number of terms in a product is not important.

Example of PLA Design

- $F_1(A, B, C) = \Sigma (0, 1, 2, 4)$; $F_2(A, B, C) = \Sigma (0, 5, 6, 7)$
 - Both the original and the complement of the function should be checked for simplification

		B			
		BC		00	01
A	0	m_0 1	m_1 1	m_3 0	m_2 1
	1	m_4 1	m_5 0	m_7 0	m_6 0
		C			

		B			
		BC		00	01
A	0	m_0 1	m_1 0	m_3 0	m_2 0
	1	m_4 0	m_5 1	m_7 1	m_6 1
		C			

		B			
		BC		00	01
A	0	m_0 1	m_1 0	m_3 0	m_2 0
	1	m_4 0	m_5 1	m_7 1	m_6 1

- Function form with minimal # product terms

- $F_1 = (AB + AC + BC)'$
- $F_2 = AB + AC + A'B'C'$


PLA programming table

	Product term	Inputs			Outputs	
					(C)	(T)
		A	B	C	F_1	F_2
AB	1	1	1	–	1	1
AC	2	1	–	1	1	1
BC	3	–	1	1	1	–
$A'B'C'$	4	0	0	0	–	1

Programmable Array Logic

- ❑ A PAL contains a programmable AND array and a fixed OR array

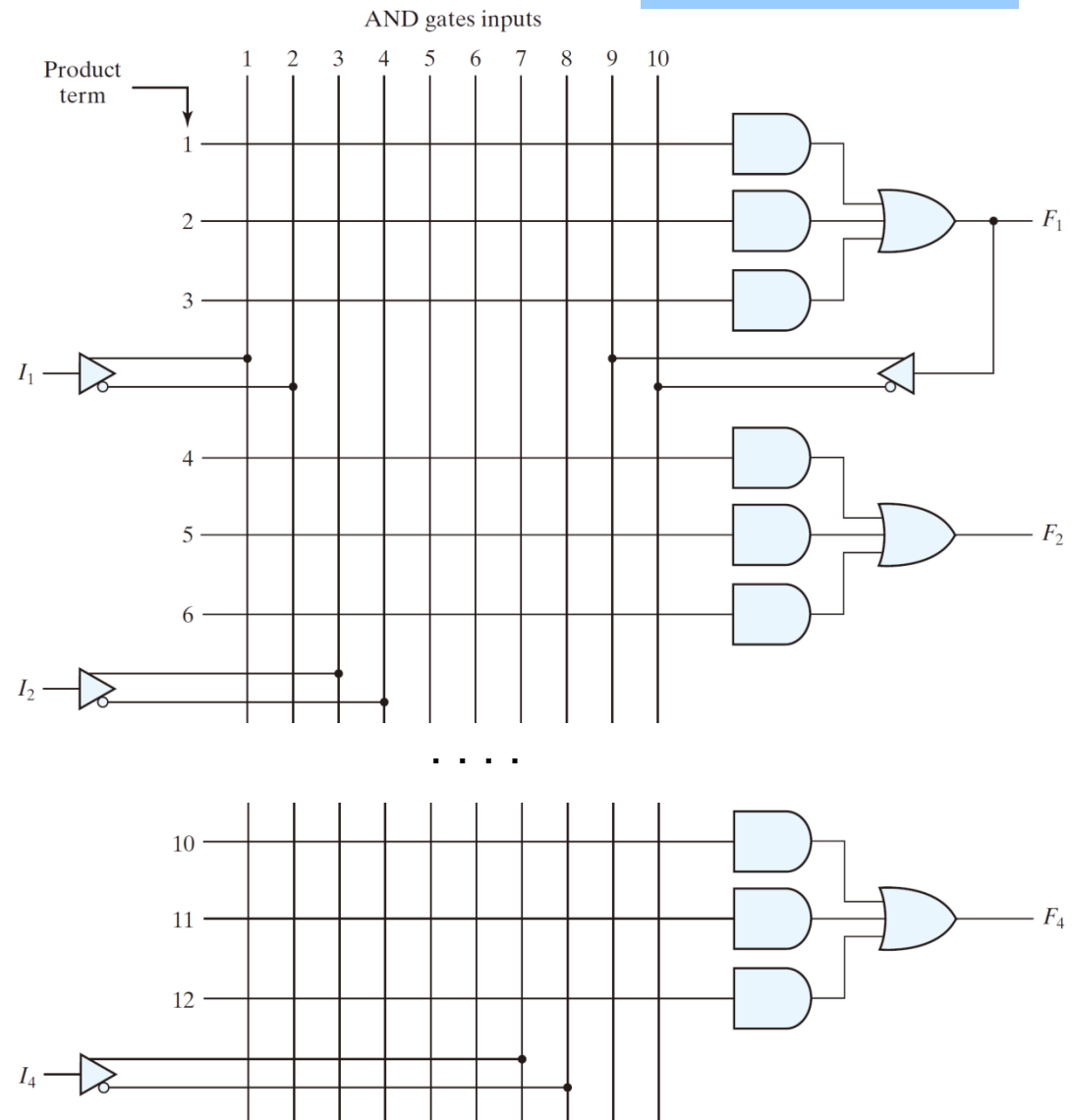- A PAL is easier to program, but is not as flexible as a PLA
- For PAL, product terms cannot be shared



Example of PAL Design (1/3)

❑ Original functions:

- $w(A, B, C, D) = \Sigma(2,12,13)$
- $x(A, B, C, D) = \Sigma(7,8,9,10,11,12,13,14)$
- $y(A, B, C, D) = \Sigma(0,2,3,4,5,6,7,8,10,11,15)$
- $z(A, B, C, D) = \Sigma(1,2,8,12,13)$

❑ Simplified functions:

- $w = ABC' + A'B'CD'$
- $x = A + BCD$
- $y = A'B + CD + B'D'$
- $z = ABC' + A'B'CD' + AC'D' + A'B'C'D$
 $= w + AC'D' + A'B'C'D$

Example of PAL Design (2/3)

- Again, a programming table is used for PAL fuse map for logic implementation

PAL Programming Table

Product Term	AND Inputs					Outputs
	A	B	C	D	w	
1	1	1	0	—	—	$w = ABC' + A'B'CD'$
2	0	0	1	0	—	
3	—	—	—	—	—	
4	1	—	—	—	—	$x = A + BCD$
5	—	1	1	1	—	
6	—	—	—	—	—	
7	0	1	—	—	—	$y = A'B + CD + B'D'$
8	—	—	1	1	—	
9	—	0	—	0	—	
10	—	—	—	—	1	$z = w + AC'D' + A'B'C'D$
11	1	—	0	0	—	
12	0	0	0	1	—	

Example of PAL Design (3/3)


□ The final implementation of the functions:

■ $w = ABC' + A'B'CD'$

■ $x = A + BCD$


■ $y = A'B + CD + B'D'$

■ $z = w + AC'D' + A'B'C'D$

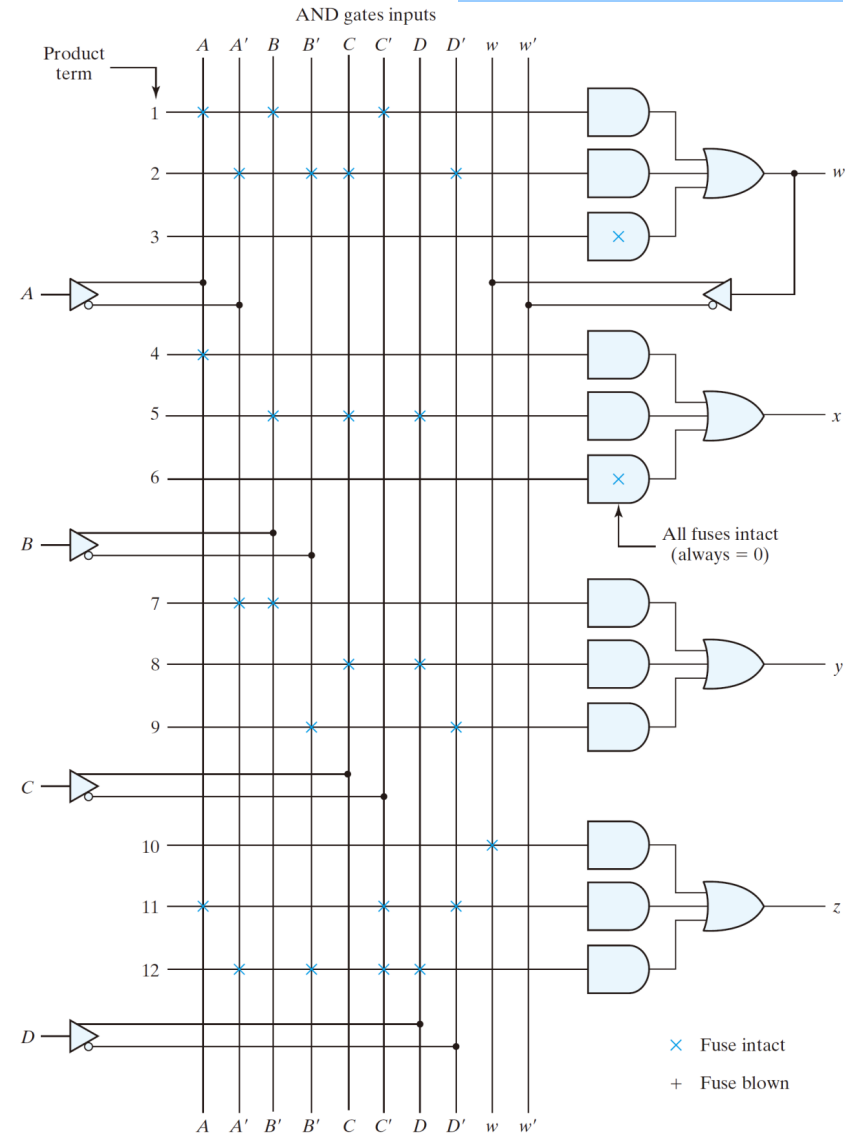


Sequential Programmable Devices

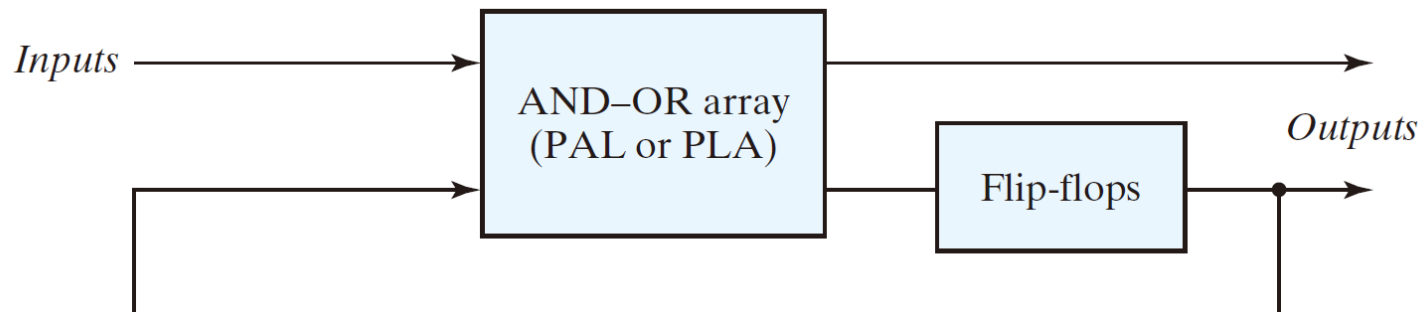- ❑ Sequential programmable logic device is composed of gate level logics and flip-flops
- ❑ There are several types of sequential programmable devices
 - Simple programmable logic device (SPLD)
 - Complex programmable logic device (CPLD)
 - Field programmable gate array (FPGA)



Macrocell of SPLD

 - ❑ A typical SPLD contains 8-10 macrocells, each macrocell has the following architecture:




SPLD Programmable Components

- ❑ The following features of a SPLD can be programmed:
 - AND array
 - Use or bypass the flip-flop
 - Select clock edge polarity
 - Preset or clear for the register
 - Complement or straight output
 - Programmable input/output pins

Complex PLD

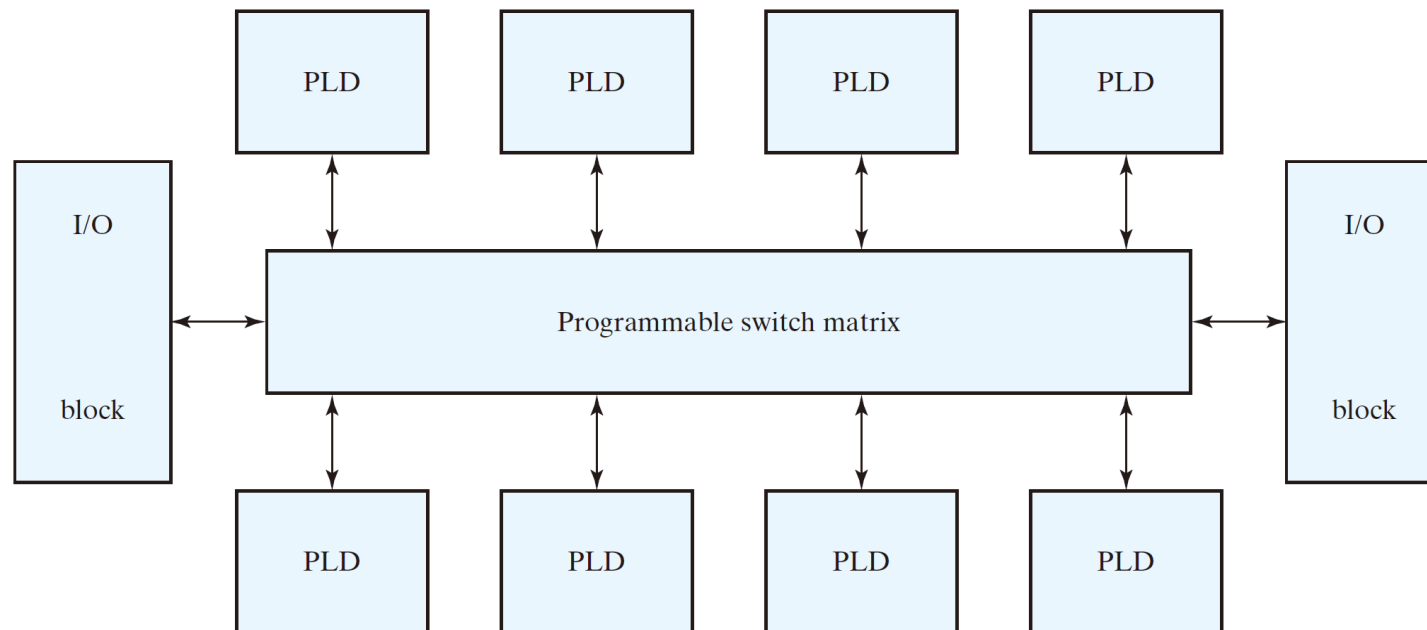- ❑ A CPLD is a device that
 - Puts a lot of PLDS on a chip
 - Add wires between them whose connections can be programmed
 - Use fuse/EEPROM technology




Field-Programmable Gate Array

- ❑ An FPGA emulate gate array technology by lookup tables (LUTs)
- ❑ FPGA can be programmed as easy as programming a flash memory electronically
- ❑ PALs and PLAs typically can implement digital circuits with complexity of 10 ~ 100 gates
- ❑ FPGAs can implement circuits with complexity anywhere from 100 to several millions of gates

Basic Xilinx Architecture


❑ Xilinx Spartan Architecture

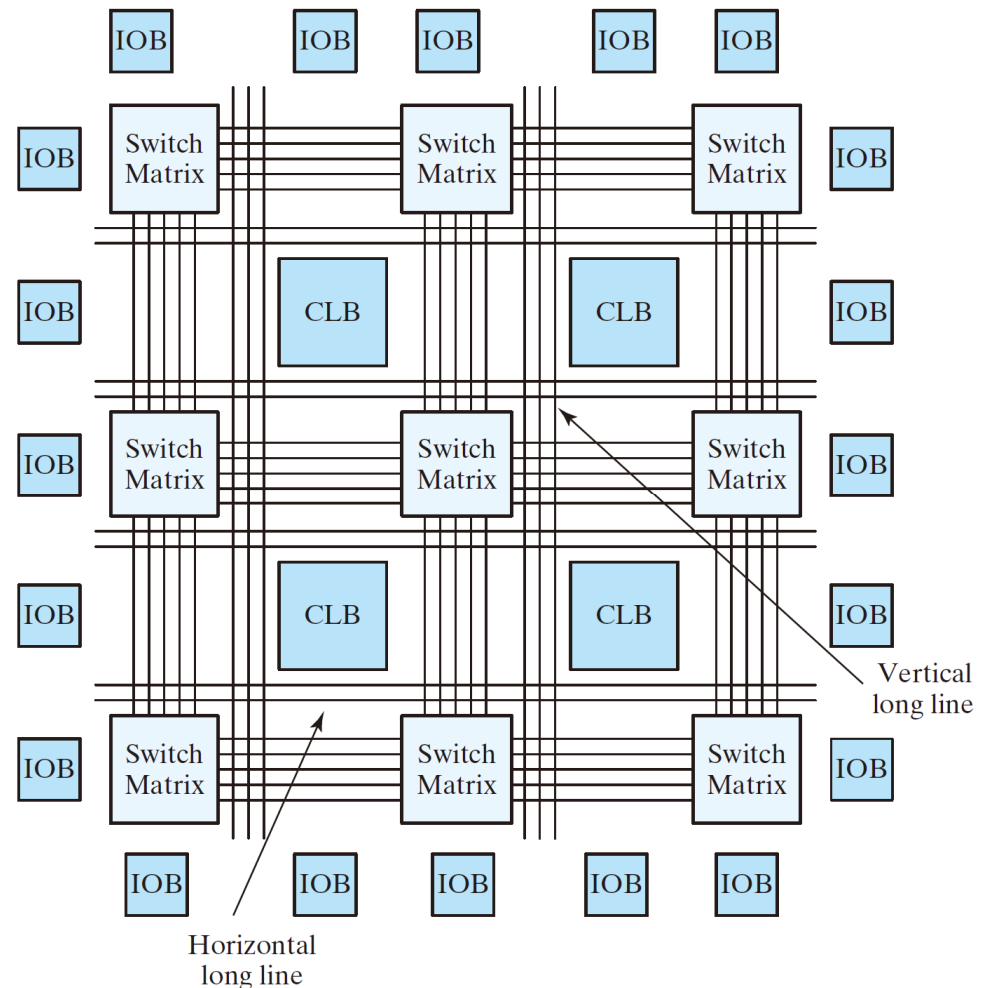- A CLB contains several logic slices
- A logic slice contains several logic cells
- A logic cell contains a lookup tables (LUTs) a flip-flop, and a few gates



Xilinx FPGA Slice

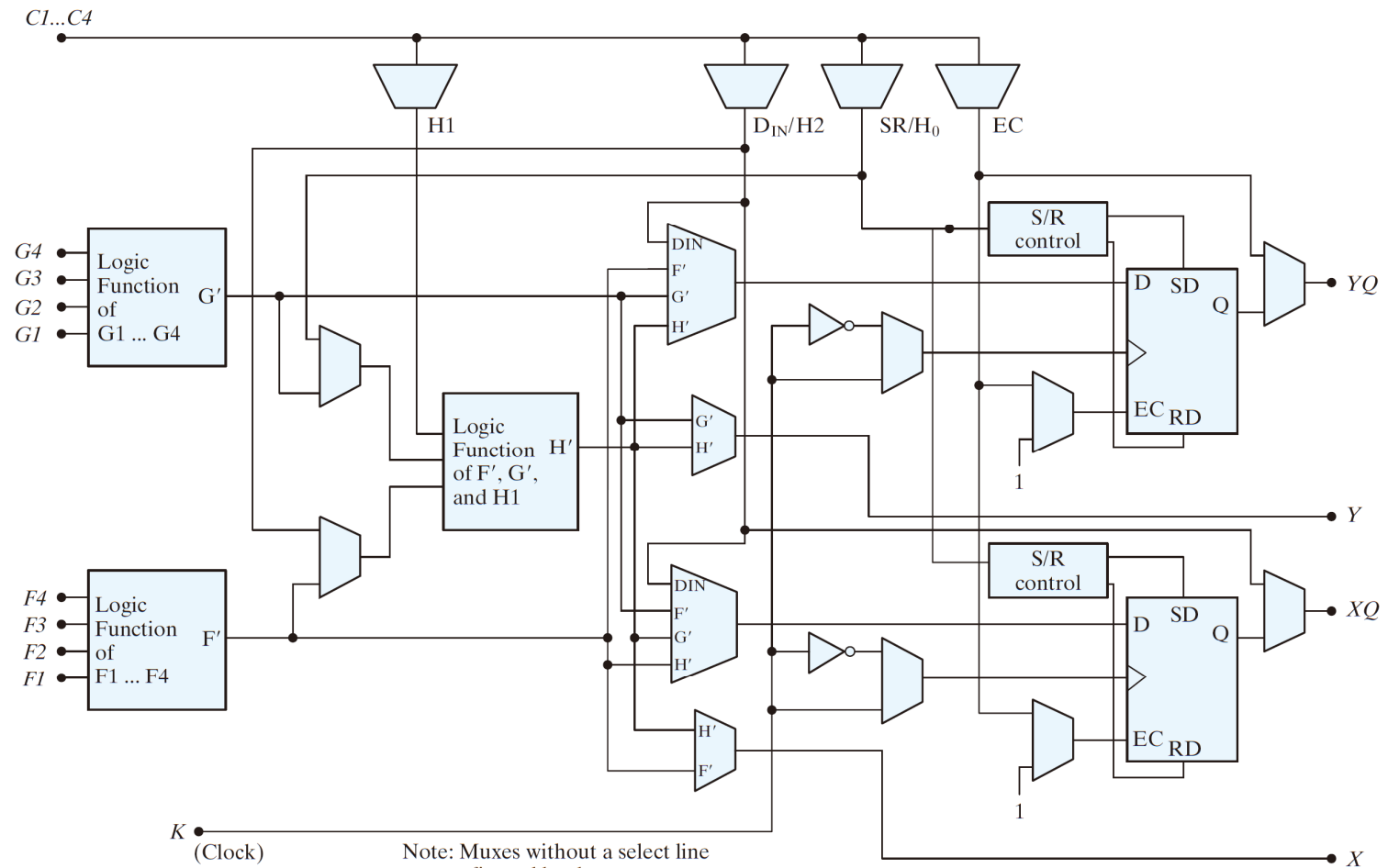
- ❑ A slice is a fine-grain logic unit in Xilinx FPGAs



Note: Muxes without a select line are configured by the program memory.


Interconnect Resources

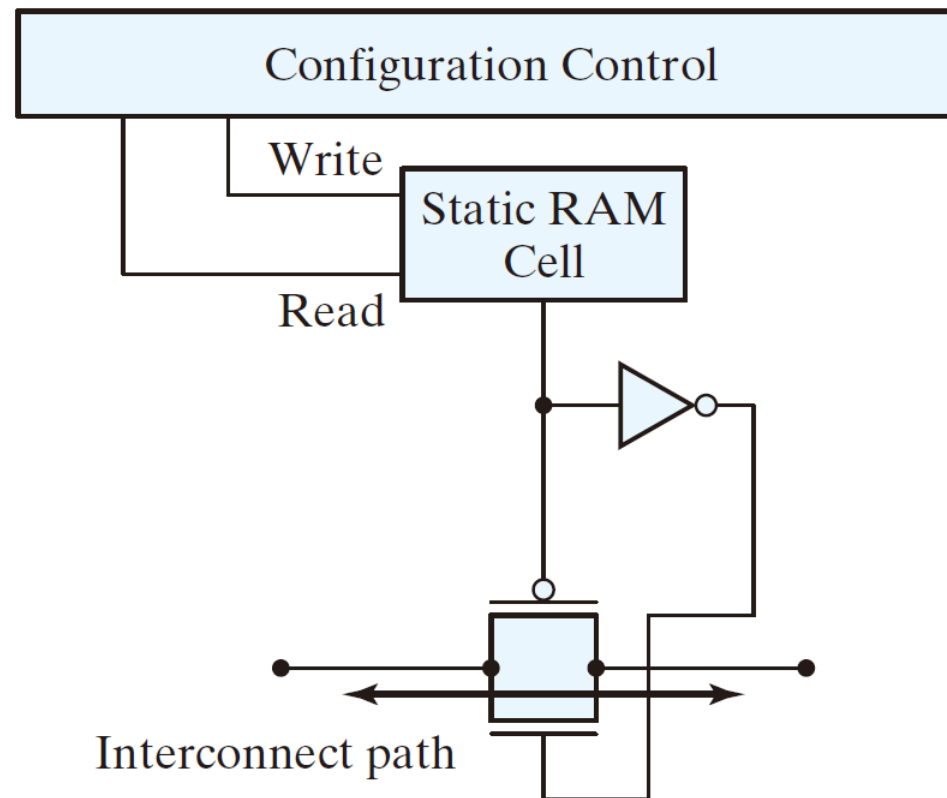- ❑ RAM cell controlling a PIP transmission gate:




Programmable Interconnect Point

 - ❑ Circuit for a programmable interconnect point (PIP)




IO Block

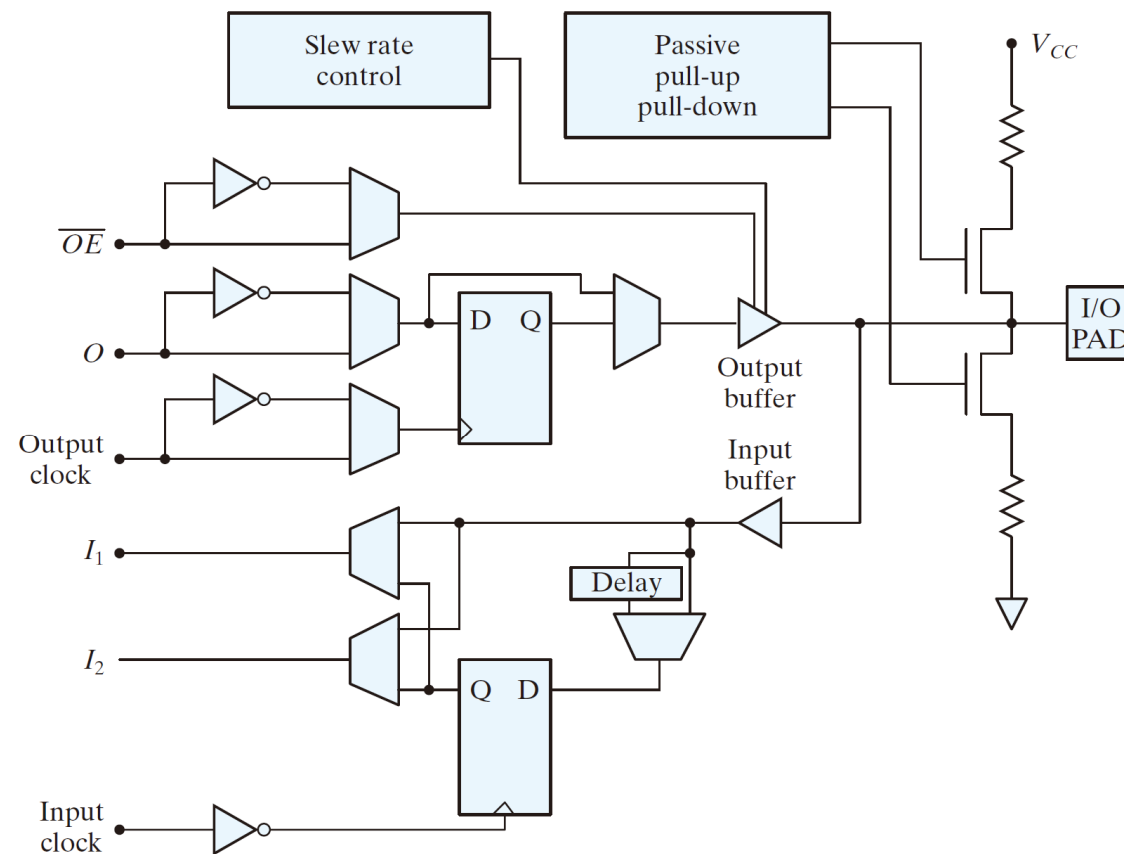- ❑ An FPGA IO block (IOB) is similar to the IO pad in an custom IC




Distributed RAM Cells

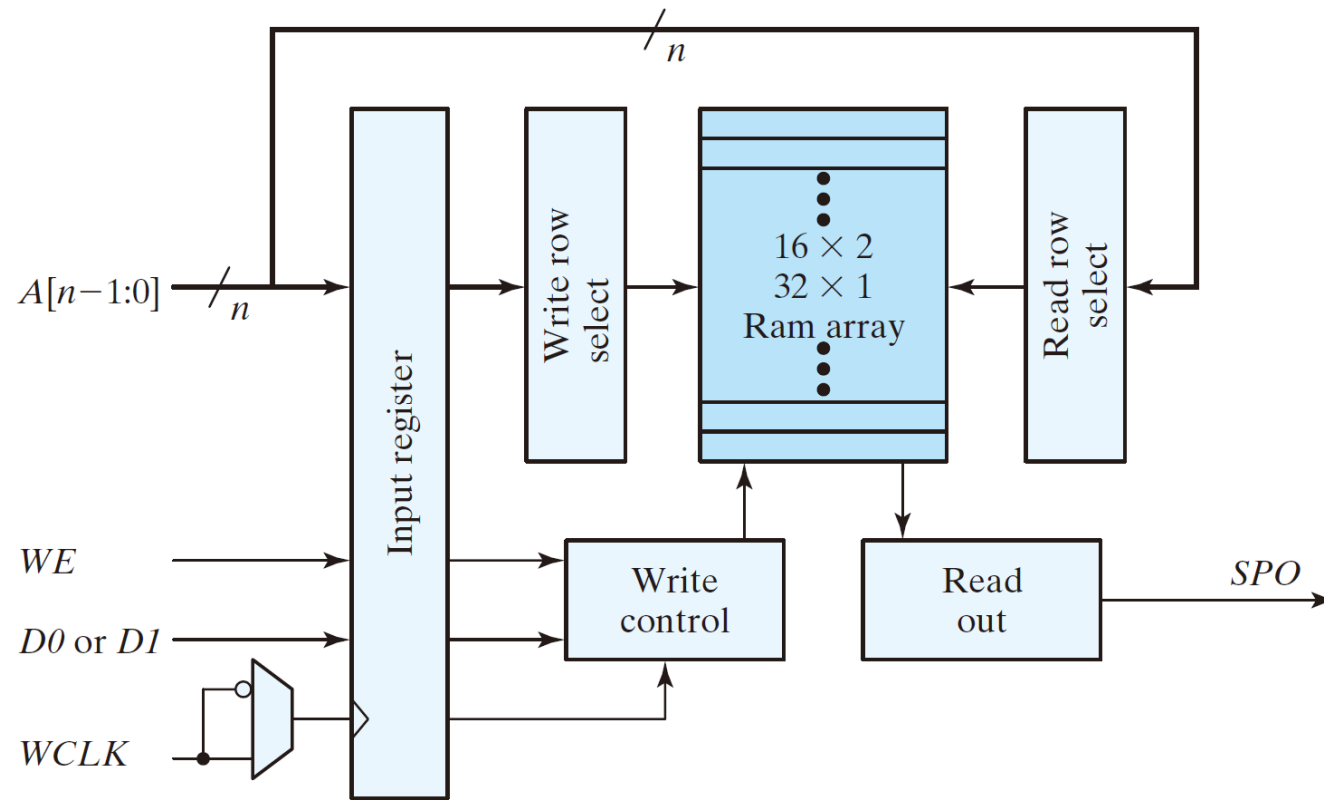- ❑ Distributed RAM cell formed from a lookup table:



Block RAMs

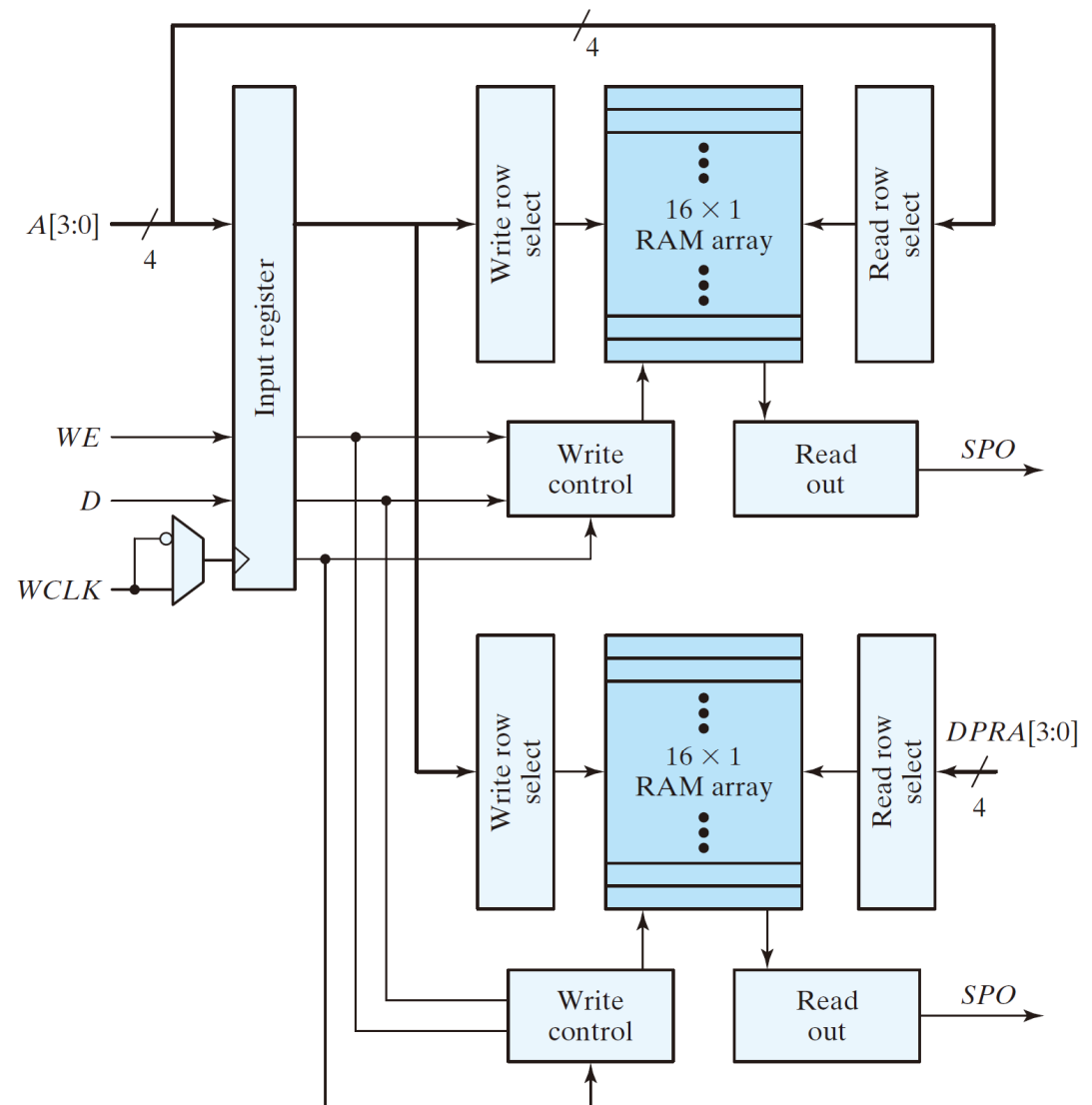- ❑ Xilinx FPGAs contains larger memory devices called BRAMs
 - Dual-port
 - Word-length configurable



Xilinx Spartan II FPGAs


□ Attribute of the Xilinx Spartan II FPGAs

Spartan II FPGAs	XC2S15	XC2S30	XC2S50	XC2S100	XC2S150	XC2S200
System Gates ¹	6K–15K	13K–30K	23K–50K	37K–100K	52K–150K	71K–200K
Logic Cells ²	432	972	1,728	2,700	3,888	5,292
Block RAM Bits	16,384	24,576	32,768	40,960	49,152	57,344
Max Avail I/O	86	132	176	196	260	284

¹20–30% of CLBs as RAM.


²1 Logic cell = four-input lookup table + flip-flop.

Xilinx Spartan II FPGAs

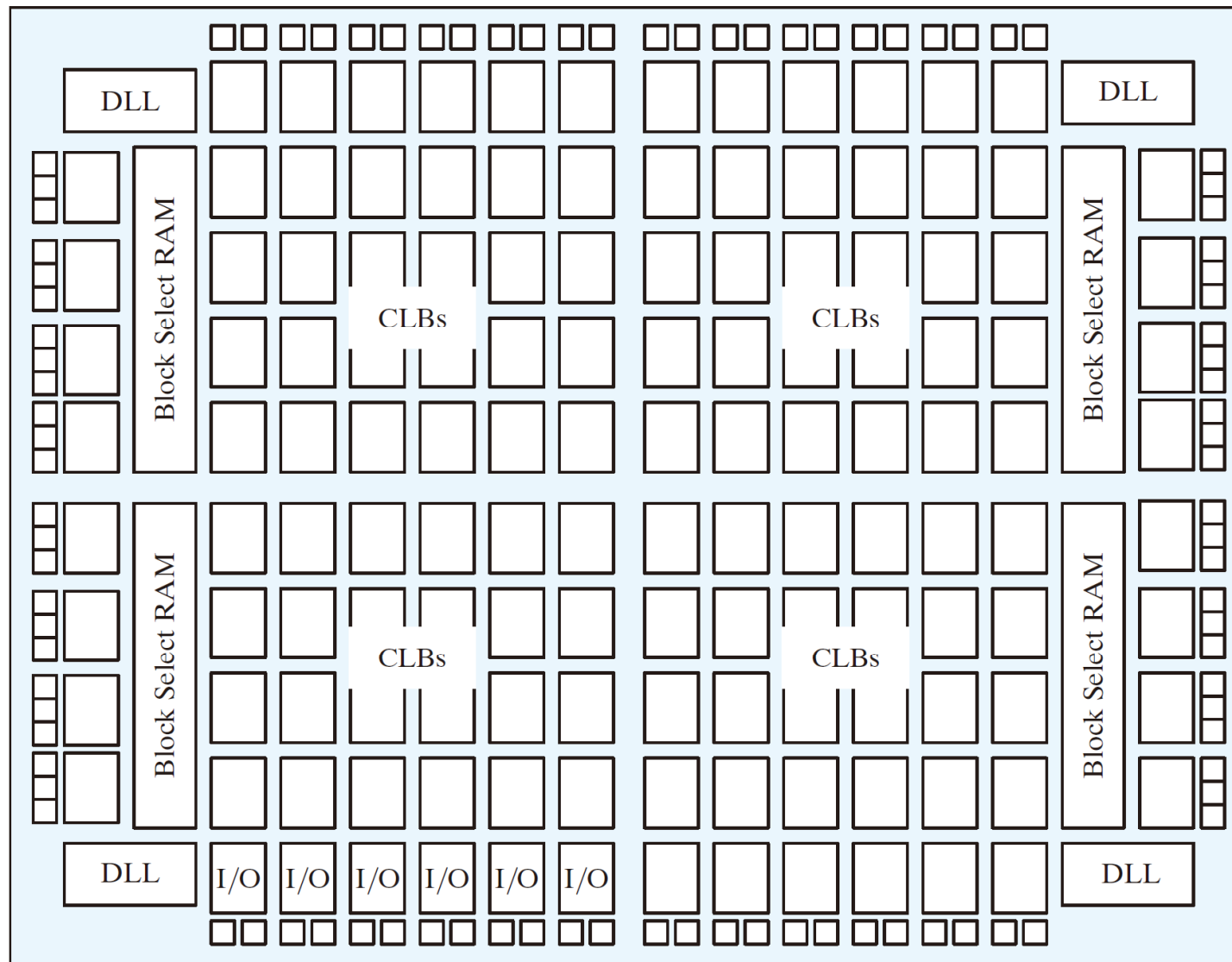


Spartan II CLB Slice


- ❑ Each slice has two logic cells

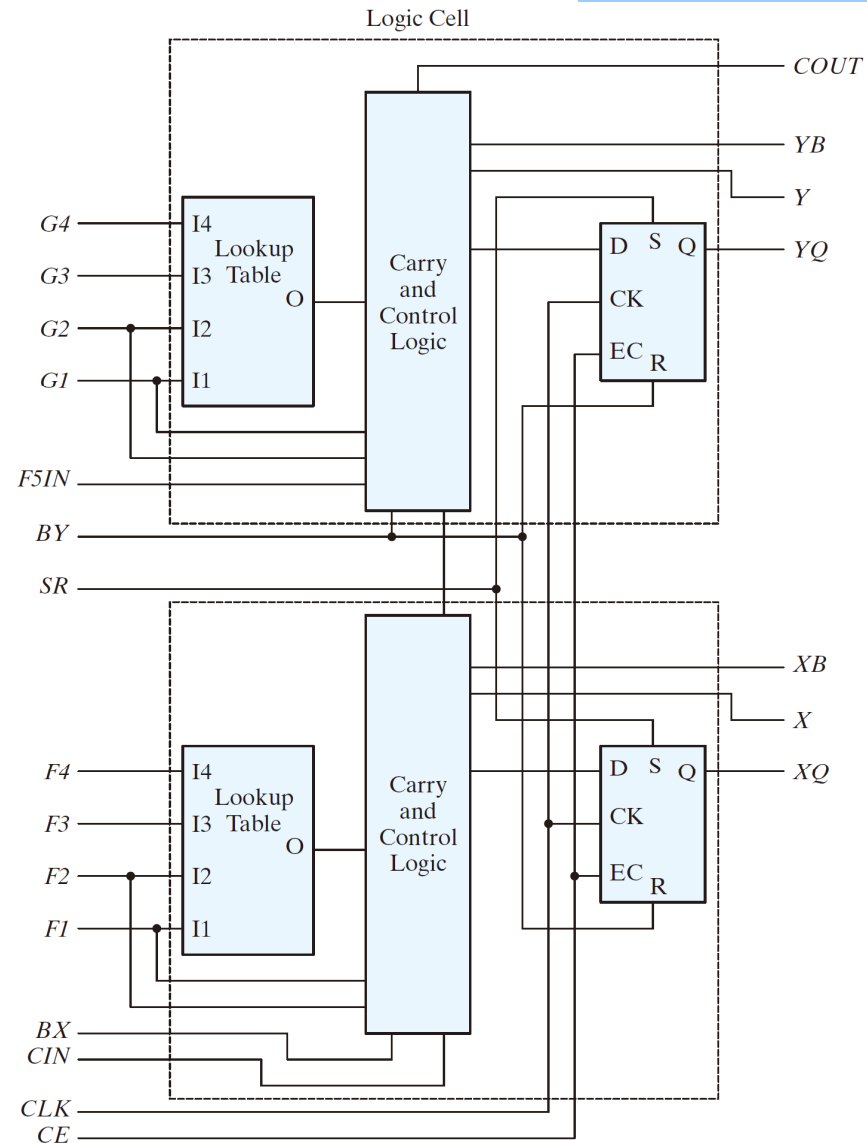

Spartan II IOB

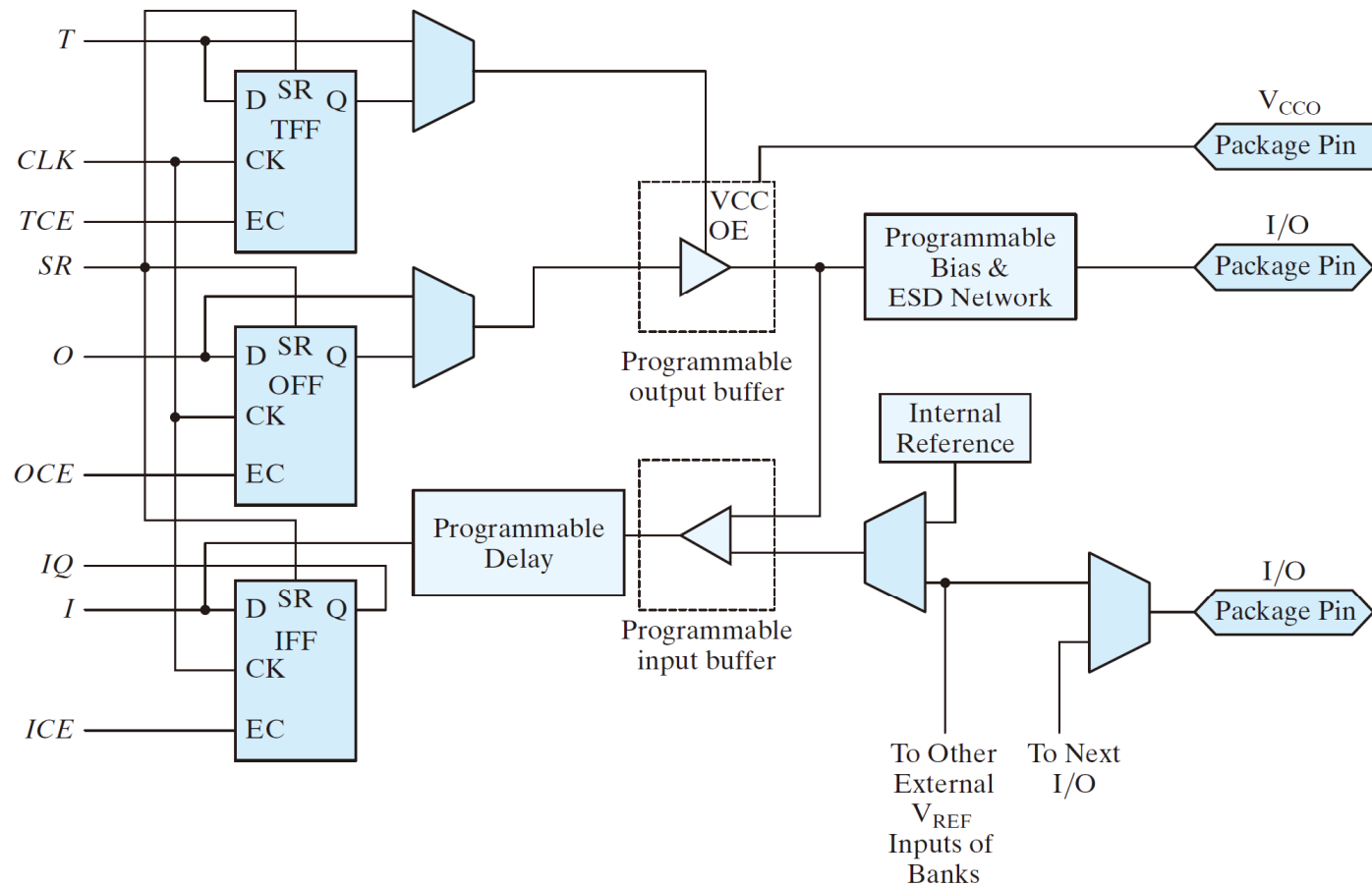

Xilinx Virtex FPGAs

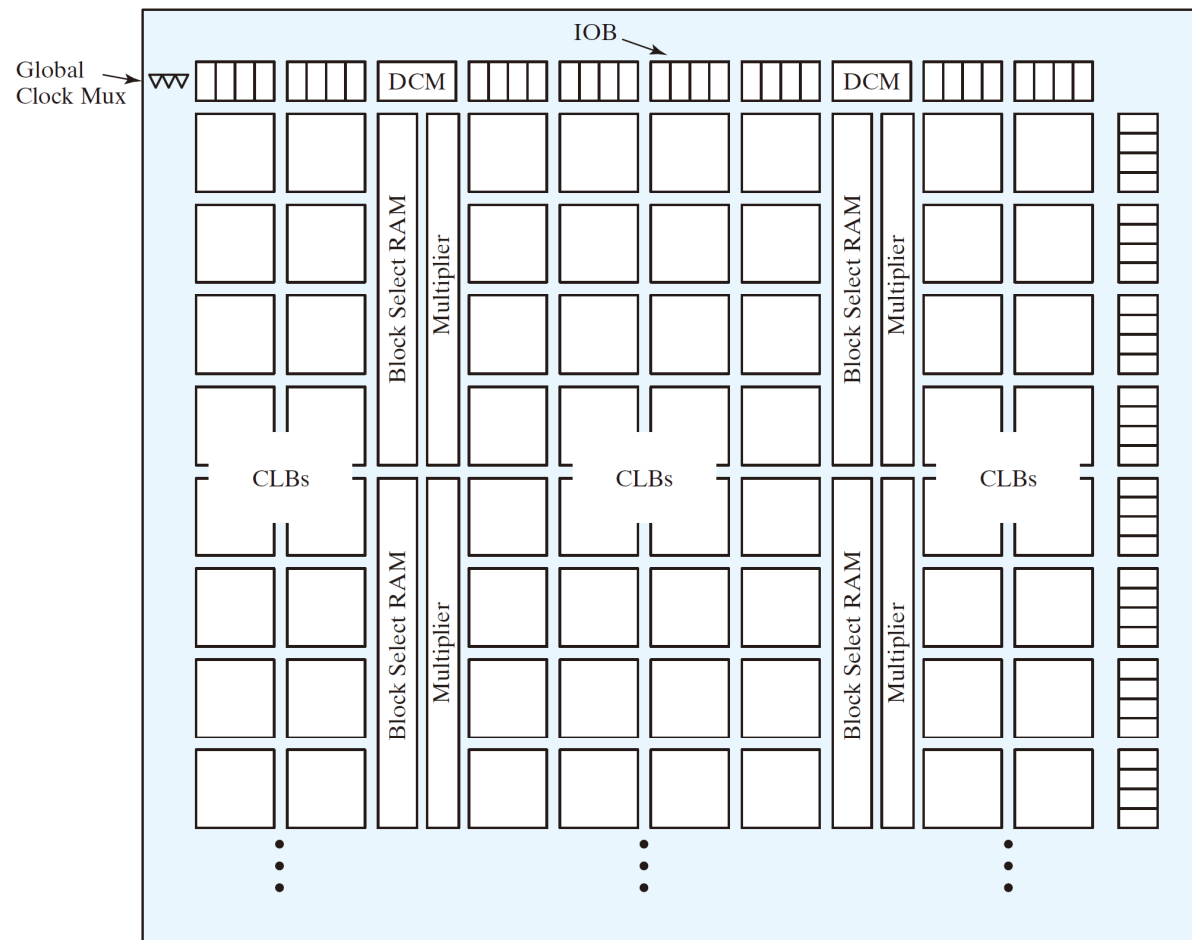

DCM: Clock Manager

Xilinx Virtex IOBs

- ❑ Virtex IOBs support more IO standards at physical layer

