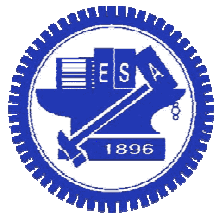


# Gate-Level Minimization



Chun-Jen Tsai  
National Chiao Tung University  
10/11/2012

# Gate-Level Minimization

---

- ❑ The design task of finding an optimal gate-level implementation of Boolean functions describing a digital circuit.
- ❑ Logic minimization approaches:
  - Algebraic approaches: lack specific rules
  - The Karnaugh map (or K-map):
    - a pictorial form of a truth table of a 2-D array of squares
    - each square represents one minterm
    - Certain patterns of adjacent squares have an equivalent (simpler) Boolean expression

# Goal of Minimization

---

- ❑ We assume that the simplest algebraic expression is an algebraic expression with:
  - A minimum number of terms
  - The smallest number of literals in each term
- ❑ Note that
  - The simplified expression may not be unique
  - In practice, the best expression depends on the target technology used to implement the digital circuit

# Two-Variable Map (1/2)

- ❑ A K-map is a truth table illustrated in square diagram
- ❑ Example: a two-variable map
  - A two-variable Boolean function has four minterms
  - $x'$  shows up in row 0;  $x$  shows up in row 1
  - $y'$  shows up in column 0;  $y$  shows up in column 1

$m_0$	$m_1$
$m_2$	$m_3$

(a)


		$y$	
		0	1
$x$	0	$m_0$ $x'y'$	$m_1$ $x'y$
	1	$m_2$ $xy'$	$m_3$ $xy$

(b)


# Two-Variable Map (2/2)
 
## □ Mapping functions to K-maps:

- $xy$  is  $m_3$ , thus we put a 1 in the square of  $m_3$  when the canonical form of the function contains  $m_3$ .
- $x + y = x'y + xy' + xy$ , put 1's in the squares of  $m_1$ ,  $m_2$ , and  $m_3$ .



(a)  $xy$

 

(b)  $x + y$

# Three-Variable Map

- ❑ A three-variable Boolean function has eight minterms
- ❑ The minterm squares are arranged in the K-map by Gray code sequence
  - Any two adjacent squares in the map differ by one variable (i.e, primed in one square and unprimed in the other)  
→ they can be merged into one term
  - Example:  $m_5$  and  $m_7$  can be simplified to  $xz$ .

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$


(a)

		$y$			
		00	01	11	10
$x$	0	$m_0$ $x'y'z'$	$m_1$ $x'y'z$	$m_3$ $x'yz$	$m_2$ $x'yz'$
	1	$m_4$ $xy'z'$	$m_5$ $xy'z$	$m_7$ $xyz$	$m_6$ $xyz'$
		$z$			

(b)
 
# Example: Function Simplification

$$\square F(x, y, z) = \Sigma(2,3,4,5) \rightarrow F = x'y + xy'$$



# Simplification across Boundaries

- ❑ Merging of minterms can go across the boundaries
- ❑ Example:  $m_0$  and  $m_2$  as well as  $m_4$  and  $m_6$  are adjacent
  - $m_0 + m_2 = x'y'z' + x'yz' = x'z' (y' + y) = x'z'$
  - $m_4 + m_6 = xy'z' + xyz' = xz' (y' + y) = xz'$

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$

(a)

		$y$				
		$yz$		00	01	11
$x$	0	$m_0$	$m_1$	$m_3$	$m_2$	
		$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$	
$x$	1	$m_4$	$m_5$	$m_7$	$m_6$	
		$xy'z'$	$xy'z$	$xyz$	$xyz'$	
		$z$				


(b)


 
# Example: $F(x, y, z) = \Sigma(3, 4, 6, 7)$

□  $F$  contains four minterms, or two merged terms:

$$F(x, y, z) = (m_3 + m_7) + (m_6 + m_4) = yz + xz'$$



# Four-Square Simplification

□ Four adjacent squares can be simplified as well:

$$\begin{aligned} \blacksquare m_0 + m_2 + m_4 + m_6 &= x'y'z' + x'yz' + xy'z' + xyz' \\ &= x'z'(y' + y) + xz'(y' + y) \\ &= x'z' + xz' = z' \end{aligned}$$

$$\begin{aligned} \blacksquare m_1 + m_3 + m_5 + m_7 &= x'y'z + x'yz + xy'z + xyz \\ &= x'z(y' + y) + xz(y' + y) \\ &= x'z + xz = z \end{aligned}$$

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$


(a)

		$y$					
		$yz$		00	01	11	10
$x$	0	$m_0$ $x'y'z'$	$m_1$ $x'y'z$	$m_3$ $x'yz$	$m_2$ $x'yz'$		
	1	$m_4$ $xy'z'$	$m_5$ $xy'z$	$m_7$ $xyz$	$m_6$ $xyz'$		
		$z$					

(b)
 
# Example: $F(x, y, z) = \Sigma(0, 2, 4, 5, 6)$


- $F$  contains five minterms, with two overlapping areas, thus, the simplified function becomes  $F = z' + xy'$



Note:  $y'z' + yz' = z'$
 
# Equivalent Function Discovery

- ❑ K-Map can be used to find various forms of the same Boolean expression.
- ❑ Example:  $F = A'C + A'B + AB'C + BC$ 
  - Express it in sum of minterms:  $m_1 + m_2 + m_3 + m_5 + m_7$
  - Find the minimal sum of products expression:  $A'B + C$



# Four-Variable Maps (1/2)

- ❑ A four-variable Boolean function has 16 minterms
- ❑ There are sums of 2, 4, 8, and 16 adjacent squares

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$
$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
$m_8$	$m_9$	$m_{11}$	$m_{10}$

(a)

		$y$				
		$yz$	00	01	11	10
$w$	$x$	00	$m_0$ $w'x'y'z'$	$m_1$ $w'x'y'z$	$m_3$ $w'x'yz$	$m_2$ $w'x'yz'$
	01		$m_4$ $w'xy'z'$	$m_5$ $w'xy'z$	$m_7$ $w'xyz$	$m_6$ $w'xyz'$
	11		$m_{12}$ $wxy'z'$	$m_{13}$ $wxy'z$	$m_{15}$ $wxyz$	$m_{14}$ $wxyz'$
	10		$m_8$ $wx'y'z'$	$m_9$ $wx'y'z$	$m_{11}$ $wx'yz$	$m_{10}$ $wx'yz'$
			$z$			


(b)

# Four-Variable Maps (2/2)

- ❑ Simplification rules of adjacent squares that has 1's in the K-map are as follows
  - a 1-square represents one minterm with four literals
  - a 2-square reduces to a product term with three literals
  - a 4-square reduces to a product term with two literals
  - a 8-square reduces to a product term with one literal
  - a 16-square reduces to a constant 1
- ❑ Note:
  - There are usually more than one ways to simplify a function
  - Overlapping of  $n$ -squares do not affect the rules
- ❑ Goal: find the minimal number of  $n$ -squares that can cover all the 1's in the K-map
 
# Example: Sum of 11 minterms

$\square F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$   
 $\rightarrow F = y' + w'z' + xz'$




Note:  $w'y'z' + w'y'z = w'z'$   
 $w'yz' + w'yz = w'z$   
 $xz' + xz = x$

 Example:  $F = A'B'C' + B'CD' + A'B'CD' + AB'C'$

□  $F \rightarrow B'D' + B'C' + A'CD'$ :

- Four corners:  $A'B'C'D' + A'B'CD' + AB'C'D' + AB'CD' = B'D'$ .
- 4-squares on the left:  $B'C'$ .
- 2-squares on the top-right:  $A'CD'$ .






# Prime Implicants

---

- ❑ A prime Implicant is a product term obtained by combining the maximum possible number of adjacent squares in the map.
  - A subset of a prime implicant is not a prime implicant. E.g., a 2-square contained in a 4-square is not a prime implicant.
- ❑ An essential prime implicant is the only prime implicant that covers certain minterms.
  - At least one of the minterms covered by the essential prime implicant is unique.
- ❑ A function can be simplified to summations of prime implicants.

 
# Example: Prime Implicants

- $F(A, B, C, D) = \Sigma(0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$ .
- $F = BD + B'D' + CD + AD = BD + B'D' + CD + AB'$   
 $= BD + B'D' + B'C + AD = BD + B'D' + B'C + AB'$




Note:  $A'B'C'D' + A'B'CD' = A'B'D'$   
 $AB'C'D' + AB'CD' = AB'D'$   
 $A'B'D' + AB'D' = B'D'$

 (a) Essential prime implicants  
 $BD$  and  $B'D'$



 (b) Prime implicants  $CD$ ,  $B'C$ ,  
 $AD$ , and  $AB'$

- ❑ Map for more than four variables becomes very complicated
- ❑ A possible way to draw five-variable map is to stack two four-variable maps together:



# Product of Sum (PoS) Simplification

- ❑ K-map is designed for sum-of-product simplification
- ❑ To have simplified forms in product-of-sum, you can:

(1) Apply duality principle in K-map:

■  $(x+y')(x+y) = x$


		y	
		0	1
x	0	$M_0$ 0	$M_1$ 0
	1	$M_2$	$M_3$

(2) Start with sum-of-product form, and follow the steps:

- Simplify  $F'$  in the form of sum-of-product
- Apply DeMorgan's theorem  $F = (F')'$  to turn sum-of-product into product-of-sum
 
# Example: PoS Simplification (1/2)


- ❑  $F = \Sigma(0, 1, 2, 5, 8, 9, 10) \rightarrow B'D' + B'C' + A'C'D$
- ❑ To get the simplified PoS form, we can combine zeros in the K-map to get the simplified form of  $F'$ 
  - $F' = AB + CD + BD'$ , then  $F = (A'+B')(C'+D')(B'+D)$




Note:  $BC'D' + BCD' = BD'$

# Example: PoS Simplification (2/2)
 
## □ Gate implementations of the simplified function



(a)  $F = B'D' + B'C' + A'C'D$

 


(b)  $F = (A' + B')(C' + D')(B' + D)$

# Summary Example

- $F = \Sigma(1, 3, 4, 6) = (\Sigma(0, 2, 5, 7))' = \Pi(0, 2, 5, 7)$
- To simplify  $\Sigma(1, 3, 4, 6)$ , we combine 1's:  $F = x'z + xz'$
  - To simplify  $(\Sigma(0, 2, 5, 7))'$ , we combine 0's:  $F' = xz + x'z'$
  - To simplify  $\Pi(0, 2, 5, 7)$ , we complement the function to draw K-map, then complement the simplified form of  $(\Sigma(0, 2, 5, 7))'$

*Truth Table of Function F*

$x$	$y$	$z$	$F$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

# Don't Care Conditions

---

- ❑ The value of a function is not specified for certain combinations of variables
  - In BCD codes; 1010 ~ 1111: don't care
- ❑ The don't care conditions can be utilized in logic minimization
  - can be implemented as 0 or 1



# Example: Don't Care Conditions

□  $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$ ,  $d(w, x, y, z) = \Sigma(0, 2, 5)$

- (a) :  $F = yz + w'x'$ , from  $F = \Sigma(0, 1, 2, 3, 7, 11, 15)$
- (b) :  $F = yz + w'z$ , from  $F = \Sigma(1, 3, 5, 7, 11, 15)$
- Either expression is acceptable

		$y$						
		$\begin{matrix} & 00 & 01 & 11 & 10 \end{matrix}$						
$w$	$w'x'$	$m_0$	$m_1$	$m_3$	$m_2$	$x$	$yz$	
	00	X	1	1	X			
	01	$m_4$	$m_5$	$m_7$	$m_6$			
	11	0	X	1	0			
$w$	10	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$			
	10	0	0	1	0			
		$m_8$	$m_9$	$m_{11}$	$m_{10}$			
		0	0	1	0			

(a)  $F = yz + w'x'$




		$y$						
		$\begin{matrix} & 00 & 01 & 11 & 10 \end{matrix}$						
$w$	$w'z$	$m_0$	$m_1$	$m_3$	$m_2$	$x$	$yz$	
	00	X	1	1	X			
	01	$m_4$	$m_5$	$m_7$	$m_6$			
	11	0	X	1	0			
$w$	10	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$			
	10	0	0	1	0			
		$m_8$	$m_9$	$m_{11}$	$m_{10}$			
		0	0	1	0			

(b)  $F = yz + w'z$


# NAND and NOR Implementation
   
## □ NAND gate is a universal gate


- An universal gate can implement any digital system



## □ Two symbols for a NAND gate:

 


(a) AND-invert

 


(b) Invert-OR
 
# Two-level Implementation of Func.


- ❑ Use two-level logic to implement  $F = AB + CD$ 
  - Sum of products can be implemented by NAND-NAND logic
  - $F = AB + CD = ((AB)'(CD)')'$



(a)

 




(b)

 

(c)
   
# Example: NAND Implementation

□  $F(x, y, z) = \Sigma(1, 2, 3, 4, 5, 7) = xy' + x'y + z,$




# NAND Implementation Procedure

---


- ❑ To implement a function using NAND gates alone, execute the following procedure
  - Simplified in the form of sum of products
  - A NAND gate for each product term;  
the inputs to each NAND gate are the literals of the term
  - A single NAND gate for the second sum term
  - A single literal requires an inverter in the first level
 
# Multilevel NAND Circuits

- ❑ Steps to convert AND-OR logic implementations to NAND-NAND logic implementations
  - AND  $\rightarrow$  NAND + inverter-to-next-input
  - OR  $\rightarrow$  inverted-input + OR ( $\equiv$  NAND)




(a) AND-OR gates

 


(b) NAND gates

# NAND Implementation

$$\square F = (AB' + A'B)(C + D')$$

 


(a) AND-OR gates

 


(b) NAND gates
 
# NOR Implementation


- ❑ NOR function is the dual of NAND function
  - The NOR gate is also universal



- ❑ Two symbols for a NOR gate:

 

(a) OR-invert

 


(b) Invert-AND


 
# Multilevel NOR Circuits

- ❑ Steps to convert AND-OR logic to NOR-NOR logic
  - AND  $\rightarrow$  inverted-input + AND ( $\equiv$  NOR)
  - OR  $\rightarrow$  NOR
  
- ❑ Example:  $F = (AB' + A'B)(C + D')$



# Other Two-level Implementations

---


- ❑ Two-level function implementation is the basic of digital computing, we have studied AND-OR, OR-AND, NAND-NAND, and NOR-NOR
- ❑ There are other possibilities of two-level implementations
  - Wired logic
  - Non-degenerate forms of NOR-OR, NAND-AND, OR-AND, and AND-OR

# Wired Logic Implementation


❑ Some gates can use a wire connection of the outputs to “*emulate an extra 2nd-level gate*”

❑ Examples:

 - wire TTL NAND gates gives us wired-AND logic  
→ AND-OR-INVERT function:  $F = (AB)'(CD)'$
- wire ECL NOR gates gives us wired-OR logic  
→ OR-AND-INVERT function  $F = (A+B)' + (C+D)'$



 (a) Wired-AND in open-collector  
TTL NAND gates.



(b) Wired-OR in ECL gates

# Non-degenerate Forms


- ❑ If four types of gates, AND, OR, NAND, NOR, are used for two-level logics, there are 16 combinations
- ❑ Eight of them are degenerate forms, i.e., equivalent to a single-level logic of multiple inputs
  - Examples: AND-AND  $\rightarrow$  AND; OR-NOR  $\rightarrow$  NOR
- ❑ The other eight non-degenerate forms are:
  - AND-OR, OR-AND, NAND-NAND, NOR-NOR, NAND-AND, AND-NOR, OR-AND, NOR-OR
- ❑ Popular forms:
  - AND-OR and NAND-NAND = sum of products
  - OR-AND and NOR-NOR = product of sums

# AND-OR-INVERT Circuits


## □ AND-OR-INVERT (AOI) Implementation

■ AND-NOR = NAND-AND


■  $F = (AB + CD + E)'$

 

(a) AND-NOR

 

(b) AND-NOR

 


(c) NAND-AND

# OR-AND-INVERT Circuits


## ❑ OR-AND-INVERT (OAI) Implementation

- OR-NAND = NOR-OR


- $F = ((A+B)(C+D)E)'$

 

(a) OR-NAND

 

(b) OR-NAND

 

(c) NOR-OR

# Summary of Two-Level Forms

## ❑ Implementation with other two-level forms:

### *Implementation with Other Two-Level Forms*

Equivalent Nondegenerate Form		Implements the Function	Simplify $F'$ into	To Get an Output of
(a)	(b)*			
AND-NOR	NAND-AND	AND-OR-INVERT	Sum-of-products form by combining 0's in the map.	$F$
OR-NAND	NOR-OR	OR-AND-INVERT	Product-of-sums form by combining 1's in the map and then complementing.	$F$

\*Form (b) requires an inverter for a single literal term.

## Example: $F = x'y'z' + xyz'$ (1/2)

- ❑ Compliment of the function is  $F' = (x+y+z)(x'+y'+z)$ 
  - OAI expression:  $((x+y+z)(x'+y'+z))'$
- ❑ K-map of the function:

		$y$			
		00	01	11	10
$x \backslash yz$	0	$m_0$ 1	$m_1$ 0	$m_3$ 0	$m_2$ 0
	1	$m_4$ 0	$m_5$ 0	$m_7$ 0	$m_6$ 1

Annotations:  $x'y'z'$  points to  $m_0$ ;  $x$  { 1 points to the row  $x=1$ ;  $xyz'$  points to  $m_6$ ;  $z$  { 1 points to the column  $z=1$  (columns 01 and 11).



- ❑ Complement of the simplified form is  $F' = x'y + xy' + z$ 
  - $F'$  is simplified by combining zeros in K-map
  - AOI expression:  $F = (x'y + xy' + z)'$





# Example: $F = x'y'z' + xyz'$ (2/2)

## □ Gate Implementations:

■ OAI:  $F = ((x+y+z)(x'+y'+z))'$

  

■ AOI:  $F = (x'y + xy' + z)'$

  


# Exclusive-OR Function


- ❑ Exclusive-OR (XOR):  $x \oplus y = xy' + x'y$
- ❑ Exclusive-NOR (XNOR):  $(x \oplus y)' = xy + x'y'$
- ❑ Some identities:
  - $x \oplus 0 = x$
  - $x \oplus 1 = x'$
  - $x \oplus x = 0$
  - $x \oplus x' = 1$
  - $x \oplus y' = x' \oplus y = (x \oplus y)'$
- ❑ Commutative and associative
  - $A \oplus B = B \oplus A$
  - $(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$
 
# Implementations

$$\square x \oplus y = xy' + x'y = (x' + y')x + (x' + y')y$$



(a) Exclusive-OR with AND-OR-NOT gates

 

(b) Exclusive-OR with NAND gates

# Odd Function


- ❑ Exclusive-OR can be used to determine whether the number of 1's is odd
- ❑ Example:  $A \oplus B \oplus C = (AB' + A'B)C' + (AB + A'B')C$   
 $= AB'C' + A'BC' + ABC + A'B'C = \Sigma(1, 2, 4, 7)$

$A \backslash BC$		$B$			
		00	01	11	10
$A$	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$
			1		1
		1		1	


(a) Odd function  $F = A \oplus B \oplus C$

$A \backslash BC$		$B$			
		00	01	11	10
$A$	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$
		1		1	
			1		1

 (b) Even function  $F = (A \oplus B \oplus C)'$



(a) 3-input odd function

 


(b) 3-input even function


# Parity Generation and Checking
 
## ❑ XOR can be used for parity generation and checking

- Parity bit of three variables:  $P = x \oplus y \oplus z$
- Parity check function:  $C = x \oplus y \oplus z \oplus P$ , if even parity is used
  - $C = 1$ : an odd number of data bit error
  - $C = 0$ : correct or an even number of data bit error



(a) 3-bit even parity generator

 

(b) 4-bit even parity checker