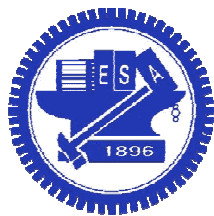


Combinational Circuits




Chun-Jen Tsai
National Chiao Tung University
10/22/2012

Logic Circuits for Digital Systems

- ❑ Logic circuits for digital systems may be combinational or sequential.
- ❑ A combinational circuit consists of logic gates whose outputs at any time are determined from only the current inputs.
- ❑ A sequential circuit contains small memory elements
 - the outputs are a function of the current inputs and the state of the memory elements
 - The memory elements imply that the outputs also depend on past inputs, not just current inputs

Combinational Circuit

 - A combinational circuits
 - 2^n possible combinations of input values



- Specific functions
 - Adders, subtractors, comparators, decoders, encoders, and multiplexers
 - MSI circuits or standard cells

Analysis of Combinational Circuits

- ❑ In general, given a logic diagram, we must perform some analysis to understand the function it implements:
- ❑ Steps of analysis:
 - Make sure that the logic is combinational, not sequential
 - No feedback path or memory elements
 - Label inputs, intermediate gate outputs, and the final outputs
 - Derive its Boolean functions (truth table)
 - A verbal explanation of its function

Example: Analysis of a Circuit (1/2)

□ The following logic diagram has three inputs, A , B , C , and two outputs:


■ $F_2 = AB + AC + BC$

■ $T_1 = A + B + C$

■ $T_2 = ABC$

■ $T_3 = F_2' T_1$

■ $F_1 = T_3 + T_2$

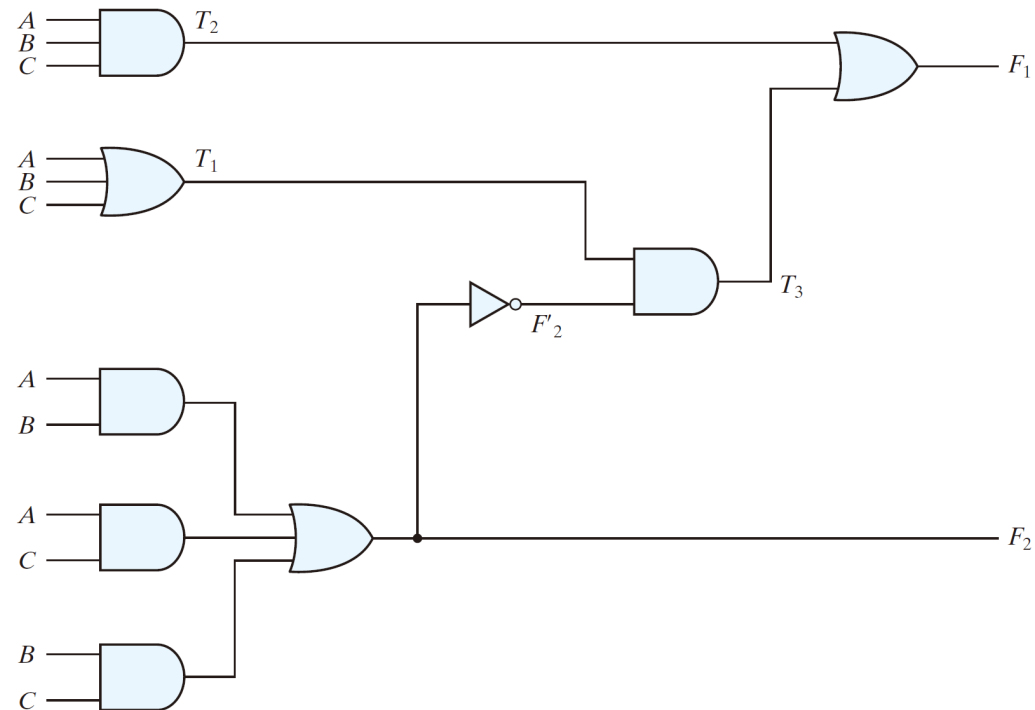

Example: Analysis of a Circuit (2/2)

□ Put the function in canonical form:

$$\begin{aligned} \blacksquare F_1 &= T_3 + T_2 = F_2' T_1 + ABC \\ &= (AB + AC + BC)'(A + B + C) + ABC \\ &= (A' + B')(A' + C')(B' + C')(A + B + C) + ABC \\ &= (A' + B'C')(AB' + AC' + BC' + B'C) + ABC \\ &= A'BC' + A'B'C + AB'C' + ABC \end{aligned}$$

□ The function is a full adder

- F_1 is the sum
- F_2 is the carry

| A | B | C | F_2 | F_2' | T_1 | T_2 | T_3 | F_1 |
|---|---|---|-------|--------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |

Design of Combinational Circuits

- ❑ The design procedure of combinational circuits
 - State the function behavior (system specification)
 - Determine the inputs and outputs
 - The input and output variables are assigned symbols
 - Derive the truth table
 - Derive the simplified Boolean functions
 - Draw the logic diagram and verify the correctness

Design Implementation

- ❑ Today, Electronic Design Automation (EDA) tools are used for design implementation.
 - EDA tools take functional description (expressed in HDL codes or schematic diagrams) and design constraints as input, and generate a “netlist” as output.
- ❑ Considerations for Logic minimization:
 - Number of gates
 - Number of inputs to a gate
 - Propagation delay
 - Number of interconnection
 - Limitations of the driving capabilities

Code Conversion (1/4)

- ❑ Design a circuit to convert from BCD to excess-3 codes
- ❑ System specification:

| Input BCD | | | | Output Excess-3 Code | | | |
|-----------|----------|----------|----------|----------------------|----------|----------|----------|
| <i>A</i> | <i>B</i> | <i>C</i> | <i>D</i> | <i>w</i> | <i>x</i> | <i>y</i> | <i>z</i> |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 |

Code Conversion (2/4)

□ K-maps:

| | | C | | | | |
|-----|------|---------------|---------------|---------------|---------------|------------|
| | | CD | 00 | 01 | 11 | 10 |
| A | AB | 00 | m_0 1 | m_1 | m_3 | m_2 1 |
| | 01 | m_4 1 | m_5 | m_7 | m_6 1 | |
| | 11 | m_{12} X | m_{13} X | m_{15} X | m_{14} X | |
| | 10 | m_8 1 | m_9 | m_{11} X | m_{10} X | |

$z = D'$

| | | C | | | | |
|-----|------|---------------|---------------|---------------|---------------|-------|
| | | CD | 00 | 01 | 11 | 10 |
| A | AB | 00 | m_0 1 | m_1 | m_3 1 | m_2 |
| | 01 | m_4 1 | m_5 | m_7 1 | m_6 | |
| | 11 | m_{12} X | m_{13} X | m_{15} X | m_{14} X | |
| | 10 | m_8 1 | m_9 | m_{11} X | m_{10} X | |

$y = CD + C'D'$

| | | C | | | | |
|-----|------|---------------|---------------|---------------|---------------|------------|
| | | CD | 00 | 01 | 11 | 10 |
| A | AB | 00 | m_0 | m_1 1 | m_3 1 | m_2 1 |
| | 01 | m_4 1 | m_5 | m_7 | m_6 1 | |
| | 11 | m_{12} X | m_{13} X | m_{15} X | m_{14} X | |
| | 10 | m_8 | m_9 1 | m_{11} X | m_{10} X | |

$x = B'C + B'D + BC'D'$

| | | C | | | | |
|-----|------|----------|----------|----------|----------|-------|
| | | CD | 00 | 01 | 11 | 10 |
| A | AB | 00 | m_0 | m_1 | m_3 | m_2 |
| | 01 | m_4 | m_5 | m_7 | m_6 | |
| | 11 | m_{12} | m_{13} | m_{15} | m_{14} | |
| | 10 | m_8 | m_9 | m_{11} | m_{10} | |

00

01

11

10

1

1

1

X

X

X

X

1

1

X

X

$w = A + BC + BD$

Code Conversion (3/4)

□ The simplified functions

- $z = D'$

$$y = CD + C'D'$$

$$x = B'C + B'D + BC'D'$$

$$w = A + BC + BD$$

□ Another implementation

- $z = D'$


$$y = CD + C'D' = CD + (C + D)'$$

$$x = B'C + B'D + BC'D' = B'(C + D) + B(C + D)'$$

$$w = A + BC + BD$$

Code Conversion (4/4)

□ The logic diagram:

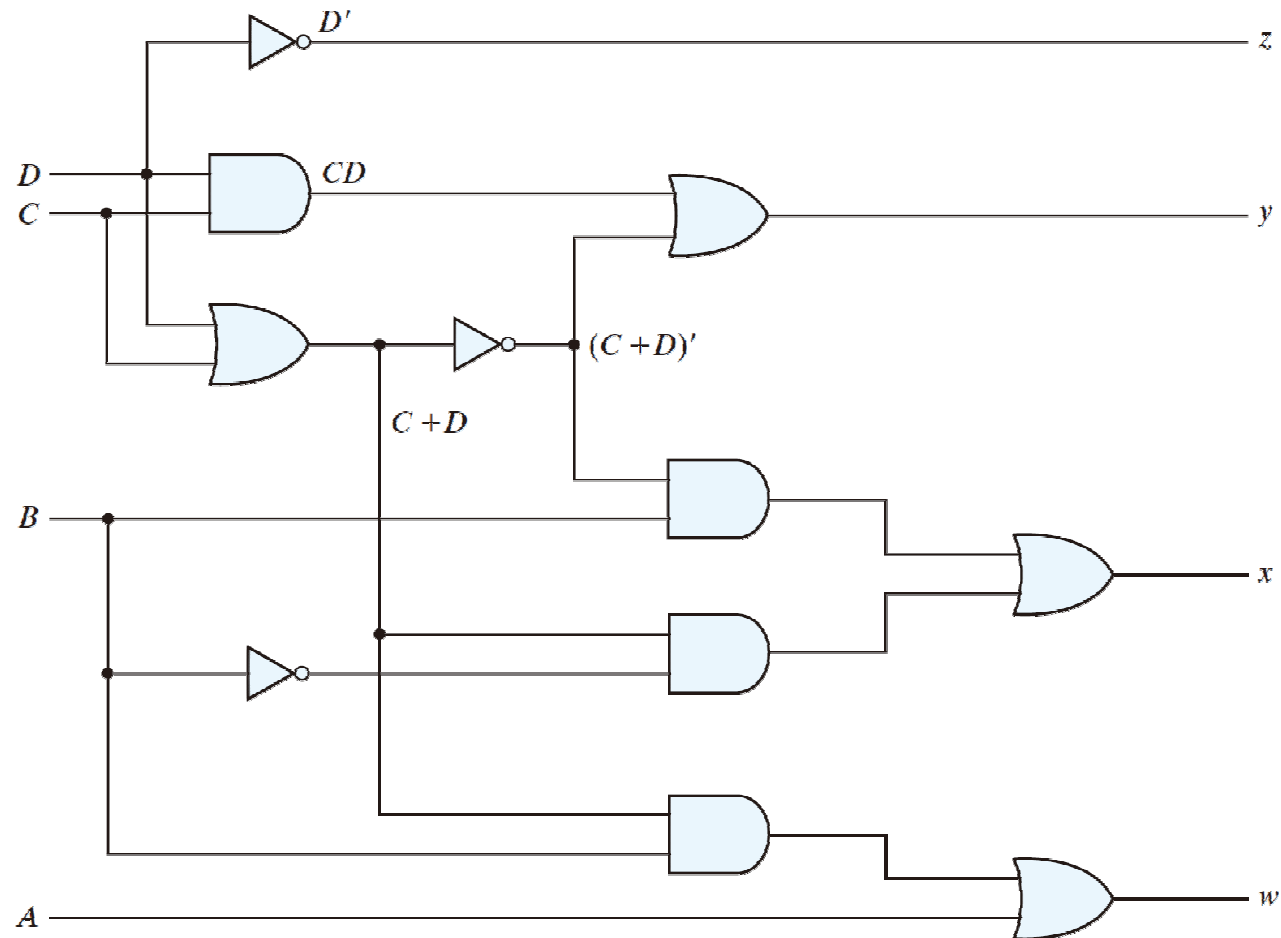

One-bit Half-Adder (1/2)

□ The behavior of a 1-bit half-adder is as follows:

- Input variables: x and y
- Output variables: Sum (S) and carry (C)
- Truth table:

Half Adder


| x | y | C | S |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

■ Boolean functions:


- $S = x'y + xy' = x \oplus y$
- $C = xy$

One-bit Half-Adder (2/2)

□ Gate-level implementation:

 
 
$$\begin{aligned} \text{(a) } S &= xy' + x'y \\ C &= xy \end{aligned}$$



$$\begin{aligned} \text{(b) } S &= x \oplus y \\ C &= xy \end{aligned}$$

□ Alternative implementations:

- $S = (x + y)(x' + y')$
- $S' = xy + x'y' \rightarrow S = (C + x'y')'$
- $C = xy = (x' + y')'$


One-bit Full-Adder (1/3)

□ The behavior of a 1-bit full-adder is as follows:


- Input variables: x , y , and z (carry from previous bit)
- Output variables: Sum (S) and carry (C)
- Truth table:
- K-maps:

Full Adder

| x | y | z | C | S |
|-----|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

 

$$(a) S = x'y'z + x'yz' + xy'z' + xyz$$

 



$$(b) C = xy + xz + yz$$

One-bit Full-Adder (2/3)

□ Gate-level implementation:

- $S = x'y'z + x'yz' + xy'z' + xyz$


- $C = xy + xz + yz$

  

One-bit Full-Adder (3/3)

□ We can use two 1-bit half-adders to construct a 1-bit full adder:

 
- $S = (x'y'z' + xy'z') + (x'y'z + xyz) = (x \oplus y)z' + (x \oplus y)'z = (x \oplus y) \oplus z$
- $C = xy + xz + yz = xy + (x + y)z = xy + (x \oplus y)z$



Binary Adder


- The behavior of a 4-bit binary adder

| Subscript i : | 3 | 2 | 1 | 0 | |
|-----------------|---|---|---|---|-----------|
| Input carry | 0 | 1 | 1 | 0 | C_i |
| Augend | 1 | 0 | 1 | 1 | A_i |
| Addend | 0 | 0 | 1 | 1 | B_i |
| Sum | 1 | 1 | 1 | 0 | S_i |
| Output carry | 0 | 0 | 1 | 1 | C_{i+1} |

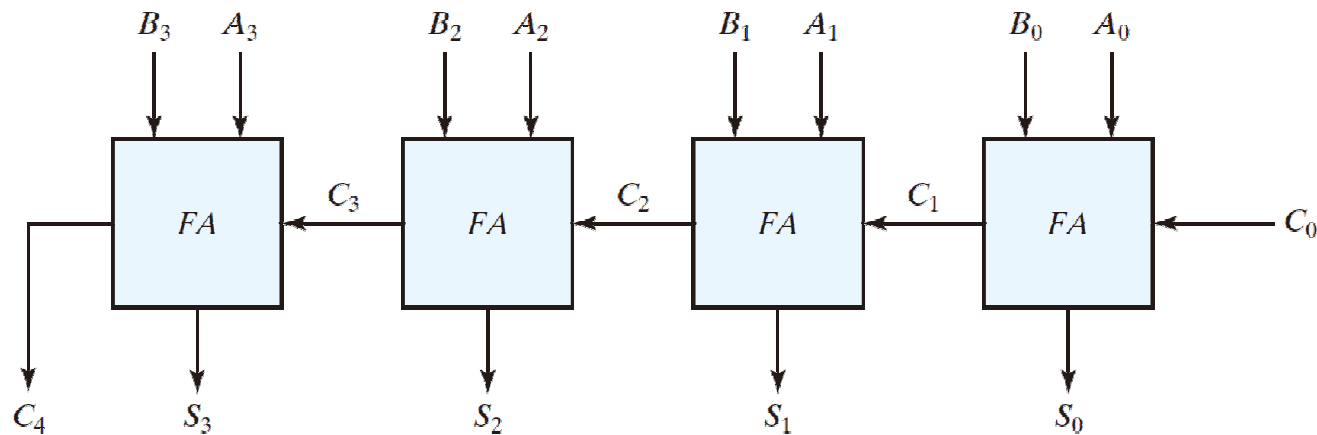

Carry Propagation of Adders

 - ❑ The carry propagation problem:
 - when the correct outputs are available
 - the critical path counts (the worst case)
 - $(A_1, B_1, C_1) > C_2 > C_3 > C_4 > (C_5, S_4)$
 - The propagation delay is 8 gate levels for a 4-bit adder




Reduction of Propagation Delay

- ❑ To reduce the carry propagation delay, we can
 - Employ faster gates
 - Use look-ahead carry logic (more complex)
- ❑ Look-ahead carry generation:
 - Define two new variables:
 - Carry propagate $P_i = A_i \oplus B_i$
 - Carry generate $G_i = A_i B_i$
 - Now, sum $S_i = P_i \oplus C_i$
 - Carry: $C_{i+1} = G_i + P_i C_i$
 - $C_1 = G_0 + P_0 C_0$
 - $C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$
 - $C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$

Look-Ahead Carry Generator


❑ Logic diagram:

 

Carry-Look Ahead Adder

□ Three-level logic diagram:

 - $P_i = A_i \oplus B_i$
- Carry generation
- $S_i = P_i \oplus C_i$



- Boolean expression:
 - If $M = 0$, $A + B$; if $M = 1$, $A + B' + 1$



Binary Subtractor (2/2)

- ❑ Since our adder has finite bits, we must perform overflow detection:
 - Add two positive numbers and obtain a negative number
 - Add two negative numbers and obtain a positive number
- ❑ Overflow detection rule:
 - If $V = 0$, no overflow; $V = 1$, overflow
- ❑ Examples:

| | |
|----------|-----------|
| carries: | 0 1 |
| +70 | 0 1000110 |
| +80 | 0 1010000 |
| <hr/> | <hr/> |
| +150 | 1 0010110 |

| | |
|----------|-----------|
| carries: | 1 0 |
| -70 | 1 0111010 |
| -80 | 1 0110000 |
| <hr/> | <hr/> |
| -150 | 0 1101010 |

Decimal Adder (1/3)

- ❑ A BCD adder adds two BCD numbers:
 - 9 inputs: two BCD codes and one carry-in
 - 5 outputs: one BCD code and one carry-out
- ❑ The truth table has 2^9 entries, too large for efficient implementation
- ❑ Question: can we use binary full adders to implement BCD adders?
 - The sum of any two digits $\leq 9 + 9 + 1 = 19$
 - After binary addition, we perform binary to BCD conversion

Decimal Adder (2/3)

- Binary-to-BCD conversion of numbers ≤ 19


Derivation of BCD Adder

| Binary Sum | | | | | BCD Sum | | | | | Decimal |
|------------|----------------------|----------------------|----------------------|----------------------|----------|----------------------|----------------------|----------------------|----------------------|---------|
| <i>K</i> | <i>Z₈</i> | <i>Z₄</i> | <i>Z₂</i> | <i>Z₁</i> | <i>C</i> | <i>S₈</i> | <i>S₄</i> | <i>S₂</i> | <i>S₁</i> | |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 2 |
| 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 3 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 4 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 5 |
| 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 6 |
| 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 7 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 8 |
| 0 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 9 |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 10 |
| 0 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 11 |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 12 |
| 0 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 13 |
| 0 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 14 |
| 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 15 |
| 1 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 16 |
| 1 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 17 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 18 |
| 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 19 |

Decimal Adder (3/3)

- ❑ Conversion is needed if the sum > 9
 - The carry of BCD sum $C = 1$ if $K = 1$ or $Z_8Z_4 = 1$ or $Z_8Z_2 = 1$
 $\rightarrow C = K + Z_8Z_4 + Z_8Z_2$
 - If $C = 1$, modify the binary sum by $-(10)_d$ or $+6$

❑ Block diagram:

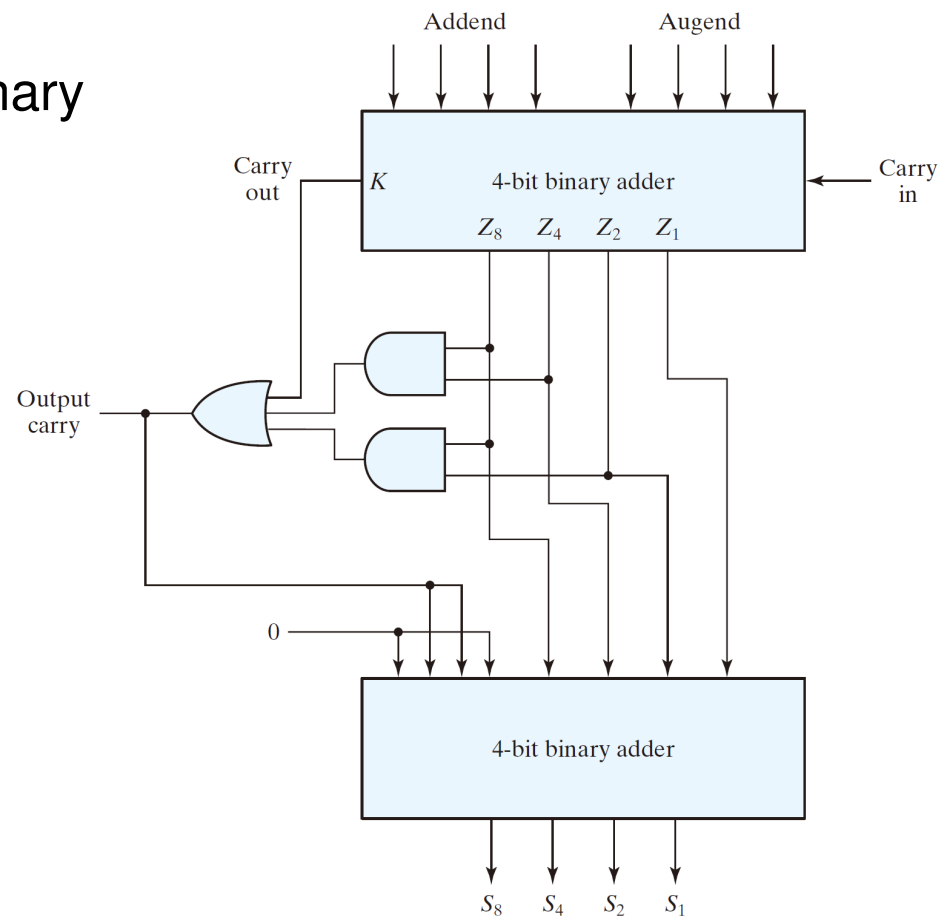


Binary Multiplier (1/2)

□ Two-bit multiplier for $(B_1B_0) \times (A_1A_0)$:


- $C_0 = A_0B_0$
- $C_1 = A_0B_1 \oplus A_1B_0$
- $C_2 = A_1B_1 \oplus (A_0B_1)(A_1B_0)$
- $C_3 = (A_1B_1)(A_0B_1)(A_1B_0)$

| | | | |
|-------|----------|----------|-------|
| | | B_1 | B_0 |
| | A_1 | A_0 | |
| | A_0B_1 | A_0B_0 | |
| | A_1B_1 | A_1B_0 | |
| C_3 | C_2 | C_1 | C_0 |

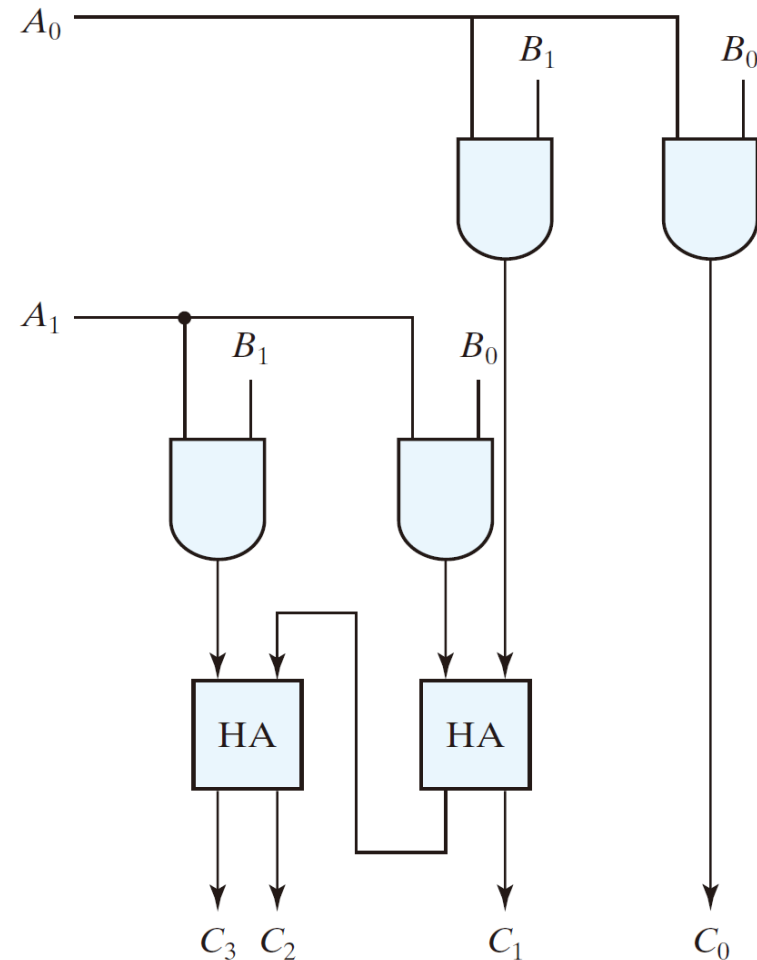

Binary Multiplier (2/2)

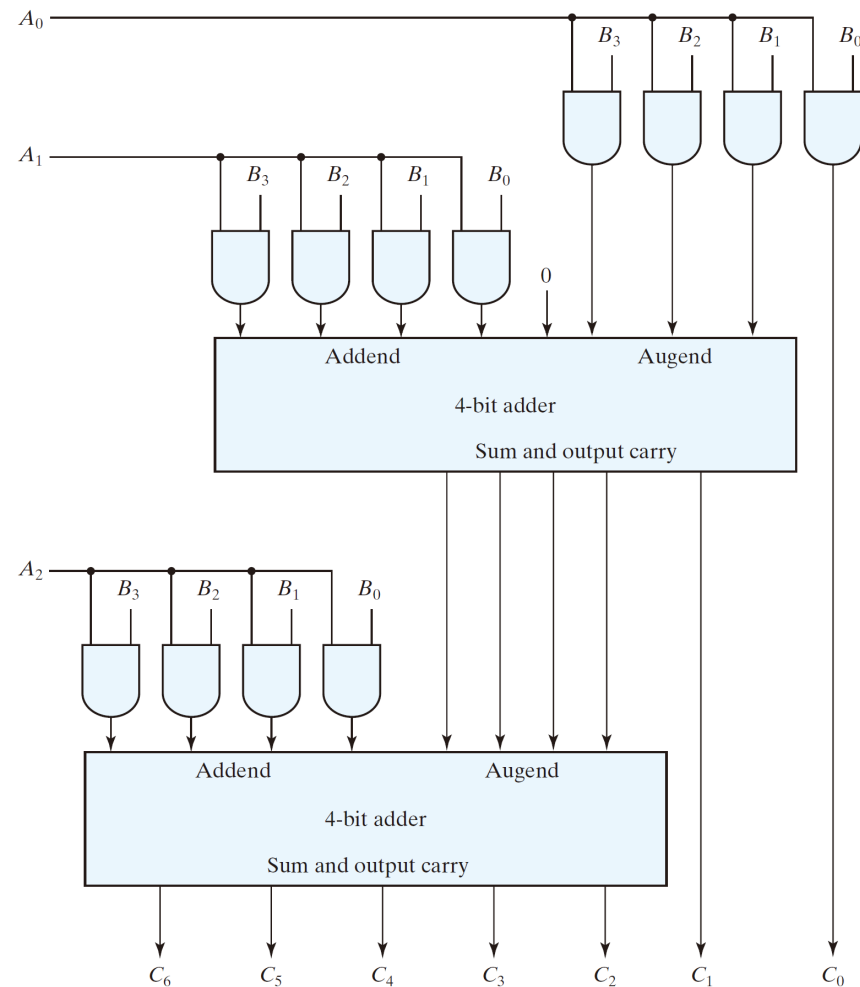❑ 4-bit by 3-bit multiplier for $(B_3B_2B_1B_0) \times (A_2A_1A_0)$:



Magnitude Comparator (1/2)

❑ Using the truth table to implement an n -bit number comparator requires 2^{2n} entries – too large.

❑ Functions of comparing

$$A = A_3A_2A_1A_0 \text{ and } B = B_3B_2B_1B_0$$


■ $F_{A=B} = x_3x_2x_1x_0$, where $x_i = (A_i'B_i + A_iB_i')$, for $i = 0, 1, 2, 3$.

■ $F_{A>B} = A_3B_3' + x_3A_2B_2' + x_3x_2A_1B_1' + x_3x_2x_1A_0B_0'$

■ $F_{A<B} = A_3'B_3 + x_3A_2'B_2 + x_3x_2A_1'B_1 + x_3x_2x_1A_0'B_0$

Magnitude Comparator (2/2)

❑ Logic diagram:

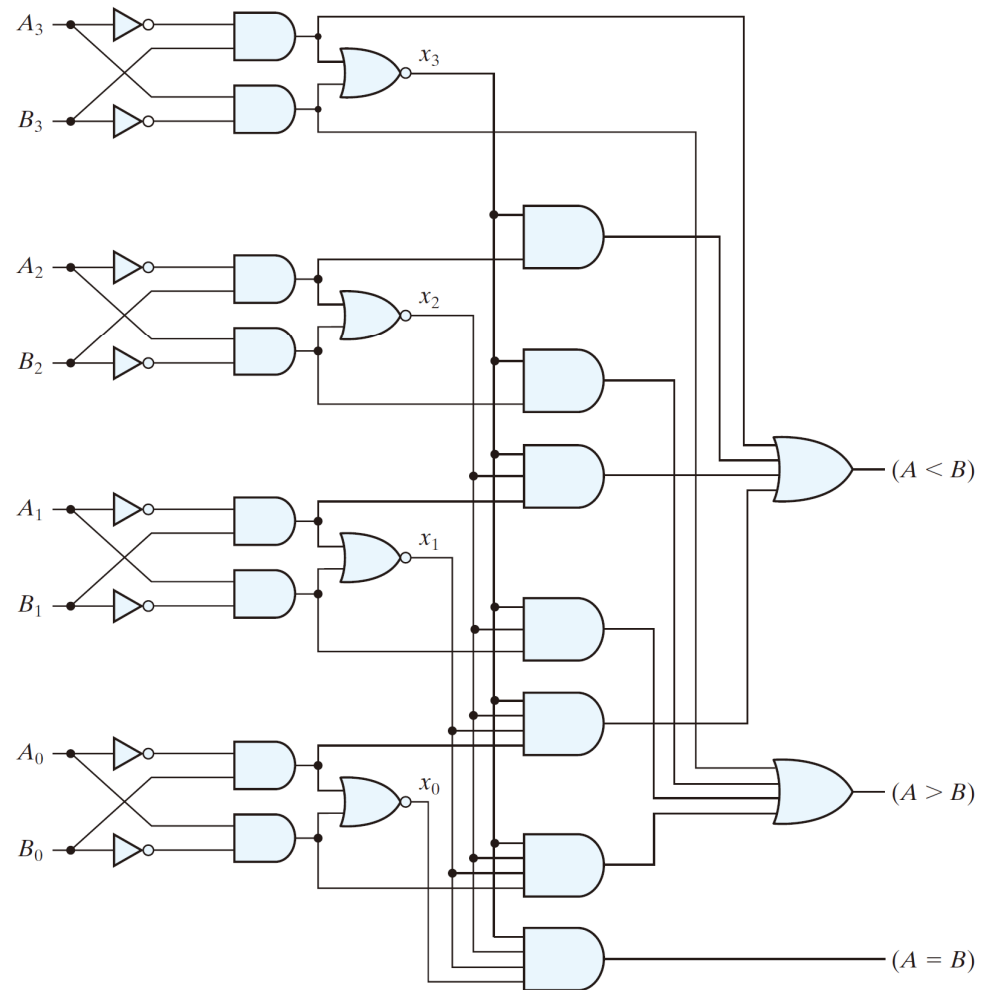

Decoder (1/2)


- ❑ An n -to- m decoder selects a particular output line give an input binary codeword:
 - an input binary code of n bits has 2^n possible output lines
 - only one output can be active (high) at any time
- ❑ Example: a 3-to-8 decoder

Truth Table of a Three-to-Eight-Line Decoder

| Inputs | | | Outputs | | | | | | | |
|--------|-----|-----|---------|-------|-------|-------|-------|-------|-------|-------|
| x | y | z | D_0 | D_1 | D_2 | D_3 | D_4 | D_5 | D_6 | D_7 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |


Decoder (2/2)

❑ Logic diagram:

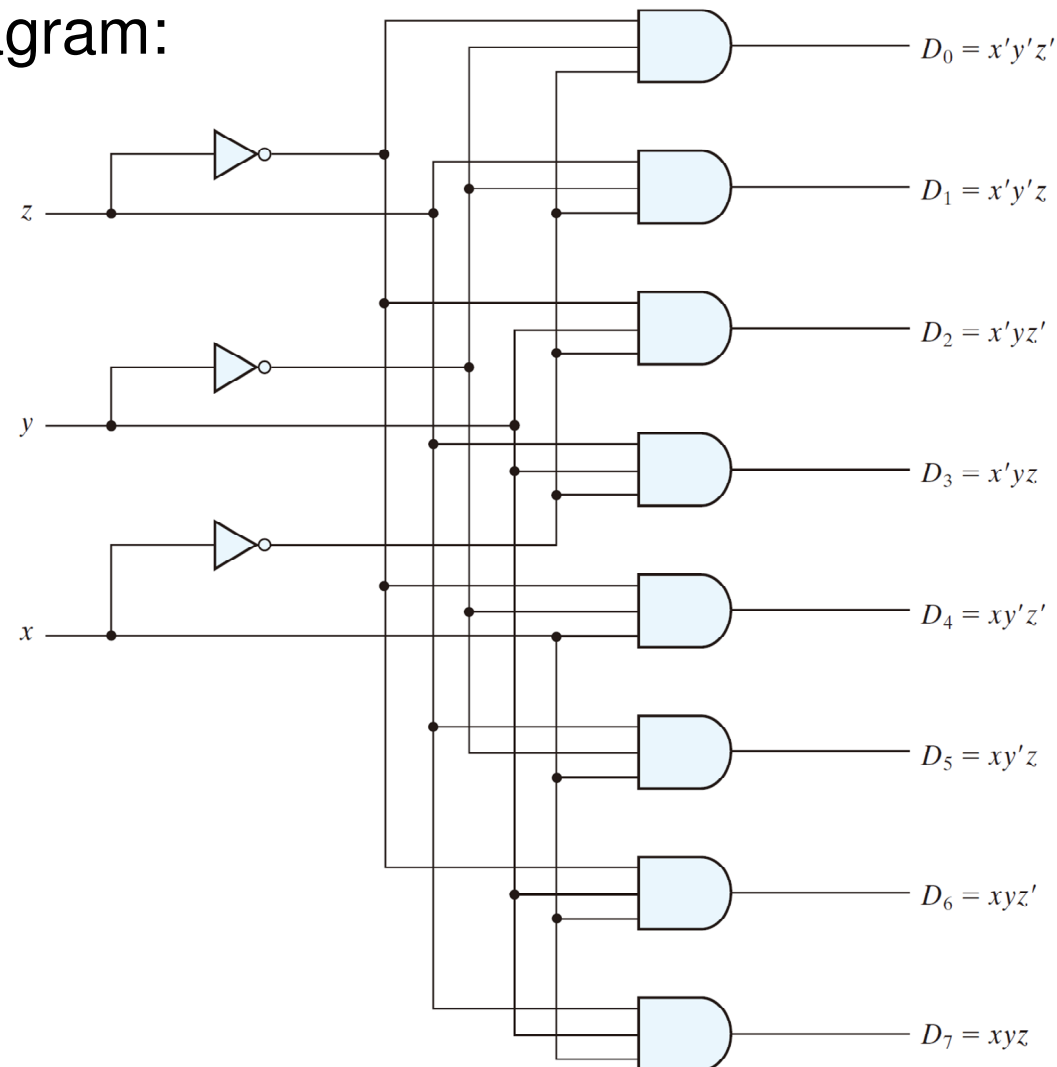

Decoder Implementation with NAND

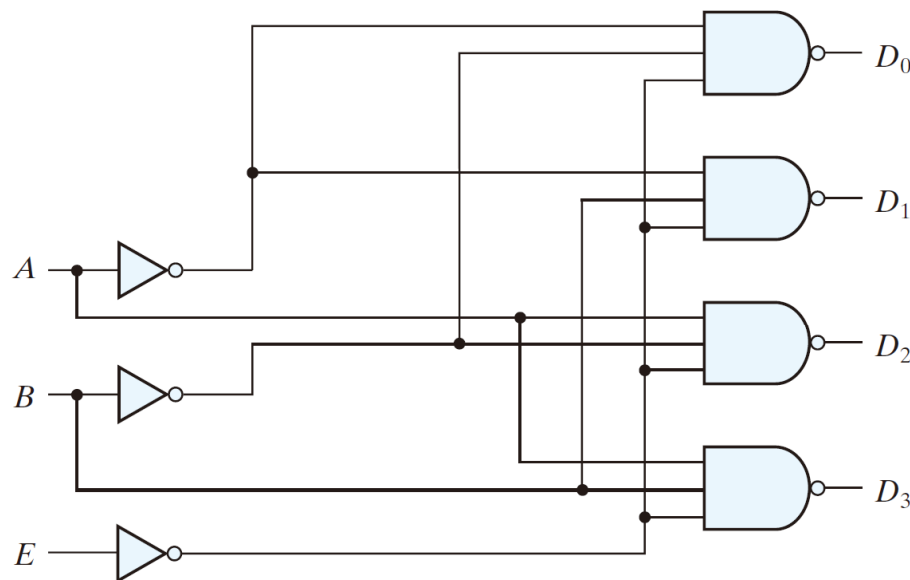- ❑ If NAND gates are used to implement a decoder, it is more efficient to use “active-low” logic
- ❑ Example: a 2-to-4 decoder with an enable input




(a) Logic diagram

| E | A | B | D_0 | D_1 | D_2 | D_3 |
|-----|-----|-----|-------|-------|-------|-------|
| 1 | X | X | 1 | 1 | 1 | 1 |
| 0 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 1 | 1 |

 (b) Truth table


Demultiplexers

- ❑ A demultiplexor (demux) is a decoder with an enable input line



Decoder Extension

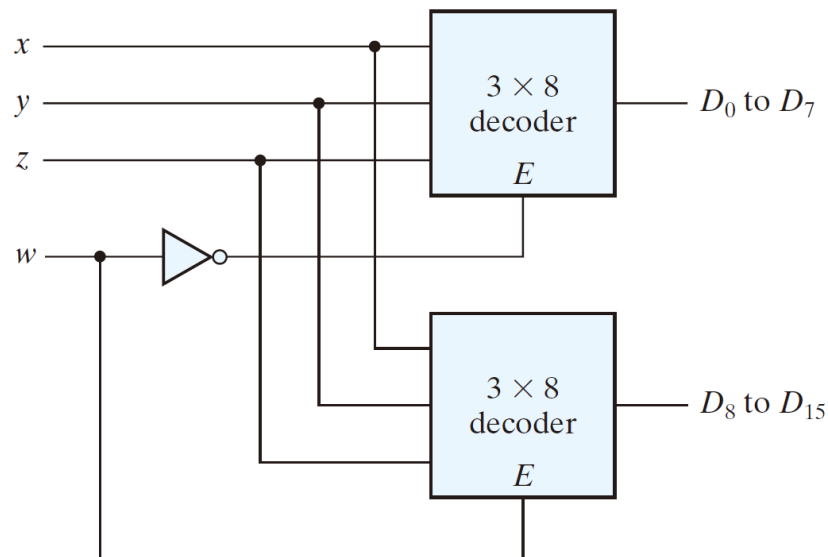- ❑ Large decoders can be constructed using smaller decoders with enable inputs.
- ❑ A 4×16 decoder constructed with two 3×8 decoders:




Combinational Logic Implementation

- ❑ A decoder can implement any combinational logics
 - Each output of the decoder represents a selected minterm
 - A function is implemented by summing all its minterms using an OR gate at the output of the decoder
 - For an n -input, m -output function, we need an $n \times 2^n$ deocder and m OR gates (each one has multiple inputs that corresponds to the number of minterms for each outputs)
- ❑ To reduce the number of inputs to OR gates, we can use NOR to combine the minterms of F'
 - If there are k minterms in F , there are $2^n - k$ minterms in F' .
- ❑ In general, it is not a practical implementation

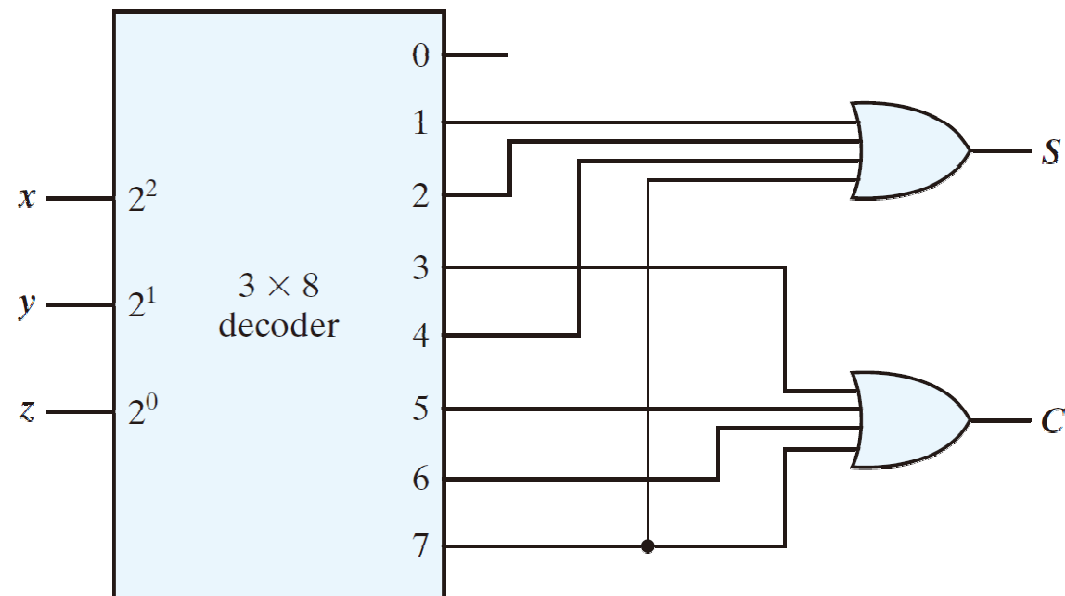Example: A Full Adder

□ Implementing a 1-bit full adder using a decoder:

- $S(x, y, z) = \Sigma(1, 2, 4, 7)$
- $C(x, y, z) = \Sigma(3, 5, 6, 7)$



Encoder

- ❑ Encoder is the inverse function of a decoder
- ❑ Example: octal-to-binary encoder

| Inputs | | | | | | | | Outputs | | |
|--------|-------|-------|-------|-------|-------|-------|-------|---------|-----|-----|
| D_0 | D_1 | D_2 | D_3 | D_4 | D_5 | D_6 | D_7 | x | y | z |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |

- Boolean functions:

$$X = D_4 + D_5 + D_6 + D_7, Y = D_2 + D_3 + D_6 + D_7, Z = D_1 + D_3 + D_5 + D_7$$

Priority Encoder (1/3)

- ❑ A priority encoder is an encoder that applies some priority policy to generate the output when multiple inputs are active simultaneously
- ❑ Example:

| Inputs | | | | Outputs | | |
|--------|-------|-------|-------|---------|-----|-----|
| D_0 | D_1 | D_2 | D_3 | x | y | V |
| 0 | 0 | 0 | 0 | X | X | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| X | 1 | 0 | 0 | 0 | 1 | 1 |
| X | X | 1 | 0 | 1 | 0 | 1 |
| X | X | X | 1 | 1 | 1 | 1 |

- D_3 has the highest priority
- D_0 has the lowest priority
- X: don't-care conditions
- V: valid output indicator

Priority Encoder (2/3)

□ The K-maps of the priority encoder:

| D_0D_1 \ D_2D_3 | | D_2 | | | |
|---------------------|----|------------|---------------|---------------|---------------|
| | | 00 | 01 | 11 | 10 |
| D_0 | 00 | m_0 X | m_1 1 | m_3 1 | m_2 1 |
| | 01 | m_4 | m_5 1 | m_7 1 | m_6 1 |
| | 11 | m_{12} | m_{13} 1 | m_{15} 1 | m_{14} 1 |
| | 10 | m_8 | m_9 1 | m_{11} 1 | m_{10} X |
| | | D_3 | | | |

$$x = D_2 + D_3$$


| D_0D_1 \ D_2D_3 | | D_2 | | | |
|---------------------|----|---------------|---------------|---------------|----------|
| | | 00 | 01 | 11 | 10 |
| D_0 | 00 | m_0 X | m_1 1 | m_3 1 | m_2 |
| | 01 | m_4 1 | m_5 1 | m_7 1 | m_6 |
| | 11 | m_{12} 1 | m_{13} 1 | m_{15} 1 | m_{14} |
| | 10 | m_8 | m_9 1 | m_{11} 1 | m_{10} |
| | | D_3 | | | |

$$y = D_3 + D_1D'_2$$

Priority Encoder (3/3)


□ Logic diagram:

 - $x = D_2 + D_3$
- $y = D_3 + D_1 D_2'$
- $V = D_0 + D_1 + D_2 + D_3$




Multiplexers

 - ❑ A multiplexor (mux) selects binary information from one of input lines and direct it to a single output line
- ❑ There are 2^n input lines, n selection lines and one output line
- ❑ Example: 2-to-1-line multiplexer




(a) Logic diagram

 

(b) Block diagram

4-to-1-line Multiplexer

❑ Logic diagram of a 4×1 multiplexor:

 


(a) Logic diagram

| S_1 | S_0 | Y |
|-------|-------|-------|
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |

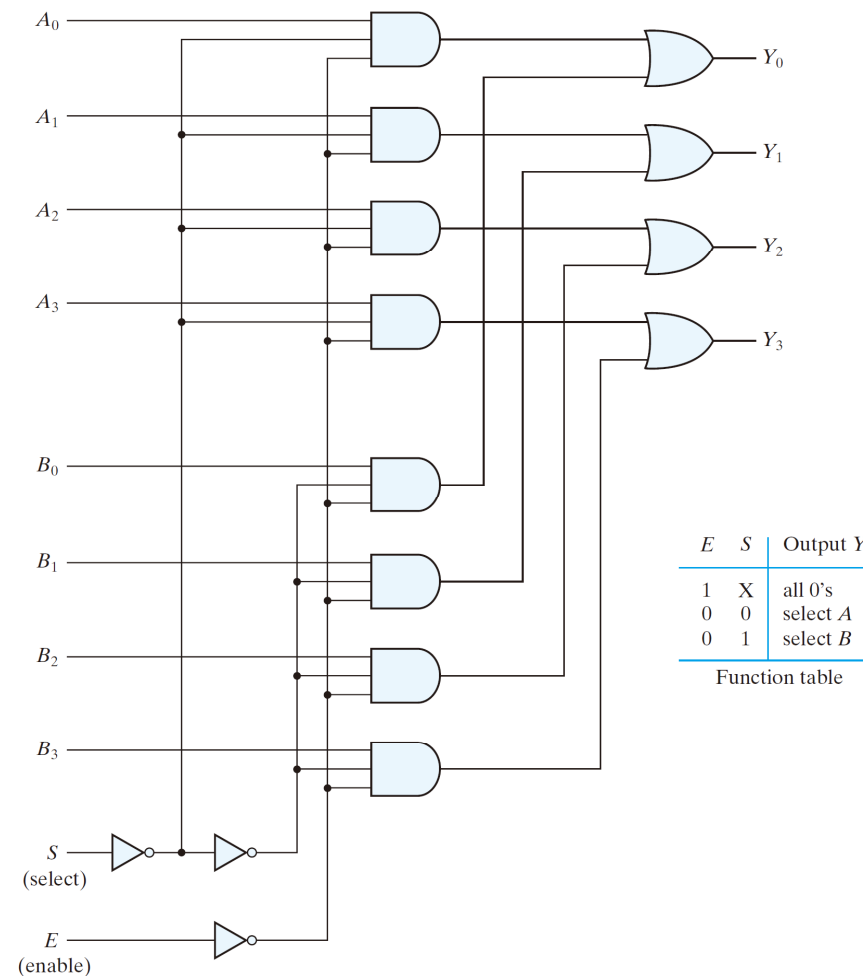(b) Function table

Multiplexor Extension

- n -bit signal selection logic can be constructed using n 1-bit multiplexors:



Multiplexors and Decoders

- ❑ Note that a 2^n -to-1 multiplexor is equivalent to an n -to- 2^n decoder plus an OR gate
 - The decoder decodes the n select lines and determines which input line of the multiplexor will be active
 - An additional OR gate that combines all the output lines of the decoder generate the 1-bit output of the multiplexor
- ❑ Similar to decoders, multiplexors can be used to implement combinational circuits as well

Boolean Function Implementation


- ❑ 2^n -to-1 mux can implement any Boolean function of n input variable
 - Function inputs connects to the select lines of the mux and the minterms of the function maps to 1's in the input lines
 - Inefficient
- ❑ A better solution is to implement the Boolean function using 2^{n-1} -to-1 mux
 - $n-1$ of these variables connects to the selection lines
 - the remaining variable (and its complement) connect to the inputs

Example: $F(x, y, z) = \Sigma(1, 2, 6, 7)$

□ Implement the function with a 4-to-1 multiplexor:

| x | y | z | F | |
|-----|-----|-----|-----|----------|
| 0 | 0 | 0 | 0 | $F = z$ |
| 0 | 0 | 1 | 1 | |
| 0 | 1 | 0 | 1 | $F = z'$ |
| 0 | 1 | 1 | 0 | |
| 1 | 0 | 0 | 0 | $F = 0$ |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 1 | $F = 1$ |
| 1 | 1 | 1 | 1 | |

(a) Truth table

 


(b) Multiplexer implementation

Example: 4-input Function


□ $F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$

| <i>A</i> | <i>B</i> | <i>C</i> | <i>D</i> | <i>F</i> | |
|----------|----------|----------|----------|----------|----------|
| 0 | 0 | 0 | 0 | 0 | $F = D$ |
| 0 | 0 | 0 | 1 | 1 | |
| 0 | 0 | 1 | 0 | 0 | $F = D$ |
| 0 | 0 | 1 | 1 | 1 | |
| 0 | 1 | 0 | 0 | 1 | $F = D'$ |
| 0 | 1 | 0 | 1 | 0 | |
| 0 | 1 | 1 | 0 | 0 | $F = 0$ |
| 0 | 1 | 1 | 1 | 0 | |
| 1 | 0 | 0 | 0 | 0 | $F = 0$ |
| 1 | 0 | 0 | 1 | 0 | |
| 1 | 0 | 1 | 0 | 0 | $F = D$ |
| 1 | 0 | 1 | 1 | 1 | |
| 1 | 1 | 0 | 0 | 1 | $F = 1$ |
| 1 | 1 | 0 | 1 | 1 | |
| 1 | 1 | 1 | 0 | 1 | $F = 1$ |
| 1 | 1 | 1 | 1 | 1 | |

 


Three-State Gates

 - ❑ A multiplexor can be implemented using a tri-state gate (namely, a tri-state buffer)
- ❑ The output states of a tri-state gate are: 0, 1, and high-impedance
 - A high-impedance wire is an “open circuit” wire that will not affect the signal level of the wire it connects to.




 Example: 4-to-1 Multiplexor

- A 4-to-1 Mux implemented with a tri-state buffer:



(a) 2-to-1-line mux

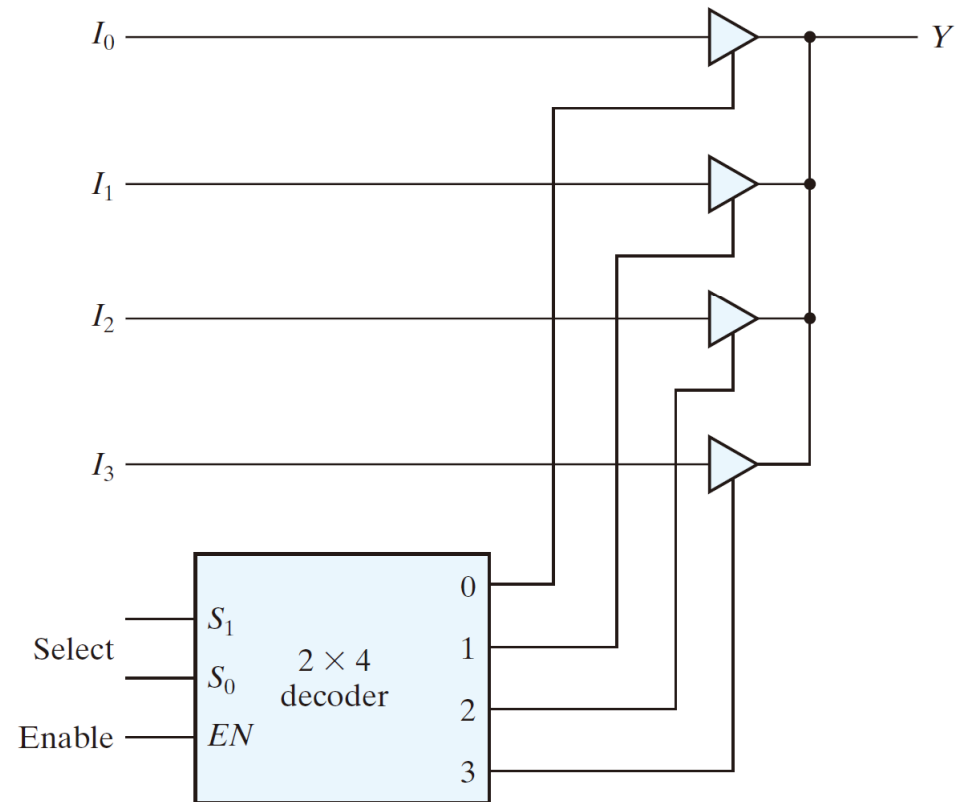

(b) 4-to-1-line mux